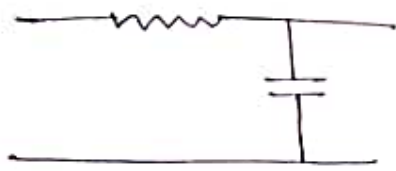


Analog Circuits (EC211)

10/05/2022


→ wave shaping ckt

→ Hybrid model (small signal analysis)



LPC

low pass ckt

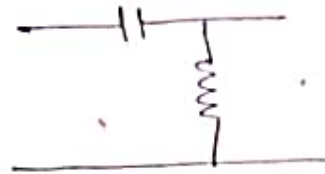

HPC

high pass ckt

RC

Book: Integrated Electronics. → Millman

signal

i_c → Small ~~insta.~~ ~~current~~ ^{signal} current.


i_c → Instantaneous current

I_c → Quiescent value

$$\Delta i_c = i_c$$

$$i_c = i_c - I_c$$

Hybrid Model (h-parameter)

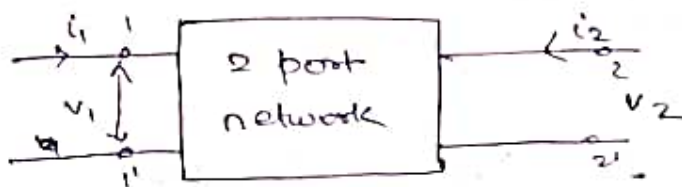

input current and output voltage are
(i) independent terms.

v_1 and i_2 are dependent terms.

$$V_1 = f_1(i_1, v_2) \quad \text{--- (I)}$$

$$i_2 = f_2(i_1, v_2) \quad \text{--- (II)}$$

$$\begin{bmatrix} V_1 \\ i_2 \end{bmatrix} = \underbrace{\begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix}}_{h\text{-parameter}} \begin{bmatrix} i_1 \\ v_2 \end{bmatrix}$$

$$V_1 = h_{11}i_1 + h_{12}v_2 \quad \text{--- (III)}$$

$$i_2 = h_{21}i_1 + h_{22}v_2 \quad \text{--- (IV)}$$

Using eqn (III)

$$h_{11} = \frac{V_1}{i_1} \quad \text{--- (V)} \quad \left(\begin{array}{l} \text{if } v_2 = 0 \\ \text{(} v_2 \text{ is short circuited)} \end{array} \right)$$

$$\left(\begin{array}{l} \text{reverse voltage} \\ \text{amplification} \end{array} \right) \quad h_{12} = \frac{V_1}{v_2} \quad \text{--- (VI)} \quad \left(\begin{array}{l} \text{if } i_1 = 0 \\ \text{open circuit} \end{array} \right)$$

Using eqn (IV)


$$\left(\begin{array}{l} \text{forward current} \\ \text{amplification} \end{array} \right) \quad h_{21} = \frac{i_2}{i_1} \quad \text{--- (VII)} \quad \left(\begin{array}{l} \text{if } v_2 = 0, \text{ short circuited} \\ \text{(unit less)} \end{array} \right)$$

$$h_{22} = \frac{i_2}{v_2} \quad \text{--- (VIII)} \quad \left(\begin{array}{l} \text{if } i_1 = 0, \text{ open circuit} \\ \text{(mho)} \end{array} \right)$$

$$\begin{aligned} h_{11} &\rightarrow h_i \\ h_{12} &\rightarrow h_r \\ h_{21} &\rightarrow h_f \\ h_{22} &\rightarrow h_o \end{aligned}$$

KVL, $N_1 = h_i i_1 + h_r v_2$


KCL, $i_2 = h_f i_1 + h_o v_2$

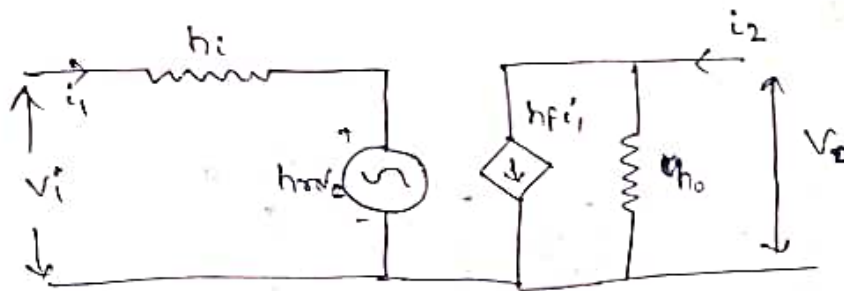

of
Hybrid model 2 port network

CE
CB
CC

16/08/22

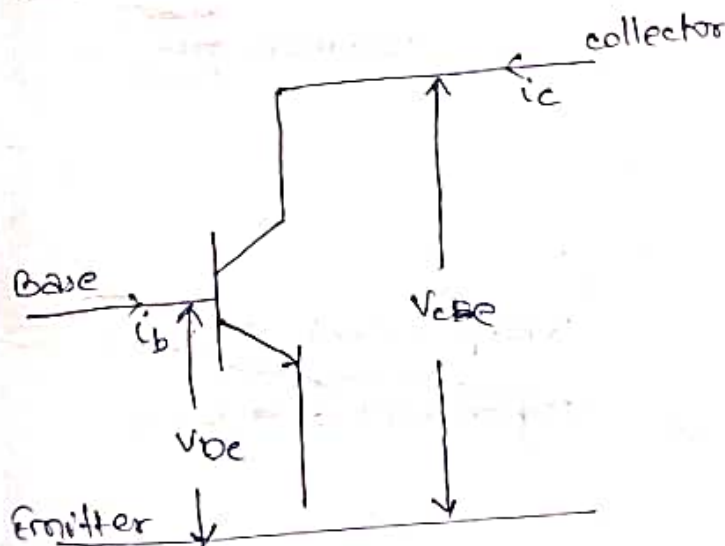

Independent $\rightarrow i_b, V_{cb}$

Dependent $\rightarrow V_{be}, i_c$

$$V_{be} = f_1(i_b, V_{cb})$$

$$i_c = f_2(i_b, V_{cb})$$

$$\begin{bmatrix} V_{be} \\ i_c \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} i_b \\ V_{cb} \end{bmatrix}$$

$$V_{be} = h_{11} i_b + h_{12} V_{cb}$$


$$i_c = h_{21} i_b + h_{22} V_{cb}$$

$$h_{11} = \frac{V_{be}}{i_b} \quad (V_{ce} = 0) = h_{ie}$$

$$h_{12} = \frac{V_{be}}{V_{ce}} \quad (i_b = 0) = h_{re}$$

$$h_{21} = \frac{i_c}{i_b} \quad (V_{ce} = 0) = h_{fe}$$

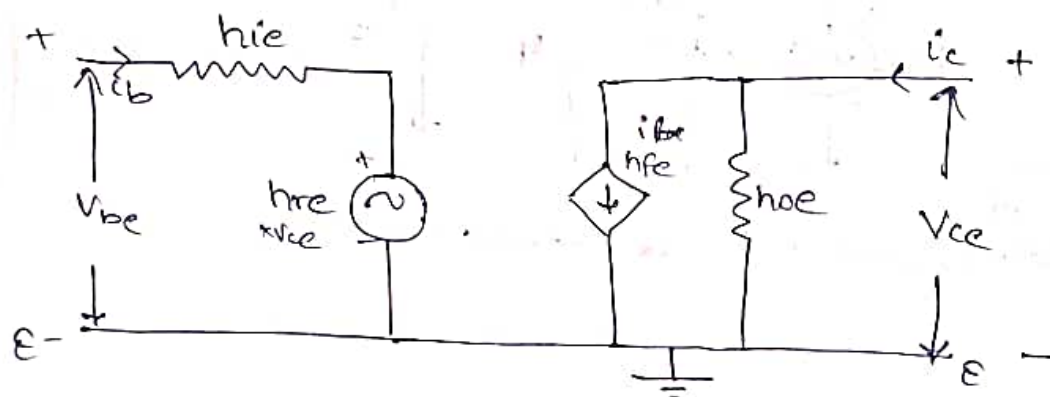
$$h_{22} = \frac{i_c}{V_{ce}} \quad (\text{if } i_b = 0) = \text{hoe}$$



$$V_{be} \approx V_b$$

$$V_{ce} \approx V_c$$

Common ~~Base~~ ~~Emitter~~ ~~Emitter~~

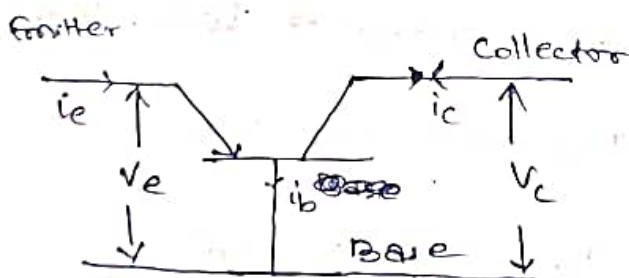

Independent $\rightarrow i_e, V_c$

Dependent $\rightarrow i_c, V_e$

$$\begin{bmatrix} i_e \\ V_e \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} i_c \\ V_c \end{bmatrix}$$

$$v_e = f(i_e, v_c)$$

$$i_c = f(i_e, v_c)$$

$$v_e = h_{11} i_e + h_{12} v_c$$

$$i_c = h_{21} i_e + h_{22} v_c$$


$$h_{11} = \frac{v_e}{i_e} = h_{ie}$$

$$h_{12} = \frac{v_e}{v_c} = h_{re}$$

$$h_{21} = \frac{i_c}{i_e} = h_{fe}$$

$$h_{22} = \frac{i_c}{v_c} = h_{oe}$$


common-emitter, base

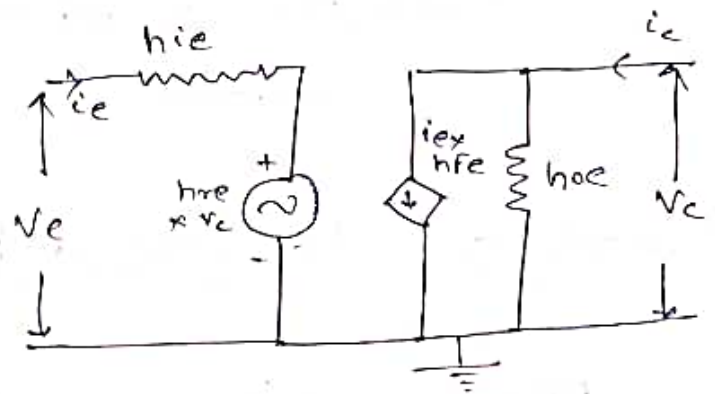

h-Parameter ($I_E = 1.3 \text{ mA}$)

Parameter	CE	CC	CB
h_i	1100Ω	1100Ω	21.6Ω
h_e	2.5×10^{-4}	1	2.9×10^{-4}
h_f	50	-51	-0.98
h_o	$24 \mu\text{A/V}$	$25 \mu\text{A/V}$	$0.49 \mu\text{A/V}$
$1/h_o$	$40 \text{ K}\Omega$	$40 \text{ K}\Omega$	$2.04 \text{ M}\Omega$

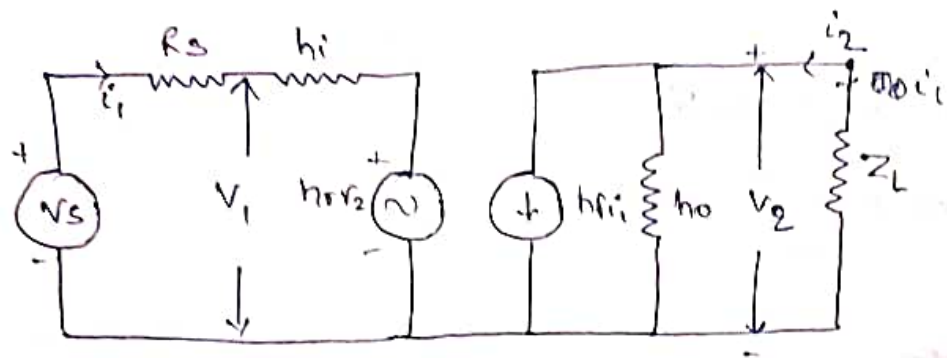Analysis of a transistor amplifier circuit using h-parameter.



Transistor in h-parameter model.

Current gain / current amplification:

$$A_i = \frac{i_L}{i_1} = \frac{-i_2}{i_1} \quad \text{--- (i)}$$

$$i_2 = h_f i_1 + h_o V_2 \quad \text{--- (ii)}$$

$$V_2 = i_2 \times Z_L$$

$$\Rightarrow V_2 = -i_2 \times Z_L \quad \text{--- (iii)}$$

from (ii) and (iii)

$$i_2 = h_f i_1 + h_o i_2 Z_L$$

$$i_2 (1 + h_o Z_L) = h_f i_1$$

$$\frac{i_2}{i_1} = \frac{h_f}{1 + h_o Z_L}$$

$$\Rightarrow \boxed{A_i = \frac{-h_f}{(1 + h_o Z_L)}} \quad \text{--- (iv)}$$

Input Impedance (Z_i)

$$Z_i = \frac{V_1}{i_1}$$

$$V_1 = h_i i_1 + h_r V_2$$

$$Z_i = \frac{h_i i_1 + h_r V_2}{i_1} = h_i + \frac{h_r V_2}{i_1} \quad \text{--- (v)}$$

$$V_2 = -i_2 Z_L = A_i i_1 Z_L \quad \text{--- (vi)}$$

from (v) and (vi)

$$Z_i = h_i + h_r A_i Z_L$$

$$\boxed{Z_i = h_i - \frac{h_f h_r}{Y_L + h_o}} \quad \text{--- (vii)}$$

Voltage Gain/voltage Amplification:


$$A_v = \frac{V_2}{V_1}$$

$$= \frac{A_i i_1 Z_L}{V_1} \quad \text{--- (viii)}$$

$$\boxed{A_v = \frac{A_i Z_L}{Z_i}} \quad \text{--- (ix) (ideal value)}$$


Voltage Amplification Considering R_s as Source
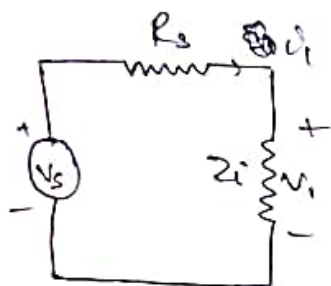
$$AV_s = \frac{V_2}{V_s} = \frac{V_2}{V_1} \frac{V_1}{V_s} = A_v \left(\frac{V_1}{V_s} \right) \quad \text{--- (x)}$$



Thevenin's equivalent of source.

(a)

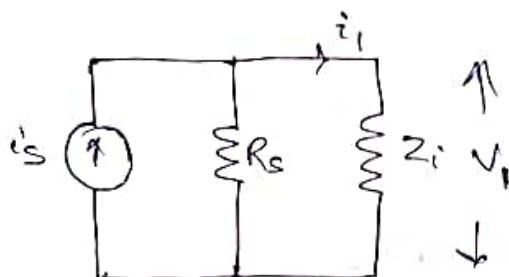

Norton's eqv. of source.

(b)

From fig (a)

$$V_1 = \left(\frac{Z_i}{Z_i + R_s} \right) V_s \quad \text{--- (x1)}$$

$$AV_s = \frac{A_v Z_i}{Z_i + R_s} = \frac{A_i Z_L}{Z_i + R_s} \quad \text{--- (x11) (Real value)}$$

Current Amplification A_{Is} taking source resistance
 R_s :

$$\begin{aligned} A_{Is} &= \frac{-i_2}{i_s} \\ &= \frac{-i_2}{i_1} \frac{i_1}{i_s} \end{aligned}$$

$$A_{Is} = A_i \left(\frac{i_1}{i_s} \right) \quad \text{--- (xiii)}$$

from fig
1b)

$$i_1 = \left(\frac{R_s}{R_s + Z_i} \right) i_s$$

$$A_{Is} = A_i \frac{R_s}{R_s + Z_i} \quad \text{--- (xiv)}$$

considering $R_s = \infty$

$$A_{Is} = A_i$$

Dividing Eqn (xii) by (xiv)

$$A_{vE} = A_{Is} \frac{Z_L}{R_s} \quad \text{--- (xv)}$$

~~Output~~

Output Admittance

$$Z_0 = \frac{1}{Y_0}$$

$$Y_0 = \frac{i_2}{V_2} \quad \text{with } v_s = 0 \text{ and } R_L = \infty \quad \text{--- (vi)}$$

$$Y_0 = h_f \frac{i_1}{V_2} + h_o \quad \text{--- (vii)}$$

Considering h-model and $v_s = 0$

$$R_s i_1 + h_r v_2 + h_i \bar{e}_1 = 0$$

$$\frac{i_1}{V_2} = \frac{-h_r}{h_i + R_s} \quad \text{--- (viii)}$$

Putting i_1 from (viii) to (vii)

$$Y_0 = h_o - \frac{h_f h_r}{h_i + R_s} \quad \text{--- (ix)}$$

Hence output admittance is a function of source resistance (R_s).

17/08/2022

Small Signal Analysis of a Transistor Amplifier:

$$A_i = \frac{-h_f}{1+h_o Z_L}$$

$$Y_o = h_o - \frac{h_f h_r}{h_i + R_s} \approx \frac{1}{Z_o}$$

$$Z_i = h_i + h_r A_i Z_L$$

$$A_{V_o} = \frac{A_v Z_i}{Z_i + R_s} = \frac{A_i Z_L}{Z_i + R_s}$$


$$A_v = \frac{A_i Z_L}{Z_i}$$


$$A_{i_s} = \frac{A_i R_s}{Z_i + R_s} = A_{V_s} \frac{R_s}{Z_L}$$

Simplified Hybrid CE Model:

$$\left. \begin{matrix} h_i & h_r \\ h_f & h_o \end{matrix} \right\} \text{neglected} \quad h_o R_L < 0.1$$

5 to 10% error.

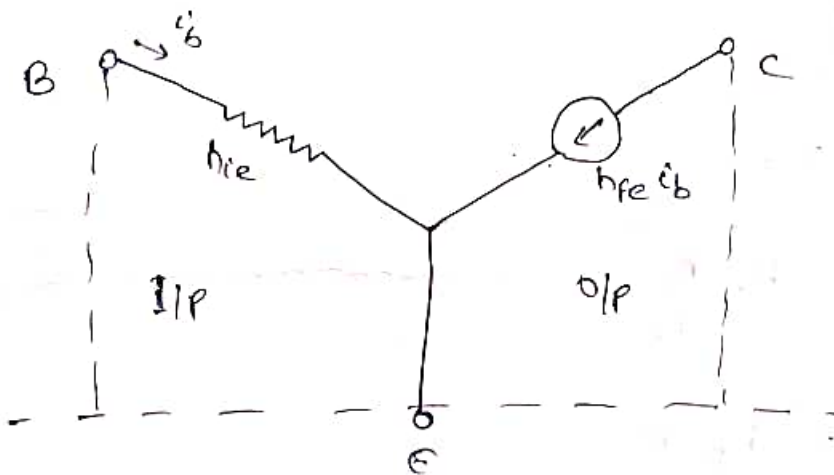

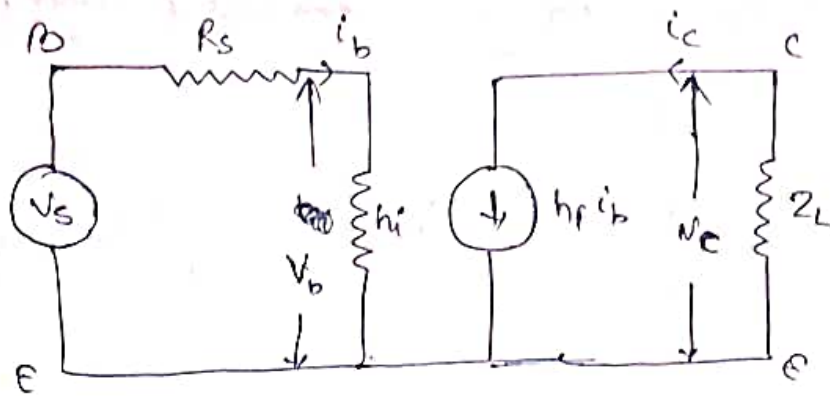

Current Gain:

$$A_i = \frac{-h_{fe}}{1 + h_{oe} R_L} \approx -h_{fe} \quad (h_{oe} R_L < 0.1)$$

$$\boxed{A_i = -h_{fe}}$$

Input Impedance:

$$R_i = h_{ie} + h_{re} A_i R_L$$

$$= h_{ie} \left[1 - \underbrace{\frac{h_{re} h_{fe}}{h_{ie} h_{oe}}}_{< 0.5} \frac{|A_i|}{h_{fe}} \underbrace{h_{oe} R_L}_{< 0.1} \right]$$



$$\boxed{R_i = h_{ie}}$$

Voltage Gain:



$$A_v = A_i \frac{R_L}{R_i}$$

$$= -h_{fe} \frac{R_L}{h_{ie}}$$

Simplified Hybrid CC Model:

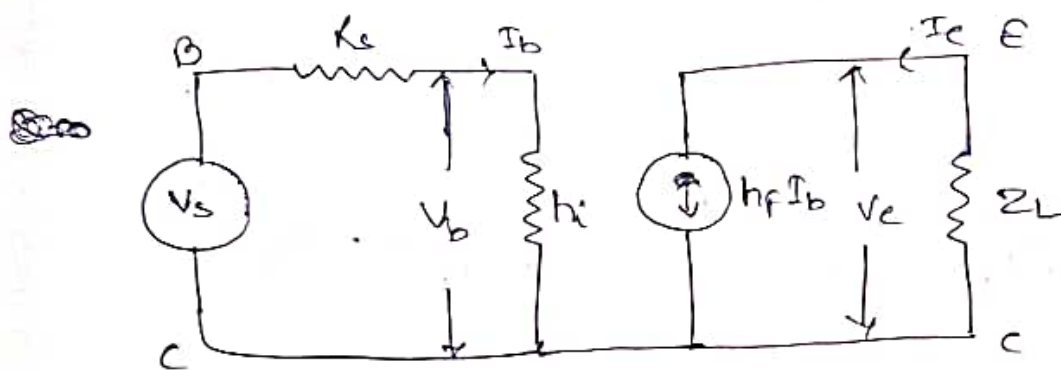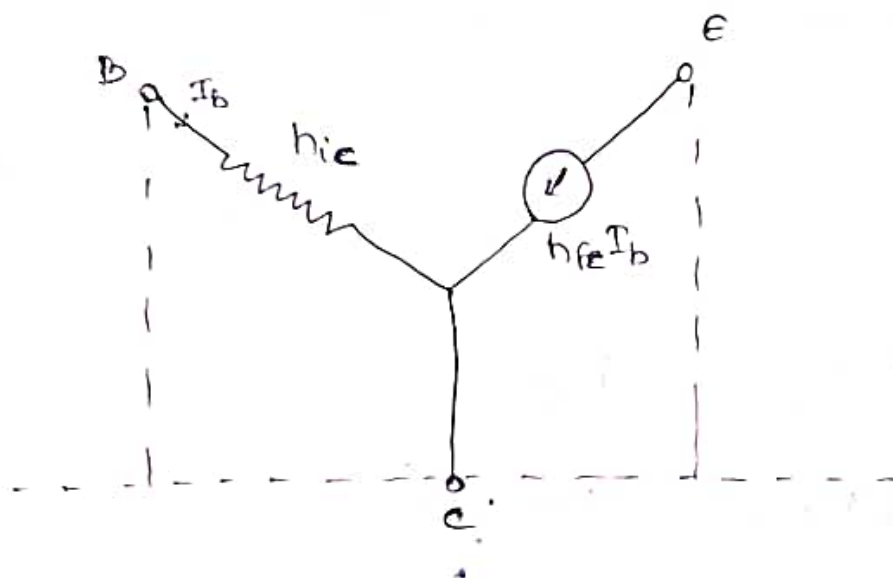

Simplified Hybrid CB Model:

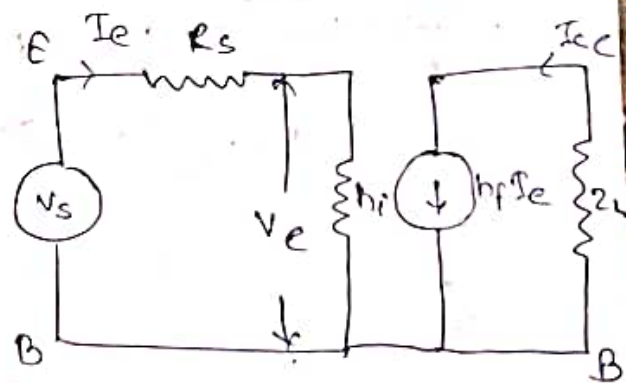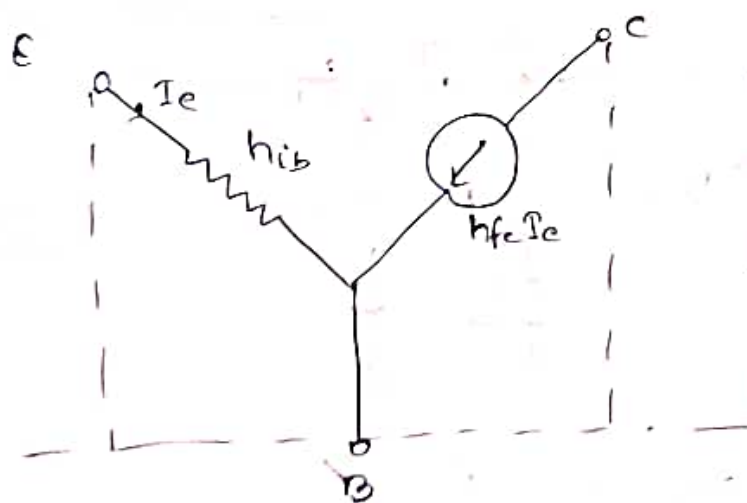

Conversion formula:

h_{ie} h_{ic}
 $CE \rightarrow CC$

$$h_{ic} = h_{ie}$$

$$h_{rc} = 1$$

$$h_{fc} = -(1 + h_{fe})$$

$$h_{oc} = h_{oe}$$

$CB \rightarrow CE$

$CE \rightarrow CB$
($b \rightarrow e$)

$$h_{ib} = \frac{h_{ie}}{1 + h_{fe}}$$


$$h_{rb} = \frac{h_{ie} h_{oe}}{1 + h_{fe}} - h_{re}$$

$$h_{fb} = \frac{-h_{fe}}{1 + h_{fe}}$$

$$h_{ob} = \frac{h_{oe}}{1 + h_{fe}}$$

Q. Find h_{re} in terms of CB h-parameters:

Ans.

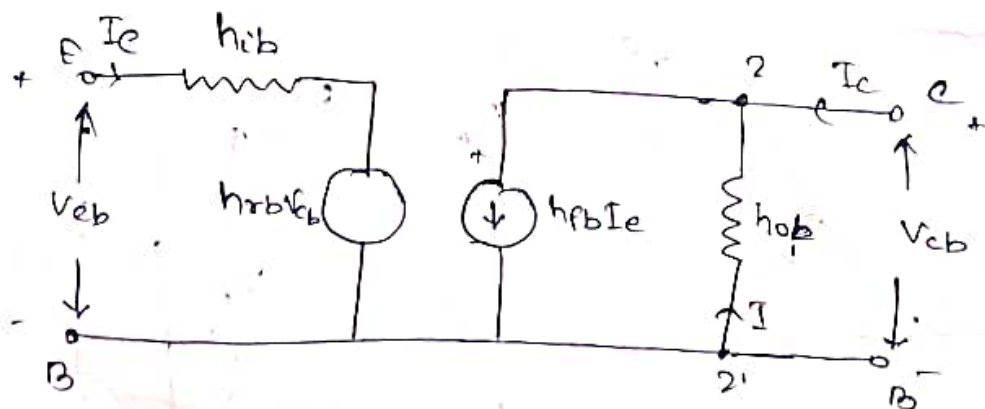

$$h_{re} = \frac{V_{be}}{V_{ce}} \quad (I_b = 0)$$

$$= \frac{V_{bc} + V_{ce}}{V_{ce}} \bigg|_{I_b=0}$$

$$h_{re} = \left(1 + \frac{V_{bc}}{V_{ce}} \right) \bigg|_{I_b=0}$$

At node

$$I_e + I_b + I_c = 0$$

$$I_b + I_c = 0$$

$$I_b = -I_c$$

Applying KCL at 2

$$h_{fb} I_e + I_c = 0$$

$$\Rightarrow I_e (1 + h_{fb}) = 0$$

$$= h_{ob} V_{bc}$$

$$\Rightarrow \boxed{I_c = I_e (1 + h_{fb}) = h_{ob} V_{bc}}$$

Applying KVL E-B-C-E :

$$I_e h_{ib} + h_{rb} V_{cb} + V_{bc} + V_{ce} = 0$$

$$I_e = \frac{h_{ob} V_{bc}}{1 + h_{fb}}$$

$$\Rightarrow \frac{h_{ob} V_{bc}}{1 + h_{fb}} h_{ib} + h_{rb} V_{bc} + V_{bc} + V_{ce} = 0$$

$$\Rightarrow V_{bc} \left(\frac{h_{ob} h_{ib}}{1 + h_{fb}} + h_{rb} + 1 \right) + V_{ce} = 0$$

$$V_{ce} = -V_{bc} \left(\frac{h_{ob}h_{ib} - h_{rb} + 1}{1+h_{fb}} \right)$$

$$\frac{V_{ce}}{V_{bc}} + 1 = - \frac{h_{ob}h_{ib} - h_{rb} + 1}{1+h_{fb}}$$

$$h_{re} = h_{rb} - \frac{h_{ob}h_{ib}}{1+h_{fb}}$$

$$h_{re} = \frac{h_{rb}(1+h_{fb}) - h_{ob}h_{ib}}{(1+h_{fb})}$$

$$\frac{V_{bc}}{V_{ce}} = \frac{-(1+h_{fb})}{h_{ib}h_{ob} + (1-h_{rb})(1+h_{fb})}$$

$$h_{re} = 1 + \frac{V_{bc}}{V_{ce}} = \frac{h_{ib}h_{ob} - (1+h_{fb})h_{rb}}{h_{ib}h_{ob} + (1-h_{rb})(1+h_{fb})} \quad \text{exact expression}$$

$$h_{rb} \ll 1$$

$$h_{ob}h_{ib} \ll 1+h_{fb}$$

$$h_{re} \approx \frac{h_{ib}h_{ob}}{1+h_{fb}} - h_{rb} \quad \text{Approximate expression.}$$

Q. h_{rb} in terms of CE.

A.W.

CE with resistance R_e : Stabilization

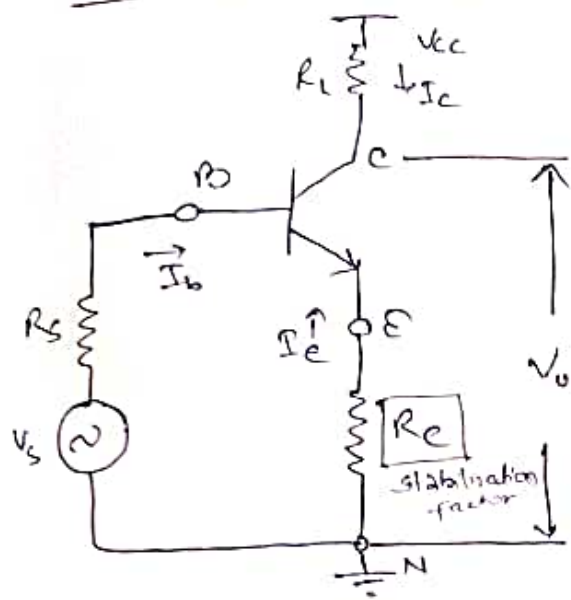


Fig. CE Amplifier
with emitter
resistance

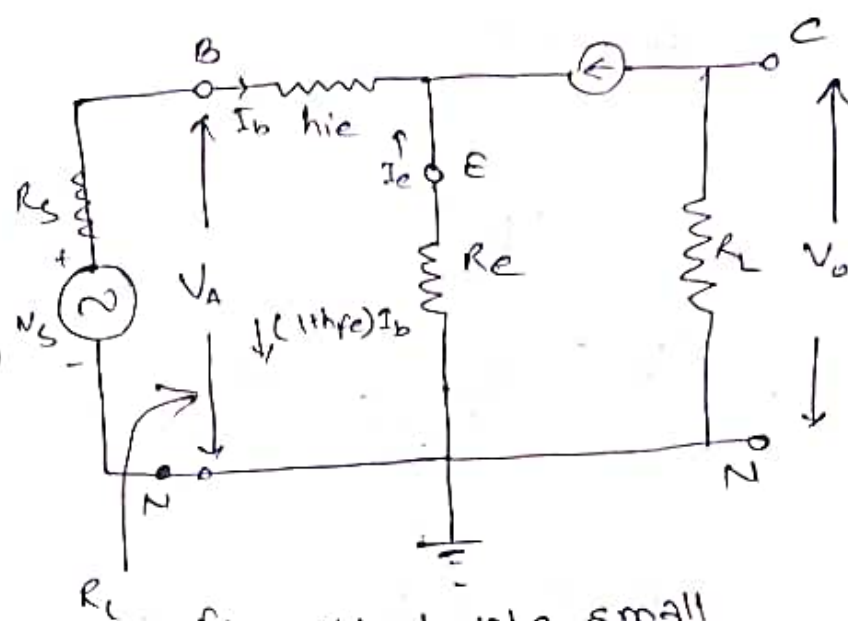


Fig. Appropriate small
signal equivalent ckt.

Transistor affected by:

- Aging
- Temp. of operation
- ~~Q factor~~ Q point.

$$A_v = -\frac{R_L}{R_e}$$

Approximate Solution

$$A_i = \frac{-I_c}{I_b}$$

$$= \frac{-h_{fe} I_b}{I_b}$$

$$\Rightarrow \boxed{A_i = -h_{fe}} \quad \text{--- (i)}$$

$$\textcircled{ii} \quad V_i = h_{ie} I_b + (1+h_{fe}) I_b R_e$$

$$R_i = \frac{V_i}{I_b}$$

$$\boxed{R_i = h_{ie} + (1+h_{fe}) R_e} \quad \text{--- (ii)}$$

$$(1+h_{fe}) R_e = 51k \gg h_{ie} (1k) \quad \text{--- (iii)}$$

$$R_e = 1k\Omega$$

$$h_{fe} = 50$$

$$\boxed{R_i = f(R_e)} \quad \text{--- (iv)}$$

Higher emitter resistance, higher input impedance.

$$A_v = \frac{A_i R_L}{R_e} \quad \frac{A_i R_L}{R_i}$$

$$= \frac{R_L}{h_{ie} + (1+h_{fe})R_e}$$

$$\approx \frac{-h_{fe}}{h_{ie} + (1+h_{fe})R_e}$$

$$A_v = \frac{A_i R_L}{R_i}$$

$$A_v = \frac{-h_{fe} R_L}{h_{ie} + (1+h_{fe})R_e}$$

$$\approx \frac{-h_{fe} R_L}{(1+h_{fe})R_e}$$

$$A_v \approx \frac{-R_L}{R_e} \quad \text{--- (v)}$$

$$\Rightarrow A_v \propto R_L$$

$$\propto 1/R_e$$


$$\npropto h_{ie}, h_{oe}, h_{re}, h_{fe}$$

Summary Table


$$h_{oe} (R_e + R_L) \leq 0.1$$

	CE	CE with R_e	CC	CB
A_i	$-h_{fe}$	$-h_{fe}$	$1+h_{fe}$	$-h_{fe} = \frac{h_{fe}}{1+h_{fe}}$
R_i	h_{ie}	$h_{ie} + (1+h_{fe})R_e$	$h_{ie} + (1+h_{fe})R_L$	$h_{ib} = \frac{h_{ie}}{1+h_{fe}}$
A_v	$-\frac{h_{fe}R_L}{h_{ie}}$	$-\frac{h_{fe}R_L}{R_i} = -\frac{R_L}{R_e}$	$1 - \frac{h_{ie}}{R_i}$	$h_{fe} \frac{R_L}{h_{ie}}$
R_o	∞	∞	$\frac{R_o + h_{ie}}{1+h_{fe}}$	∞
R_o'	R_L	R_L	$R_o \parallel R_L$	R_L

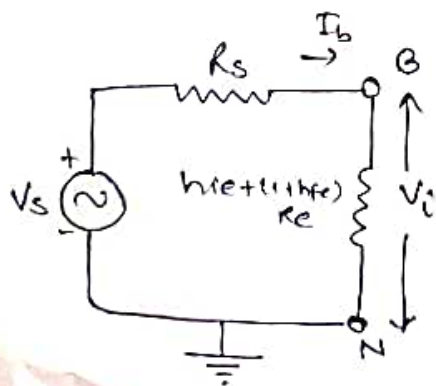Looking into Base and Emitter of Transistor:



(a) Equivalent ckt looking into base

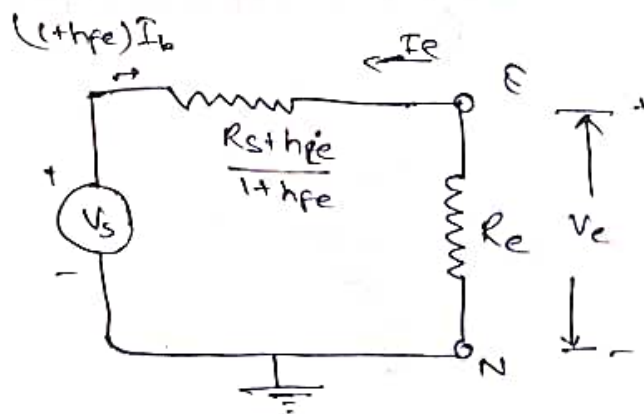

(b) Looking into emitter.

$$I_b = \frac{V_s}{R_s + h_{ie} + (1+h_{fe})R_e}$$

VI

$$V_e = (1+h_{fe})I_b \times R_e$$

$$= \frac{(1+h_{fe}) \times V_s}{R_s + h_{ie} + (1+h_{fe})R_e} \times R_e$$

$$V_e = \frac{V_s R_e}{\frac{R_s + h_{ie}}{(1+h_{fe})} + R_e}$$



VII

$$I_e = -\frac{V_e}{R_e}$$



$$I_e = \frac{-V_s}{\frac{(R_s + h_{ie})}{(1+h_{fe})} + R_e}$$

$$I_b = \frac{-I_e}{(1+h_{fe})}$$

Dual of Miller's Theorem:

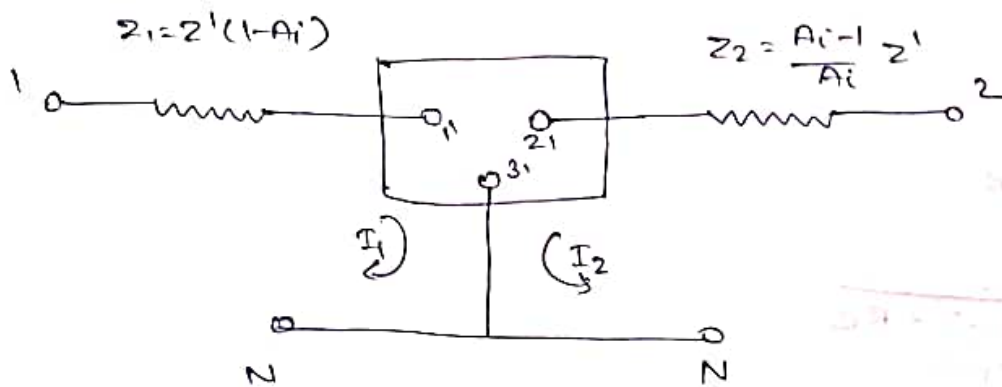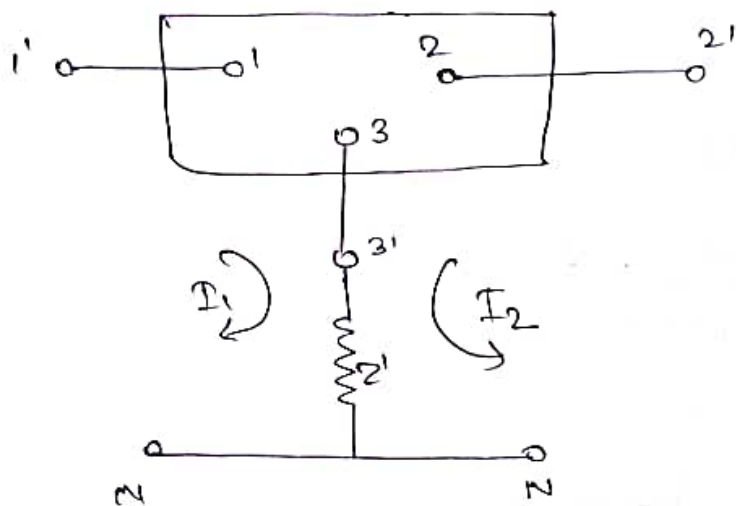

24/08/22 : CE with R_e .

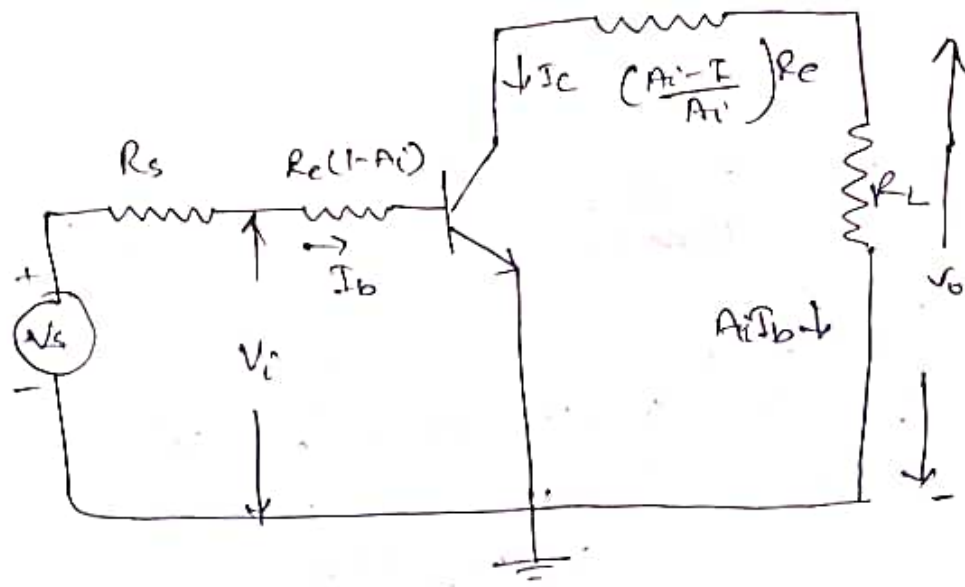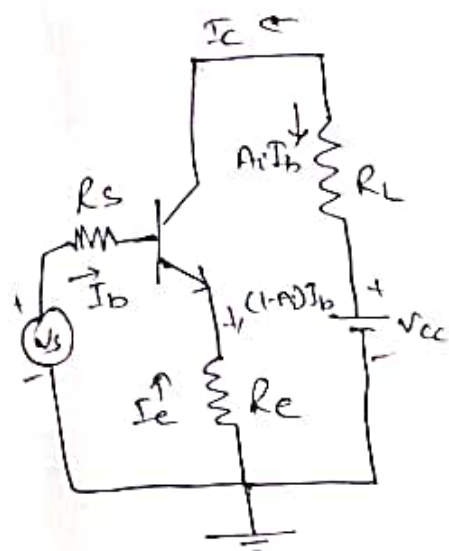

Transistor Amplifier stage with unbypassed emitter resistor.

Small signal Equ. Circuit (Miller's)

$$A_i = -\frac{I_c}{I_b} = -h_{fe}$$

Validity of Approximation:

Effective load impedance

$$R_L' = R_L + \left(\frac{A_i - 1}{A_i} \right) R_e \quad \text{--- (VIII)}$$

$$h_{oe} R_L' = h_{oe} (R_L + R_e) \leq 0.1$$

$$A_i = -h_{fe}$$

$$h_{fe} \gg 1$$

$$A_v = -\frac{R_L}{R_e}$$

$$A_v \gg 1$$

$$R_e \ll R_L$$

The Exact Solution:

$i_f \rightarrow \text{approx.}$
 $0, \sigma \rightarrow \text{exact.}$

$$A_i = \frac{-h_{fe}}{1 + h_{oe} R_L}$$

$$A_i = \frac{-h_{fe}}{1 + h_{oe} \left(R_E + \left(\frac{A_i - 1}{A_i} \right) R_L \right)} \quad \text{--- (X)}$$

$$h_{oe} R_E \ll h_{fe}$$

$$A_i \approx -h_{fe}$$


$$A_i = \frac{h_{oe} R_E - h_{fe}}{1 + h_{oe} (R_L + R_E)} \quad \text{--- (XI)}$$

$$R_i = \frac{V_i}{I_b} = (1 - A_i) R_E + h_{ie} + h_{re} A_i R_i \quad \text{--- (XII)}$$

$$A_v = \frac{A_i R_L}{R_i} \quad \text{--- (XIII)}$$

$$R_o = \frac{1}{h_{ob}} + (R_s + h_{ie}) \left(1 + \frac{1}{h_{oe} R_E} \right) \quad \text{--- (XIV)}$$

Emitter follower:

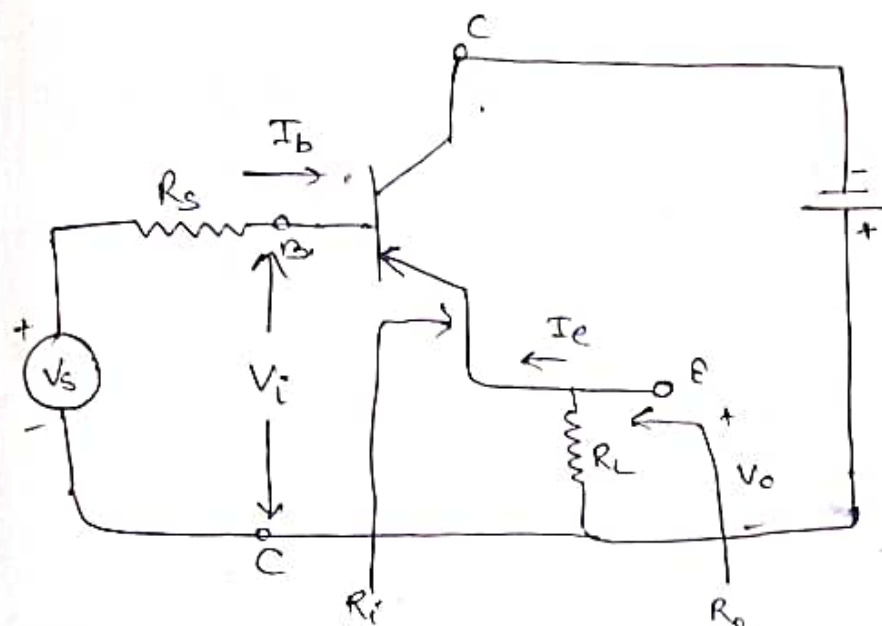

CC

$$A_v \approx 1$$

~~Av ≈ 1~~

$R_e = \text{very high (k}\Omega\text{)}$

$R_o = \text{Low (}\Omega\text{)}$

Impedance
matcher

* Buffer circuit

* Works upto $500k\Omega$ (R_e).

* emitter following change at the base of transistor.

* change to base will change the output.


* No phase shift b/w current and voltage.

$$A_i = \frac{-I_e}{I_b} = \frac{-h_{fc}}{1 + h_{oc}R_L} = \frac{1 + h_{fe}}{1 + h_{oe}R_L} \quad \text{--- (I)}$$


$$R_i = \frac{V_i}{I_b} = h_{ie} + h_{rc}A_iR_L = h_{ie} + A_iR_L \quad \text{--- (II)}$$

$$A_v = \frac{V_o}{V_i} = \frac{A_iR_L}{R_i} = \frac{R_i - h_{ie}}{R_i} = 1 - \frac{h_{ie}}{R_i} \quad \text{--- (III)}$$

Cascading:

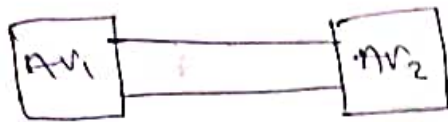

$$AV_1 + AV_2$$

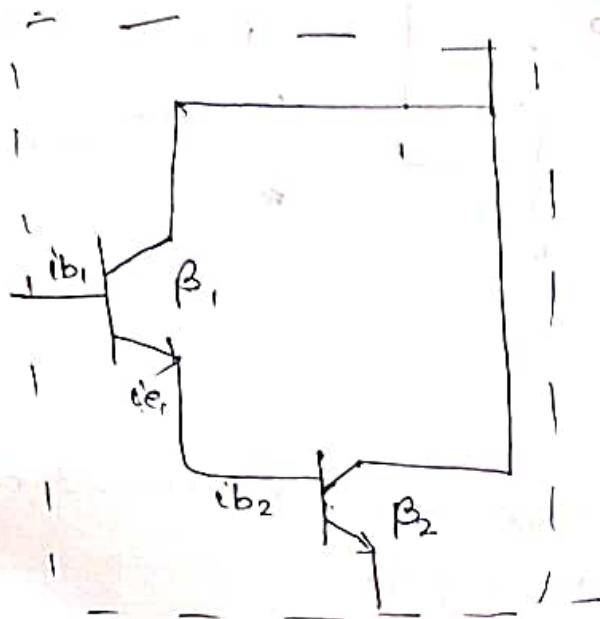

Sydney Darlington
Bell-Lab

1953.

$$\beta = \beta_1 \beta_2$$

$$= \beta^2 \quad (\text{for same transistor})$$

~~Sydney~~ Darlington Pair
or

Super- β Transistor.

* $\gg 500k\Omega$ for Buffering.

* $R_e \rightarrow \text{high}$


* $R_o \rightarrow \text{low}$

* Dissipates a lot of heat

* $V_{BE} = V_{BE1} + V_{BE2}$

* Slow and noisy.

Darlington Pair:

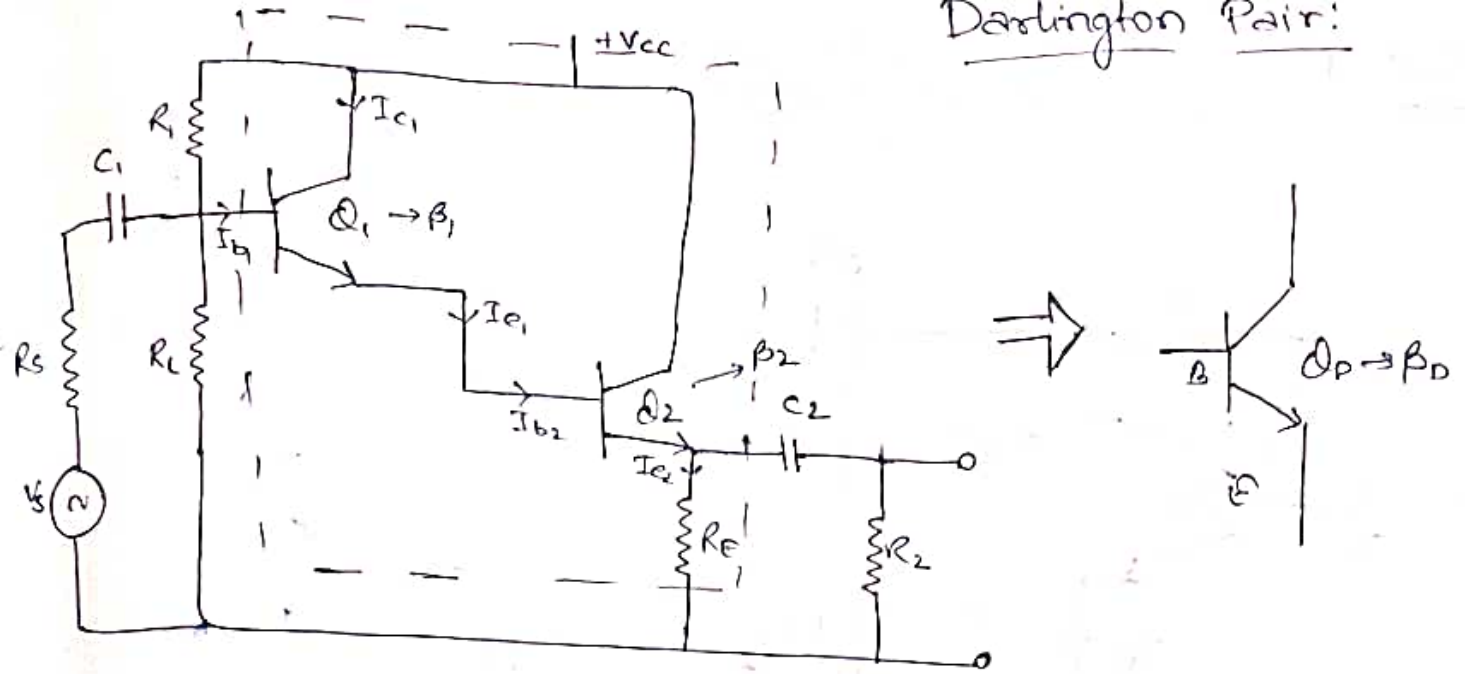

$$\text{Current gain} = \frac{I_{E2}}{I_{B1}}$$

$$I_E \approx I_C = \beta I_{B1}$$

$$\text{Current gain} = \frac{\beta_2 I_{B2}}{I_{B1}}$$

$$I_{C1} = I_{B2} \text{ (same branch)}$$

$$= \beta_2 \left(\frac{I_{C1}}{I_{B1}} \right)$$


$$= \beta_2 \beta_1 \left(\frac{I_{B1}}{I_{B1}} \right)$$

$$\beta_{\text{total}} = \beta_1 \beta_2$$

$$\beta_1 = \beta_2 = \beta \text{ (if same transistor)}$$

$$\Rightarrow \boxed{\beta_{\text{total}} = \beta^2} \text{ super } \beta\text{-Transistor.}$$


DC Analysis of Darlington Pair:

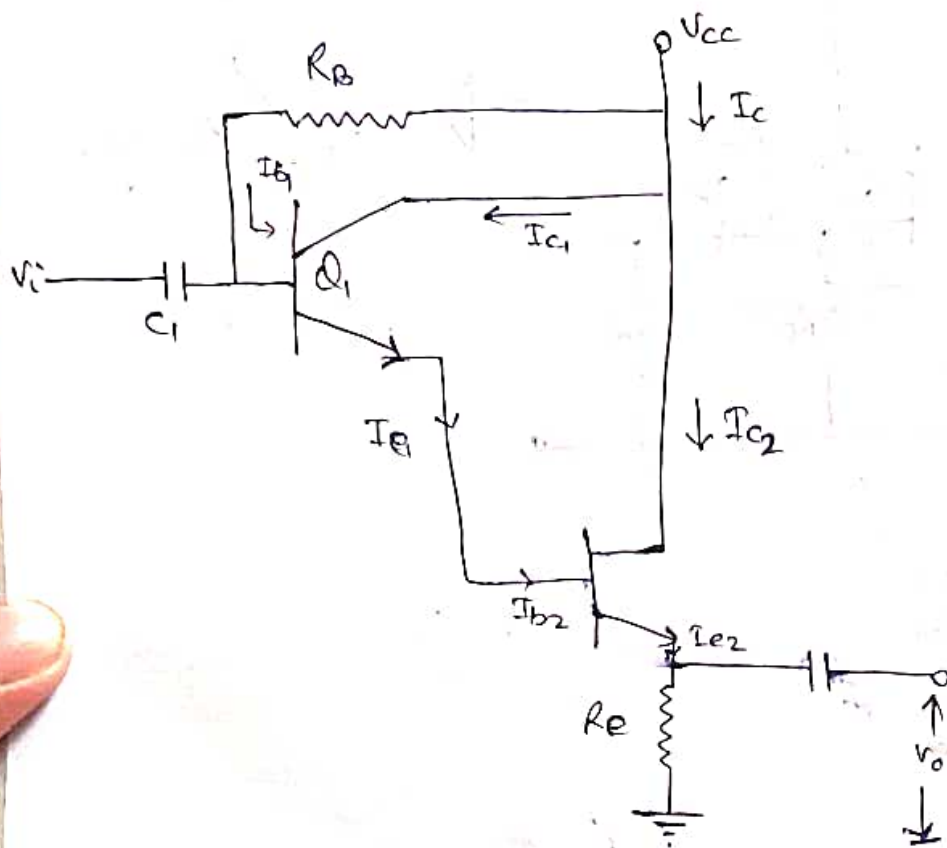


C_1 and C_2 are coupling capacitors.

for DC analysis reactance would be infinity.

Hence capacitors will be open circuited.

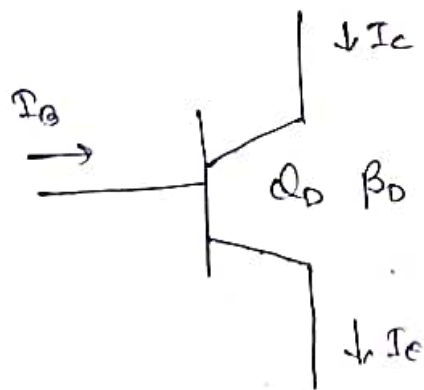

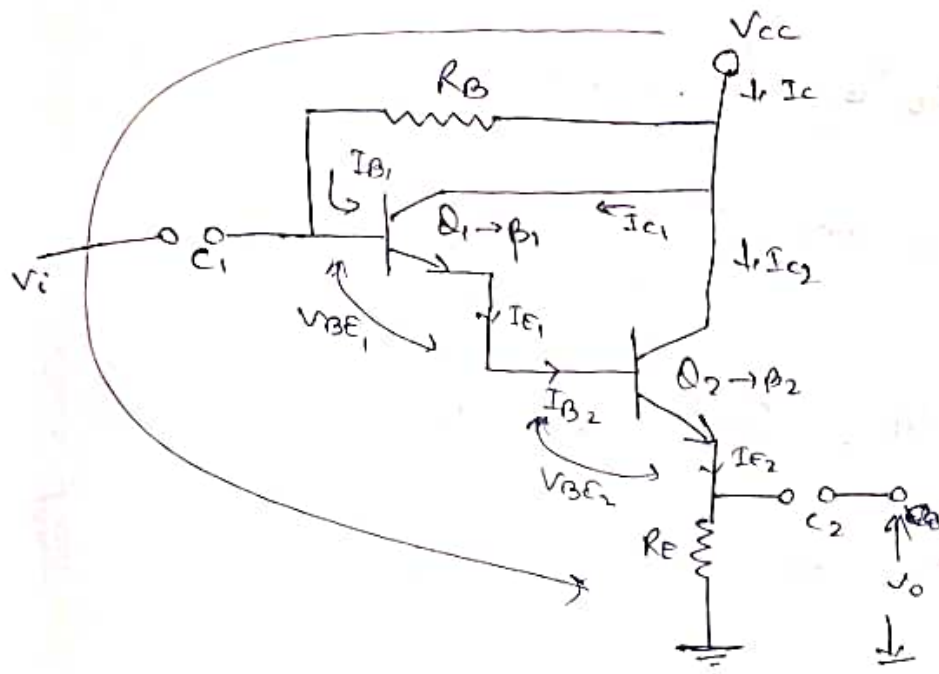

O/P voltage = V_E

Apply KVL:

$$V_{CC} - I_{B1} R_B - V_{BE1} - V_{BE2} - I_{E2} R_E = 0 \quad \text{--- (1)}$$

$$I_{B1} = I_B, \quad I_{E2} = I_E$$

$$I_E = I_C + I_B$$

$$I_E = I_{C2} + I_{B2} \quad (\text{with reference to Darlington Pair})$$

$$= \beta_2 I_{B2} + I_{B2}$$

$$\Rightarrow I_E = I_{B2} (\beta_2 + 1)$$

$$\approx I_{B2} \beta_2$$

$$I_{B2} = I_{E1} \quad (\text{same branch})$$

$$\Rightarrow I_E = \beta_2 I_{E1}$$

$$I_E = \beta_2 \beta_1 I_{B1}$$

$$\Rightarrow \boxed{I_E = \beta_D I_B} \quad \text{--- (11)}$$

from (1) and (11)

$$V_{CC} - I_B R_B - V_{BE1} - V_{BE2} - \beta_D I_B R_E = 0$$

$$\textcircled{2} \quad V_{BE1} + V_{BE2} = V_{BE}$$

$$\Rightarrow V_{CC} - I_B R_B - V_{BE} - \beta_D I_B R_E = 0$$

$$\Rightarrow V_{CC} - V_{BE} - I_B (R_B + \beta_D R_E) = 0$$

$$\Rightarrow \boxed{I_B = \frac{V_{CC} - V_{BE}}{R_B + \beta_D R_E}}$$


Sly:

$$\boxed{I_E = \frac{\beta_D (V_{CC} - V_{BE})}{R_B + \beta_D R_E}}$$

$$\boxed{V_E = V_{BE} = I_E R_E}$$

$$\boxed{V_E = \frac{\beta_D R_E (V_{CC} - V_{BE})}{R_B + \beta_D R_E}}$$


Cascode Amplifier:

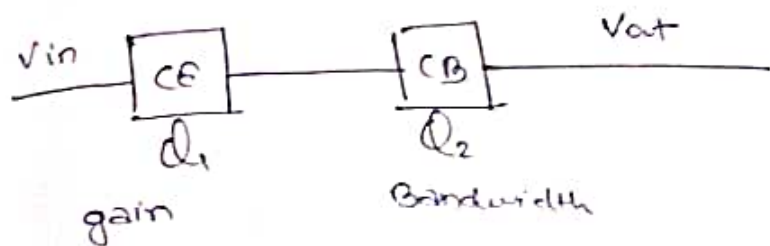




cascode provides
high gain and high
b/w.

Stability high

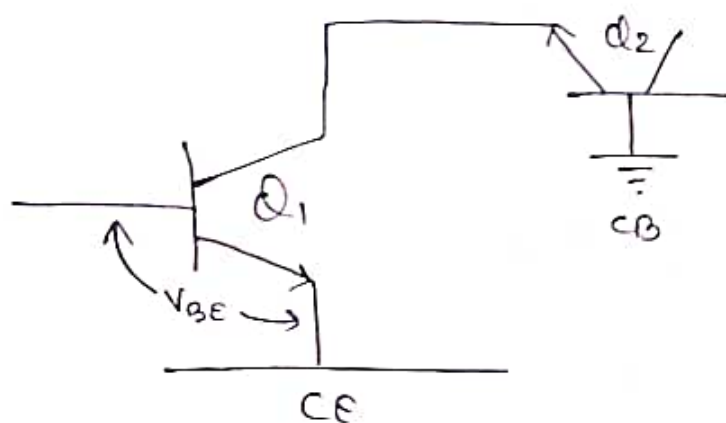~~R_e and R_o high~~
High input and O/P
impedance.





Cascode Amplifiers:

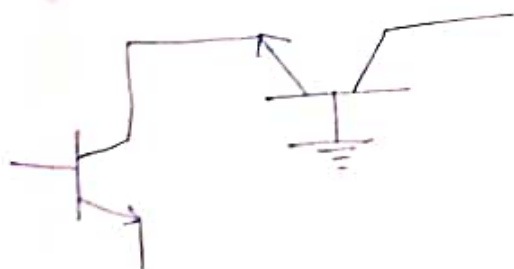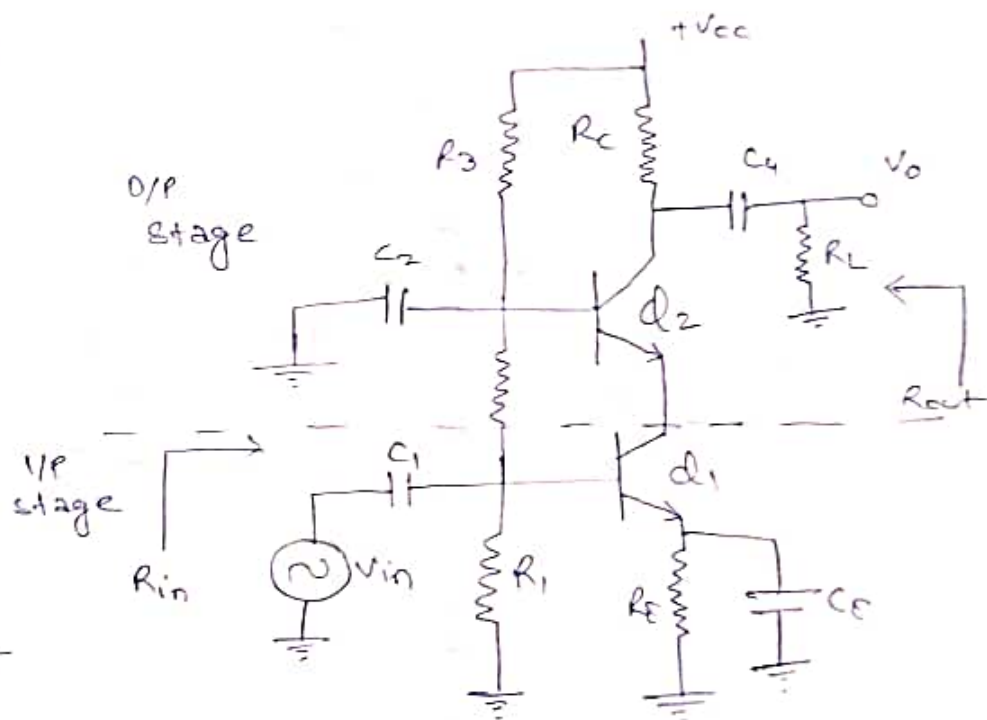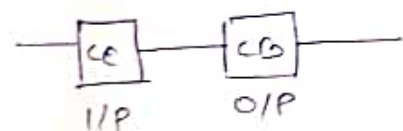


AC Analysis:

- Ground each DC component
- Use only AC V/P, or O/P
- Short ckt all capacitors
- Replace transistor with its simplified value/diagram.
- We will get R_i, R_o, A_i, A_v

~~AC Analysis~~

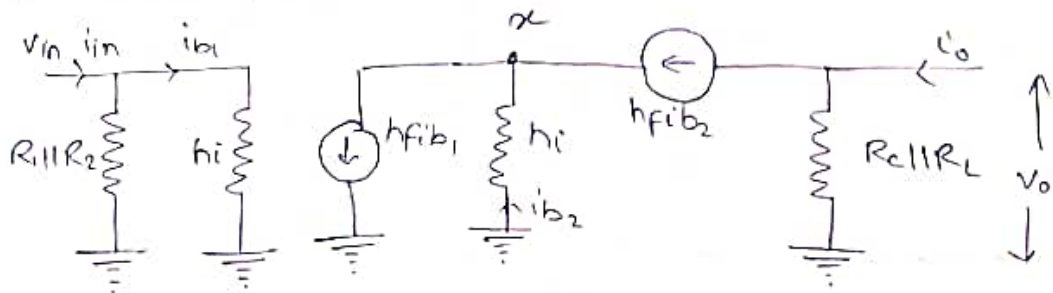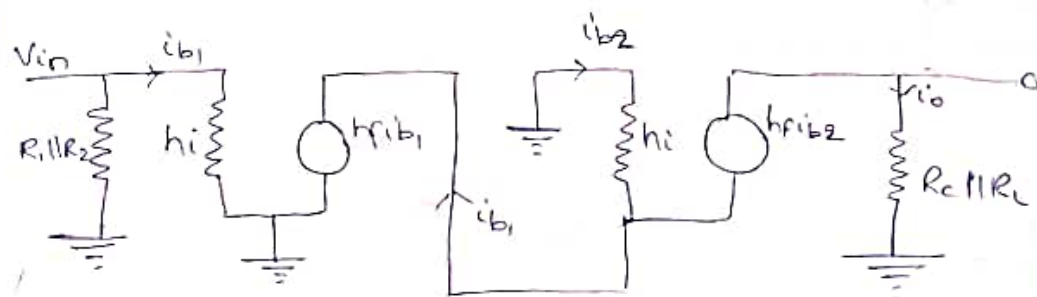

(internal impedance very high)

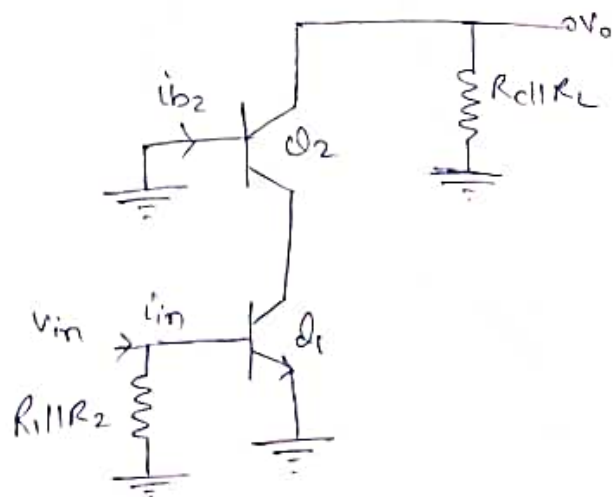

I/P Impedance, $R_i = R_1 \parallel R_2 \parallel h_i$

O/P Impedance, $R_o = R_c \parallel R_L$

$$i_o = -h_f i_{b2} \quad \text{--- (II)}$$

Nodal analysis at x

$$i_{b2} + h_f i_{b2} = h_f i_{b1}$$

$$i_{b2} (h_f + 1) = h_f i_{b1}$$

$$i_{b2} = \frac{h_f i_{b1}}{h_f + 1} \quad \text{--- (IV)}$$

$$i_{b1} = \frac{V_{in}}{h_i} \quad \text{--- (V)}$$

Putting (V) into (IV)

$$i_{b2} = \frac{h_f}{h_f + 1} \left(\frac{V_{in}}{h_i} \right)$$

Put i_{b2} in (II)

$$\text{Hence } i_o = \frac{-h_f^2 V_{in}}{h_i (1 + h_f)} \quad \text{--- (VI)}$$

$$V_o = i_o (R_c \parallel R_L)$$

$$= \frac{-h_f^2 (R_c \parallel R_L)}{h_i (1 + h_f)} V_{in}$$

$$A_v = \frac{V_o}{V_{in}} = \frac{-h_f^2 (R_c \parallel R_L)}{h_i (1 + h_f)}$$

for current gain:

$$i_{b1} = \left(\frac{R_1 \parallel R_2}{h_i + R_1 \parallel R_2} \right) i_{in} \quad \text{--- (vii)}$$

from (vii) and (iv)

$$i_{b2} = \frac{h_f [R_1 \parallel R_2] i_{in}}{(1+h_f)(h_i + R_1 \parallel R_2)} \quad \text{--- (viii)}$$

from (iii)

$$i_{b2} = \frac{-i_o}{h_f}$$


~~from~~

$$\Rightarrow \frac{-i_o}{h_f} = \frac{h_f i_{in} [R_1 \parallel R_2]}{(1+h_f)(h_i + R_1 \parallel R_2)}$$

$$\Rightarrow \boxed{\frac{-i_o}{h_f} = \frac{-h_f^2 (R_1 \parallel R_2)}{(1+h_f)(R_1 \parallel R_2 + h_i)} = A_i}$$

DC Analysis:

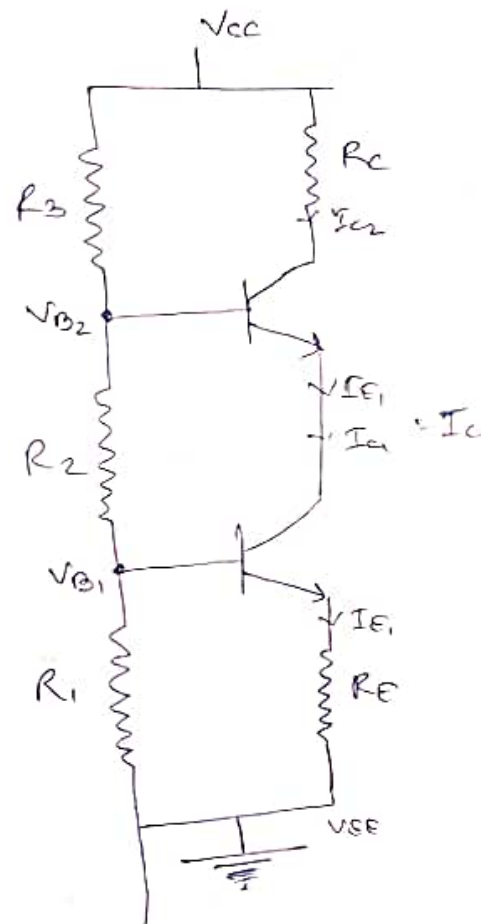- DC component (+Vcc)
- AC component nullify
- Capacitor O.C.



$$V_{B1} = \left[\frac{R_1}{R_1 + R_2 + R_3} \right] (V_{CC} + V_{EE}) \quad \text{--- (i)}$$

$$V_{B2} = \left[\frac{R_1 + R_2}{R_1 + R_2 + R_3} \right] (V_{CC} + V_{EE}) \quad \text{--- (ii)}$$

$$I_{B1} = I_{B2} = 0$$

$$I_{C1} = I_{C2} = I_{E1} = I_{E2} = I_C$$

Applying KVL in lower loop

$$V_{B1} = V_{BE} + I_E R_E - V_{EE}$$

$$I_E = \frac{V_{B1} - V_{BE} + V_{EE}}{R_E}$$


Linear Wave Shaping:

* Sinusoidal

* Non-sinusoidal

Non-sinusoidal:

(i) Step Signal

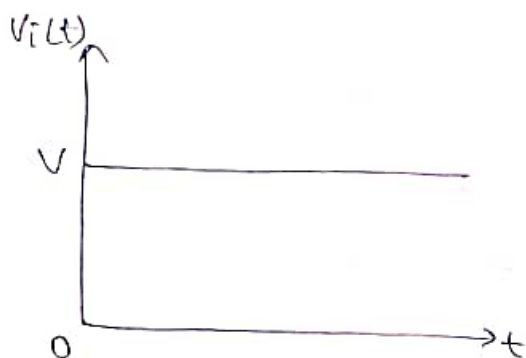


$$V_i(t) = V$$

$$t > 0$$

$$V_i(t) = 0, \text{ otherwise}$$

(ii) Pulse 1/P

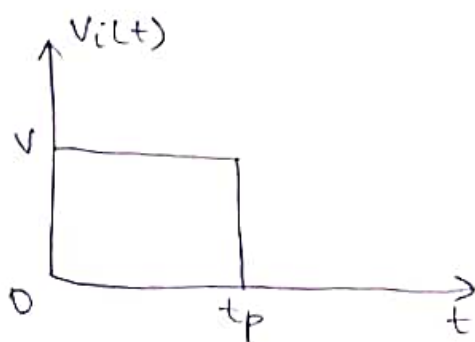

$$V_i(t) = V \quad 0 \leq t \leq t_p$$


$$= 0, \text{ otherwise}$$

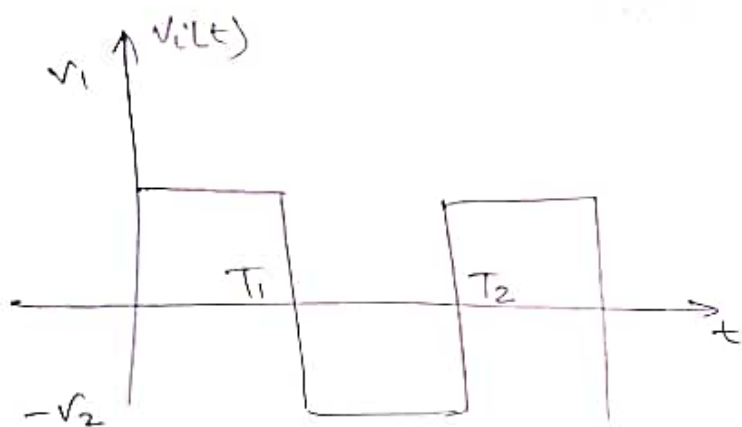(iii) Square wave v/p




$$v_i(t) = v_1 \quad t \leq T_1$$

$$= -v_2 \quad t < T_2 \text{ and } t > T_1$$




(iv) Ramp v/p

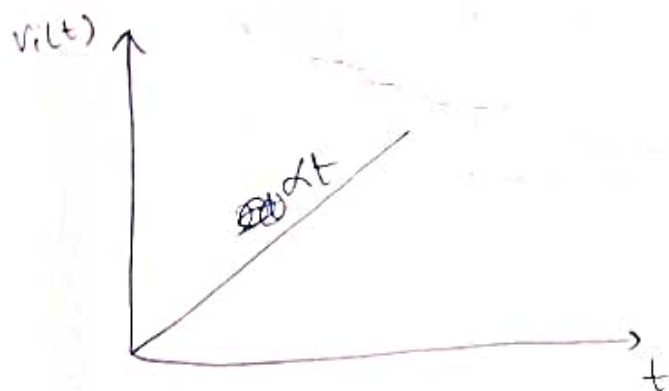

$$v_i(t) = \alpha t, \quad t \geq 0$$

$$= 0, \quad \text{otherwise}$$

1) Experimental I/P

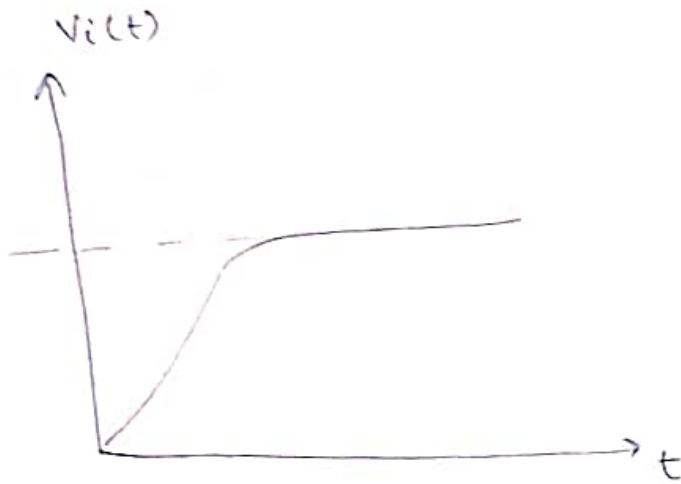


$$V_i(t) = V(1 - e^{-t/\tau}) ; t \geq 0$$


$$= 0 ; t < 0$$

$\tau \rightarrow$ time constant.

31/08/2022

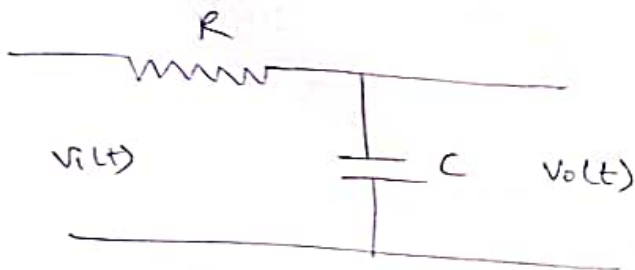

low pass filter

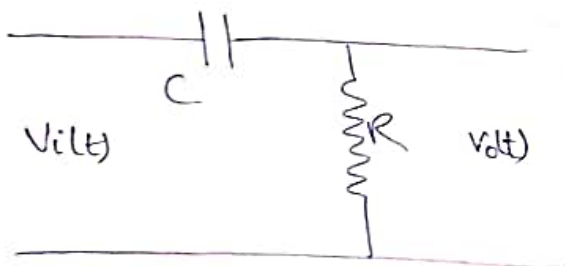


high pass filter



① Step Signal



High Pass Circuit

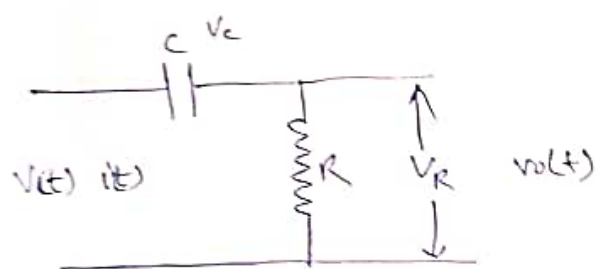

$$V_i(t) = V_C + V_R$$



Capacitance Reactance

~~$$X_C = \frac{1}{\omega C}$$~~

$$X_C = \frac{1}{2\pi f C}$$

$$f < f_1 \Rightarrow X_C \uparrow$$

$$X_C \propto \frac{1}{f}$$

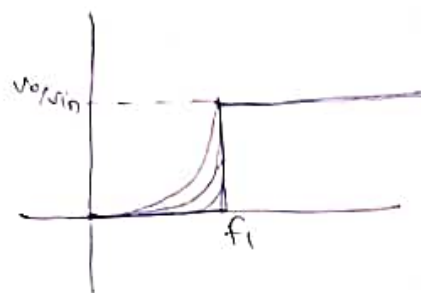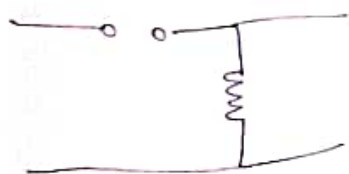


$f_1 \rightarrow$ cut off frequency

$$f_1 = \frac{1}{2\pi RC}$$


$f_1 >$ pass (gain increases)

$f_1 <$ rejected (gain 0)

$$f > f_1 \Rightarrow X_C \downarrow$$

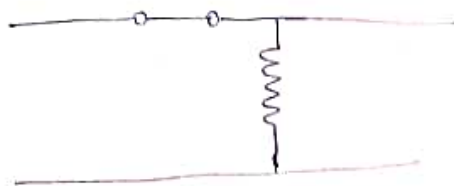

Laplace Transformation:

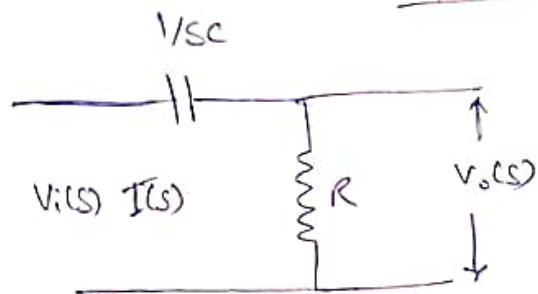

$$V_i(s) = \left(R + \frac{1}{sC} \right) I(s) \quad \text{--- (1)}$$

$$V_o(s) = I(s) R$$

$$A = \frac{V_o(s)}{V_i(s)} = \frac{I(s) R}{(R + 1/sC) I(s)}$$

Transfer function

$$= \frac{R}{R + 1/sC}$$

$$\boxed{\frac{V_o(s)}{V_i(s)} = \frac{1}{1 + 1/sRC}}$$

Putting, $s = j\omega$

$$\boxed{A = \frac{1}{1 + \frac{1}{RCj\omega}}}$$

$$\omega = 2\pi f$$

$$A = \frac{1}{1 + \frac{1}{RC 2\pi f j}}$$

$$= \frac{1}{1 + \frac{j}{RC 2\pi f j^2}} = \frac{1}{1 - \frac{j}{2\pi RC f}}$$

2.00



$$\left(\because f_c = \frac{1}{2\pi RC} \right)$$

$$\Rightarrow A = \frac{1}{1 - \frac{f_1}{f}}$$

$$|A| = \frac{1}{\sqrt{1 + \left(\frac{f_1}{f}\right)^2}}$$

$$f=0 \Rightarrow A=0$$



$$f = \infty \Rightarrow A = 1$$

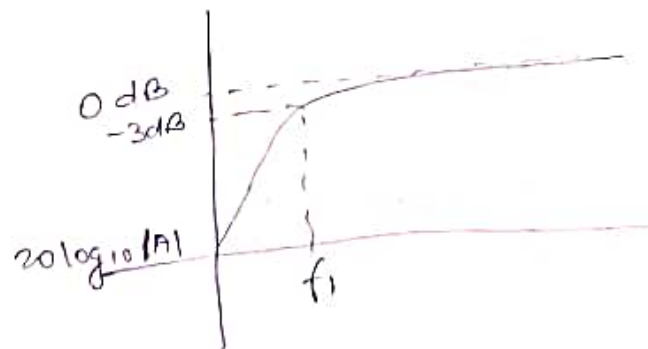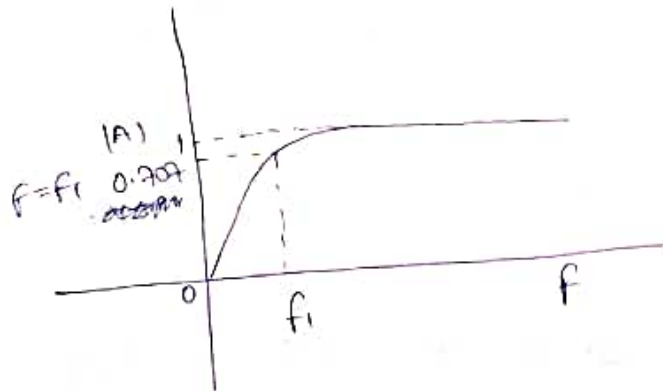

$$\frac{V_o(s)}{V_i(s)} = A \angle \theta$$

$$V_i = V_m \sin \omega t \quad V_o = V_m \sin(\omega t + \theta)$$

High Pass RC circuit with step I/P

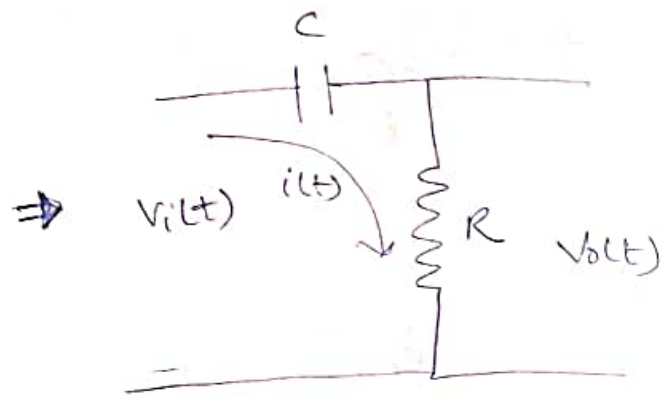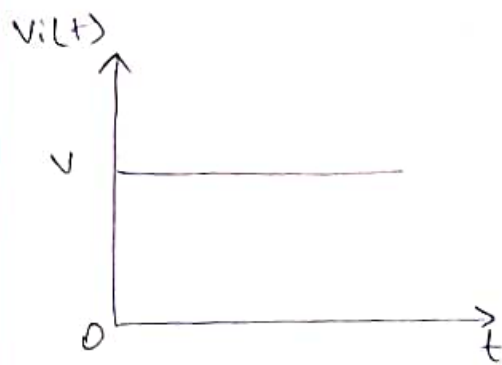

Analysis of O/P

→ Diff. eqn. method

→ Laplace method.

Case	Condition	V_i	V_c	V_R
1.	$t=0$	V	0	V
2.	$t>0$	V	expon. increases	exponentially decreases
3.	$t=\infty$ (steady state conditions)	V	V	0

Method 01: Expression for o/p voltage (Differential method).

Applying KVL:

$$V_i(t) = \frac{1}{C} \int i(t) dt + i(t)R \quad \text{--- (1)}$$

Diff. w.r.t dt

$$\frac{dV}{dt} = \frac{1}{C} i(t) + \frac{di(t)}{dt} R$$

$$\Rightarrow R \frac{di}{dt} + \frac{1}{C} i = 0$$

$$\Rightarrow \frac{di}{dt} + \frac{i}{RC} = 0$$

$$D = d/dt$$

$$\Rightarrow D i + \frac{i}{RC} = 0$$

$$= \left(D + \frac{1}{RC} \right) i = 0$$

$$D = -1/RC$$


$$i(t) = C_1 e^{-t/RC}$$

— (1)

C_1 can be found through initial conditions

$$t=0,$$

$$i(0) = \frac{V}{R}$$

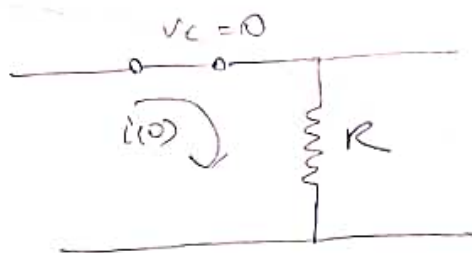

$$\Rightarrow \boxed{\frac{V}{R} = C_1}$$

$$\Rightarrow \boxed{i(t) = \frac{V}{R} e^{-t/RC}}$$

— (11)

$$V_o = i(t) R$$

$$= \frac{V}{R} e^{-t/RC} \times R$$

$$\Rightarrow \boxed{V_o = V e^{-t/RC}} \quad \leftarrow \textcircled{IV}$$


At $t=0$

$$V_o = V$$

~~At $t=0$~~

At $t = \infty$

$$V_o = 0$$

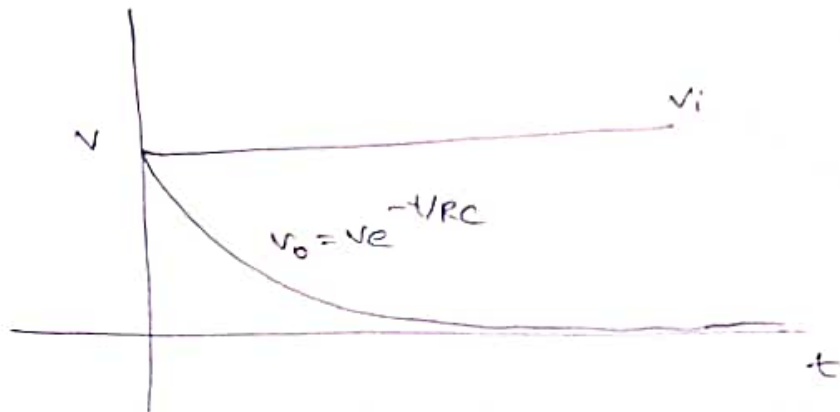

Method 2: Using Laplace Transformation Method:

for HPF,

$$\frac{V_o(s)}{V_i(s)} = \frac{1}{1 + 1/RCs} = \frac{s}{s + \frac{1}{RC}} \rightarrow \text{①}$$

$$V_i(t) = V$$

Laplace Transform of I/P signal (step)

$$V_i(s) = \frac{V}{s}$$



$$V_o(s) = \left(\frac{V}{s}\right) \left(\frac{s}{s + \frac{1}{RC}}\right)$$

$$\boxed{V_o(s) = \frac{V}{s + 1/RC}}$$

Now, taking Inverse Laplace Transform:

$$\boxed{V_o(t) = V e^{-t/RC}} \rightarrow \text{②}$$

High Pass RC Ckt with Pulse I/P

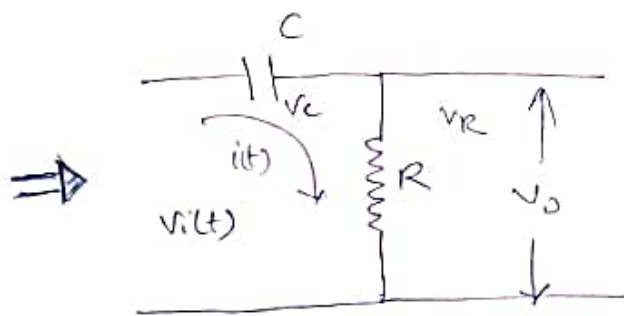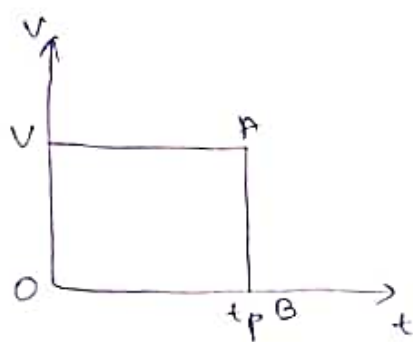

Diff. Method:

Case I $t=0$, $V_i = V$, $V_c = 0$, $V_R = V$

Case II $0 < t < t_p$, $V_i = V$, $V_c =$ starts charging exponentially

$V_R =$ starts decreasing exponentially with eqn.


$$V e^{-t/\tau} = V e^{-t/RC}$$

Case III $t = t_p$, $V_i = V$, $V_A = V e^{-t_p/RC}$
 (upper corner)

Case IV $t = t_p$, $V_i = V$, $V_B = V_A - V$
 (lower corner)

$$= V (e^{-t_p/RC} - 1)$$

Case V $t > t_p$, $V_i = 0$, $V_0(t) = V_B e^{-(t-t_p)/RC}$
 (steady state)

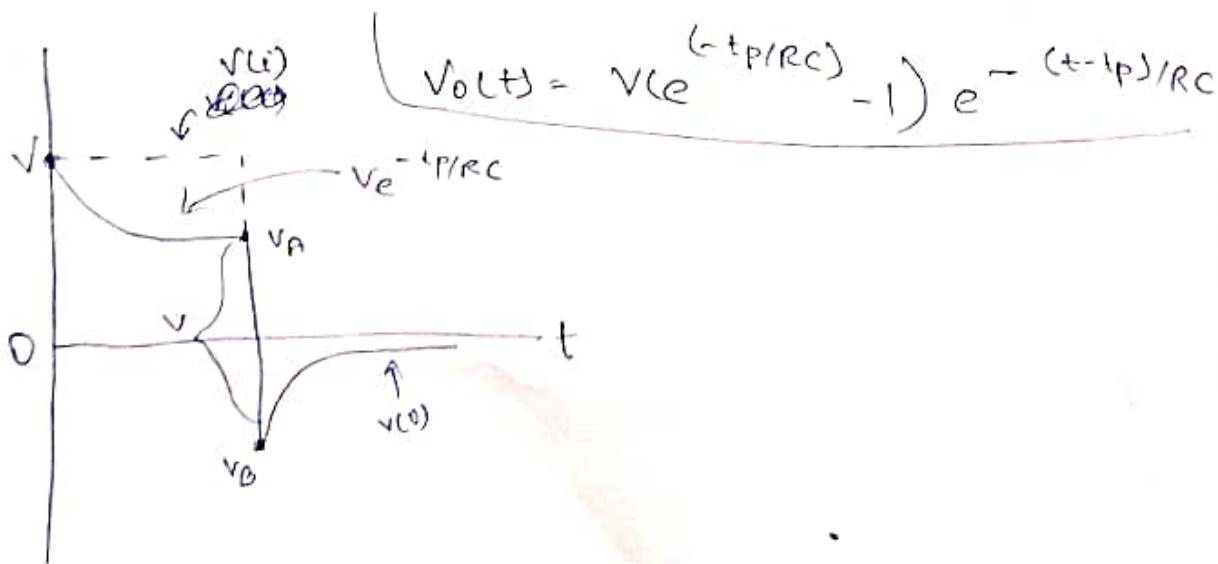

Method 2: Using Laplace Transform Method:

for HPF,

$$\frac{V_o(s)}{V_i(s)} = \frac{s}{s + \frac{1}{RC}} \quad \text{--- (i)}$$

$$\Rightarrow V_o(s) = \left(\frac{s}{s + \frac{1}{RC}} \right) V_i(s) \quad \text{--- (ii)}$$

$$V_i(s) = \int_0^{\infty} v_i(t) e^{-st} dt$$

$$= \int_0^{t_p} v e^{-st} dt$$

$$= v \int_0^{t_p} e^{-st} dt$$

$$= -\frac{v}{s} [e^{-st}]_0^{t_p}$$

$$= -\frac{v}{s} [e^{-st_p} - e^{0}]$$

$$= -\frac{v}{s} [e^{-st_p} - 1]$$

$$\Rightarrow V_i(s) = -\frac{v}{s} (e^{-st_p} - 1)$$

$$= \frac{v}{s} (1 - e^{-st_p}) \quad \text{--- (iii)}$$

from (i) and (iii)

$$V_o(s) = \left(\frac{s}{s + \frac{1}{RC}} \right) \frac{v}{s} (1 - e^{-st_p})$$

$$= \left(\frac{v}{s + \frac{1}{RC}} \right) (1 - e^{-st_p})$$

$$V_o(s) = v \left[\frac{1}{s + \frac{1}{RC}} - \frac{e^{-st_p}}{s + \frac{1}{RC}} \right] \quad \text{--- (iv)}$$


Taking reverse Laplace Transform:

$$V_o(t) = v \left[e^{-t/RC} - e^{-(t-t_p)/RC} \right]$$

$$V_o(t) = v (e^{-t_p/RC} - 1) e^{-(t-t_p)/RC} \quad \text{--- } \textcircled{v}$$


(i) $\tau = RC$

$RC \gg t_p$

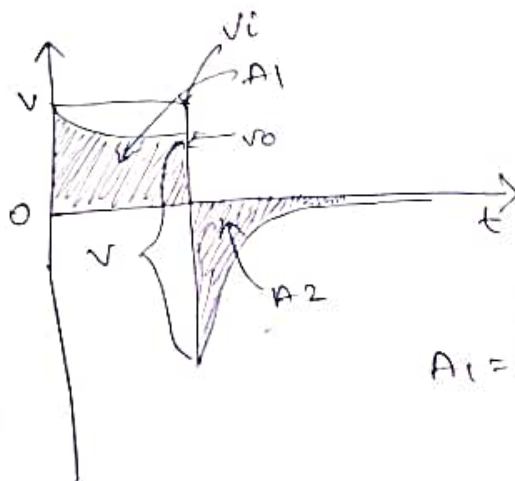

$$A_1 \approx A_2$$

(ii) $RC \ll t_p$

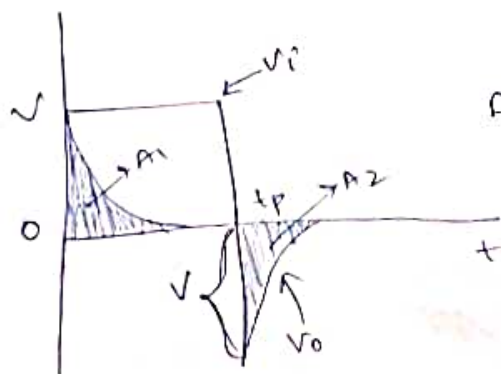

$$A_1 \gg A_2$$




for larger time constant $RC \gg t_p$,

there is only a slight tilt to the o/p pulse and under is very small.

However, the -ve portion decreases very slowly.

for small time constant $RC \ll t_p$, the o/p consists of a +ve spike or pip of amplitude V at the beginning of pulse and a -ve spike of same size at the end of pulse.

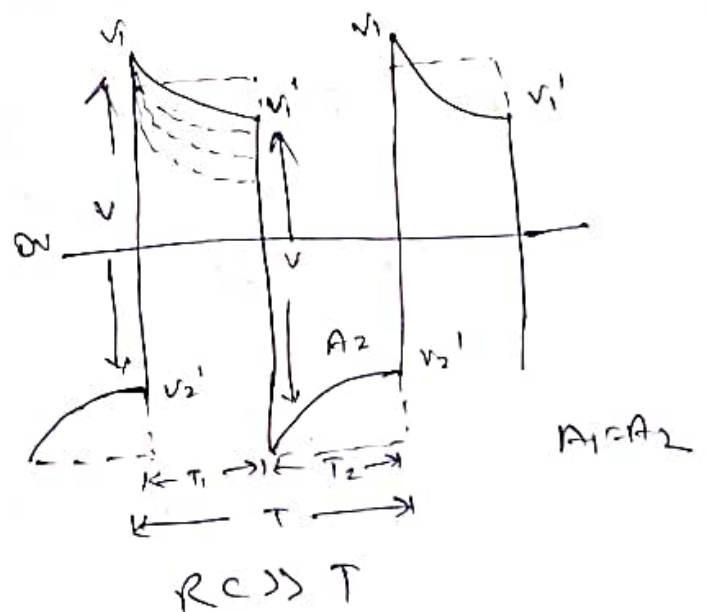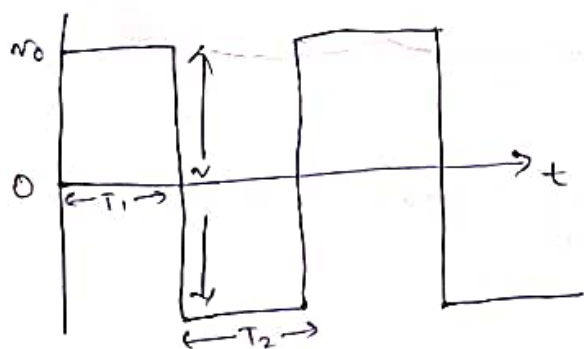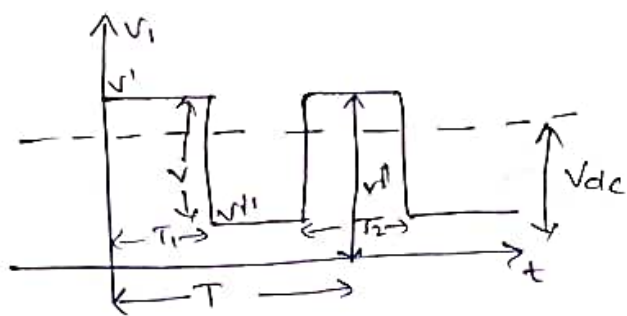High pass RC circuit with square wave IP:



$$V_1' = V_1 e^{-T_1/RC} \quad \text{--- (1)}$$

$$V_1' - V_2 = V \quad \text{--- (2)}$$

$$V_2' = V_2 e^{-T_2/RC} \quad \text{--- (3)}$$

$$V_1 - V_2' = V \quad \text{--- (4)}$$

$$T_1 = T_2 = \frac{T}{2}$$

$$V_1' = -V_2'$$

$$V_1 = -V_2$$

from (2)

$$V_1' + V_1 = V$$

$$V_1 e^{-T_1/RC} + V_1 = V$$

$$V_1 [1 + e^{-T_1/RC}] = V$$

$$V_1 = \frac{V}{1 + e^{-T_1/RC}} = \frac{V}{1 + e^{-T/2RC}} \quad \text{--- (5)}$$

$$e^x = 1 + x + \frac{x^2}{2!} + \frac{x^3}{3!} + \dots$$

AS $RC \gg T/2 = \frac{T}{2RC} \ll 1$

$$V_1 = \frac{V}{1 + 1 - \frac{T}{2RC}} \quad \text{(neglecting higher order)}$$

$$= \frac{V}{2 - \frac{T}{RC}} = \frac{V}{2(1 - \frac{T}{4RC})}$$

$$= \frac{V}{2} \left(1 - \frac{T}{4RC}\right)^{-1}$$

$$V_1 = \frac{V}{2} \left(1 + \frac{T}{4RC}\right) \quad \text{--- (6)}$$

$$V_1' = V_1 e^{-T/RC} = V_1 e^{-T/2RC}$$

$$V_1' = \frac{V e^{-T/2RC}}{1 + e^{-T/2RC}}$$

dividing num. and denominator by $e^{-T/2RC}$

$$= \frac{V}{1 + e^{T/2RC}}$$

$$e^x = 1 + x + \frac{x^2}{2!} + \frac{x^3}{3!} + \dots$$

$$= \frac{V}{1 + 1 + \frac{T}{2RC}} \quad (\text{Neglecting higher order})$$

$$V_1' = \frac{V}{2 \left(1 + \frac{T}{4RC}\right)}$$

$$V_1' = \frac{V}{2} \left(1 + \frac{T}{4RC}\right)^{-1} \quad \text{--- (7)}$$

Now % tilt is given by

$$\% \text{ tilt} = \frac{V_1 - V_1'}{V/2} \times 100\%$$

$$= \frac{\frac{T}{2} \left(1 + \frac{T}{4RC}\right) - \frac{T}{2} \left(1 - \frac{T}{4RC}\right)}{V/2} \times 100\%$$

$$\% \text{ tilt} = \frac{T}{2RC} \times 100\%$$

--- (10)


$$= \frac{1}{2fRC} \times 100\%$$

$$(T = 1/f)$$


$$= \frac{T}{2fRC} \times 100\%$$

$$\% \text{ tilt} = \frac{\pi f_2}{f} \times 100\%$$

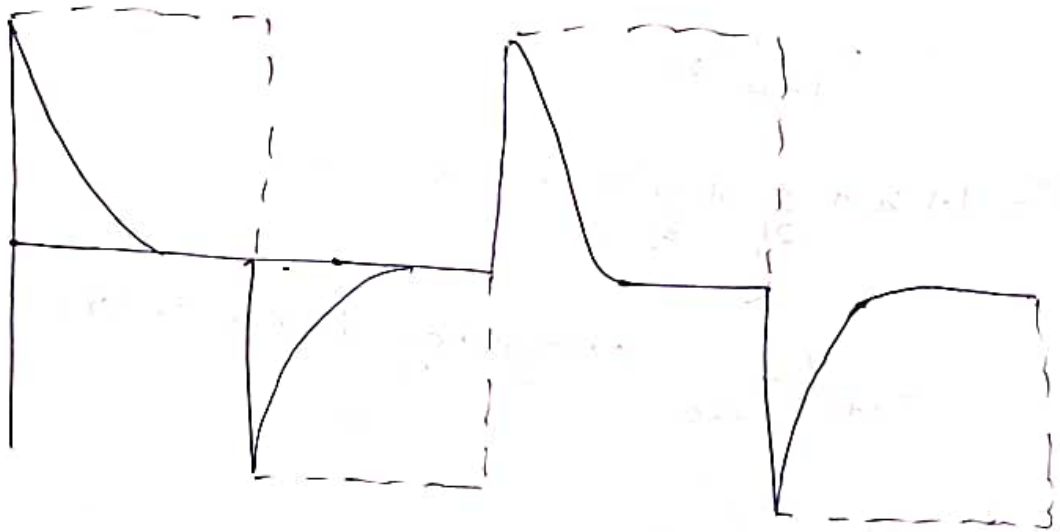$f_1 \rightarrow$ cut off frequency.
(-3dB)



Low Pass RC Circuit

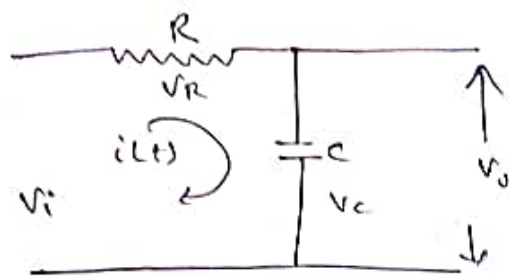

$$f_1 = \frac{1}{2\pi RC}$$

Capacitive Reactance

$$X_C = \frac{1}{\omega C}$$

$$= \frac{1}{2\pi f C}$$




$f \uparrow \Rightarrow X_C \downarrow$ short ckt

$f \downarrow \Rightarrow X_C \uparrow$ Open ckt


(i) $f_1 < f$

(ii) $f_1 > f$

(iii) $f_1 = f$

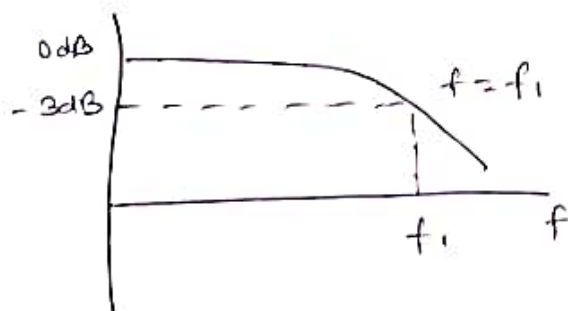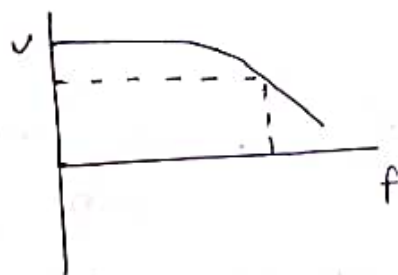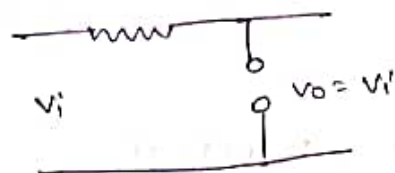

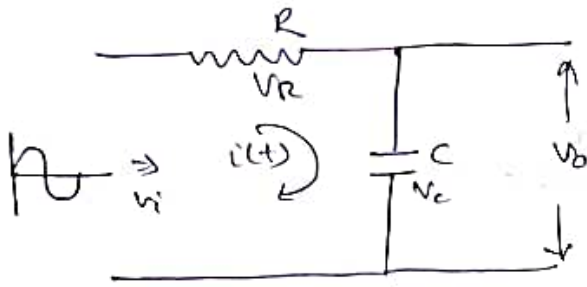Low pass RC circuit with sinusoidal input:



$$v_i(t) = V_m \sin \omega t$$

$$V_i(s) = \left(R + \frac{1}{sC}\right) I(s)$$

$$I(s) = \frac{V_i(s)}{R + \frac{1}{sC}}$$

$$= \frac{V_i(s)}{R \left(1 + \frac{1}{sRC}\right)} \quad \text{--- (i)}$$

$$V_o(s) = \frac{1}{sC} I(s) \quad \text{--- (ii)}$$

Transfer function:

$$\frac{V_o(s)}{V_i(s)} = \frac{1}{1 + sRC} = \frac{1}{1 + j2\pi fRC} \quad \text{--- (iii)}$$

$$\text{Polar form } \frac{V_o(s)}{V_i(s)} = A \angle \theta \quad \text{--- (iv)}$$

A = gain

A is the mag. of steady state gain.

$\angle \theta$ = o/p leading i/p

$$A = \frac{1}{\sqrt{1 + (f/f_2)^2}}$$

$$f_2 = \frac{1}{2\pi RC}$$

$$\theta = -\tan^{-1} \left(\frac{f}{f_2} \right) \quad \text{--- (v)}$$

Applying (v) and (vi) O/P signal is given by,


$$V_o(t) = A V_m \sin(\omega t + \theta) \quad \leftarrow \text{(vii)}$$

As the phase angle θ is negative

Hence the O/P voltage $v_o(t)$ lags behind I/P signal $v_i(t)$ by a phase angle θ .

The gain A falls to 0.707 of its low frequency value at freq. f_2 . Hence f_2 is called upper 3dB freq.

Low Pass RC circuit with step I/P:

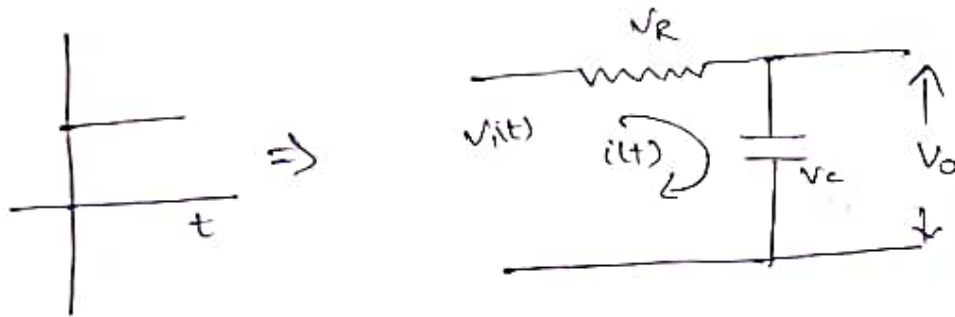

$$V_i(t) = V_R + V_C$$

$$V_i(t) = i(t)R + \frac{1}{C} \int i(t) dt \quad \text{--- (i)}$$

$$V = i(t)R + \frac{1}{C} \int i(t) dt \quad \text{--- (ii)}$$

diff. eqn (ii) w.r.t t , we have

$$R \frac{di}{dt} + \frac{1}{C} i = 0 \quad \text{--- (iv)}$$

$$\boxed{\frac{di}{dt} + \frac{1}{RC} i = 0} \quad \text{--- (v)}$$

first order diff. eqn.

$$\frac{d}{dt} = D$$

$$\left(D + \frac{1}{RC}\right)i = 0 \quad \text{--- (vi)}$$


$$D = -\frac{1}{RC} \quad (\text{possible root}) \quad \text{--- (vii)}$$

$$i(t) = C_1 e^{-t/RC} \quad \text{--- (viii)}$$

$$\text{At } t=0$$

$$i(0) = \frac{V}{R}$$

$$\frac{V}{R} = C_1 e^0$$

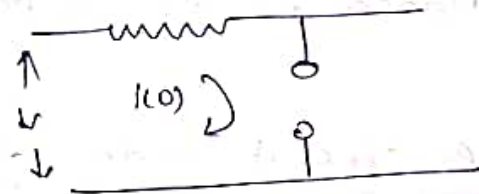

$$C_1 = \frac{V}{R} \quad \text{--- (ix)}$$

$$i(t) = \frac{V}{R} e^{-t/RC} \quad \text{--- (x)}$$

$$V_R = i(t)R$$

$$= V e^{-t/RC}$$


As we know,

$$V(t) = V_R + V_C$$


$$V = V e^{-t/RC} + V_C$$

$$V_C = V_0 = V - V e^{-t/RC}$$

$$V_C = V_0 = V(1 - e^{-t/RC})$$

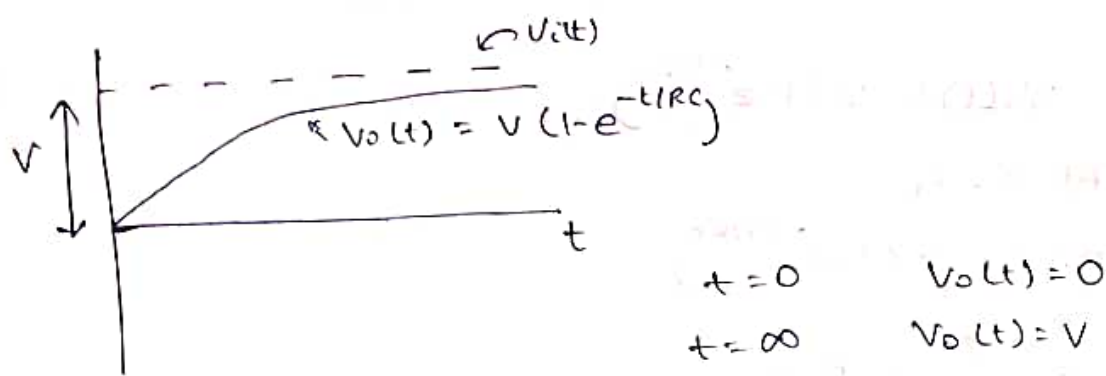


For different time constant (RC)

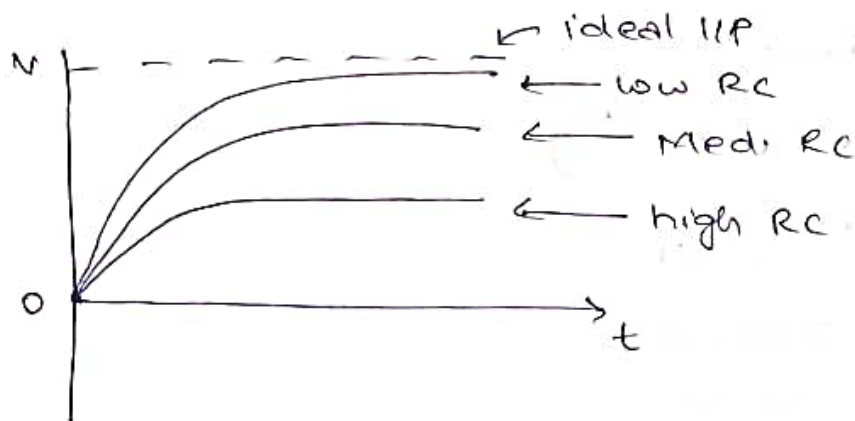

Rise Time:

$$V_c \rightarrow (10\% - 90\%) V_0$$

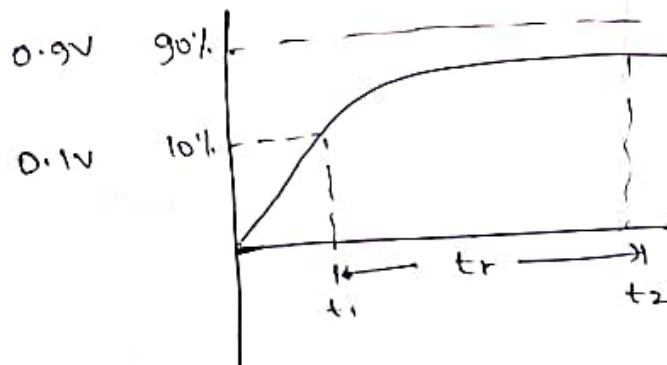Time taken by the capacitor voltage to increase from 10% to 90% of its final volt V_0 is called rise time.



$$t_r = t_2 - t_1$$

$$V_0(t) = V(1 - e^{-t/RC})$$

At $t = t_1$

$$0.1V = V(1 - e^{-t_1/RC})$$

$$e^{-t_1/RC} = 0.9$$

$$t_1 = 0.105 RC$$

$t = t_2$, we have

$$0.9V = V(1 - e^{-t_2/RC})$$

$$e^{-t_2/RC} = 0.1$$

$$t_2 = 2.303 RC$$

$$t_r = t_2 - t_1$$

$$t_r = 2.2 RC$$

let f_2 be upper 3dB freq.

$$f_2 = \frac{1}{2\pi RC}$$

$$t_r = 2.2 \times \frac{1}{2\pi f_2}$$

$$t_r = \frac{0.35}{f_2}$$