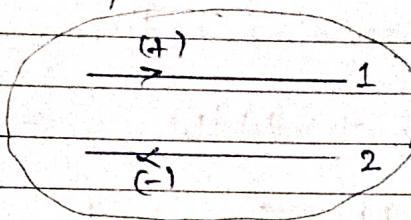


Module - 3

Two-Port Network


Port - A pair of available terminals



One-Port Network

* One pair of terminals are available.

Eg : TV, AC, etc.

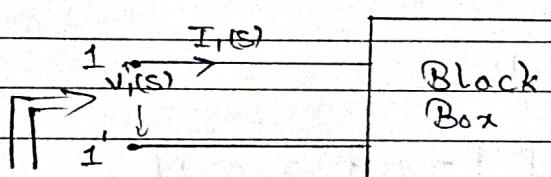

Schematic diagram
of One-Port NW.

* Our prime focus is to find voltage & current.
So, rest of the things are kept ~~at~~ together
inside a terming it a Black box.

$$Z_{11} = \frac{V_1(s)}{I_1(s)} \quad \Omega \text{ (hm)}$$

Driving point Impedance function


$$Y_{11} = \frac{I_1(S)}{V_1(S)}$$

Driving Point Admittance Function

Two-Port N/W

* 2 pairs of available terminals.

Eg: Transformers

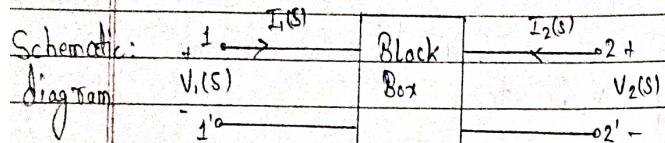

Parametric Equations

$$[V_1(S), V_2(S)] = f [I_1(S), I_2(S)]$$

$$1 \quad V_1(S) = Z_{11} I_1(S) + Z_{12} I_2(S)$$

\Rightarrow 2-Parameter

$$2 \quad V_2(S) = Z_{21} I_1(S) + Z_{22} I_2(S)$$

* Putting $I_2(S) = 0$

from Eqn (1):


$$Z_{11} = \frac{V_1(S)}{I_1(S)} \quad | \quad I_2(S) = 0$$

Driving Point Impedance / Open Circuit Impedance Parameters


from eqn (2):

$$Z_{21} = \frac{V_2(S)}{I_1(S)} \quad | \quad I_2(S) = 0$$

Forward Transfer Impedance

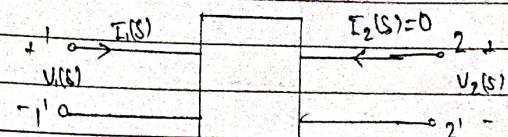

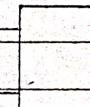* Putting $I_1(S) = 0$ i.e. Open Circuiting 11'



from eqn (1):

$$Z_{12} = \frac{V_1(S)}{I_2(S)} \quad | \quad I_1(S) = 0$$

Reverse Transfer Impedance

from eqn (2):

$$Z_{22} = \frac{V_2(S)}{I_2(S)} \quad | \quad I_1(S) = 0$$

Output Impedance


* $Z = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix}$

(i) $Z_{12} = Z_{21} \Rightarrow$ Reciprocity requirement

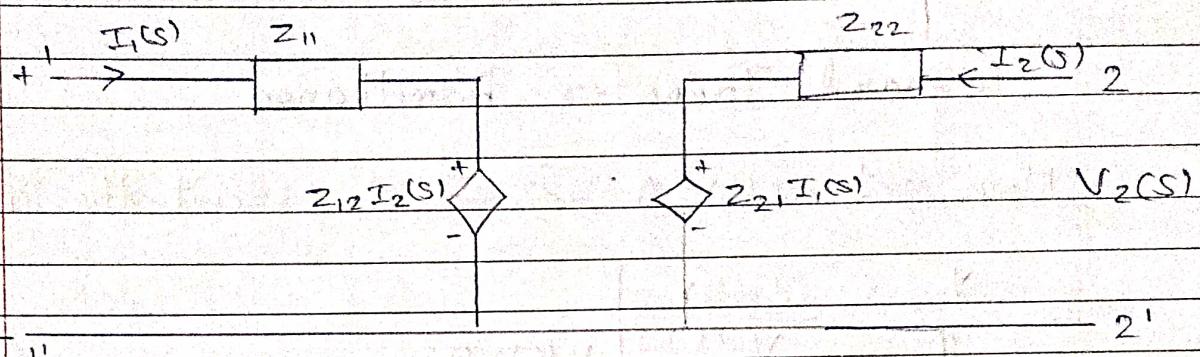(ii) $Z_{11} = Z_{22} \Rightarrow$ Symmetry requirement

DATE 31/8/23
PAGE NO.

Circuit Diagram corresponding to Eqn 1 & 2 :-




Two generator equivalent circuit diagram

γ -Parameters | Short Circuit Admittance Parameters

$$(I_1, I_2) \neq f(V_1, V_2)$$

$$I_1(S) = Y_{11} V_1(S) + Y_{12} V_2(S) \quad (1)$$
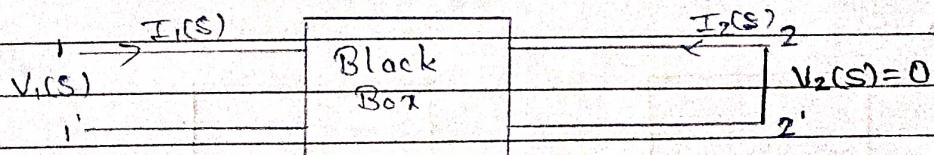
$$I_2(S) = Y_{21} V_1(S) + Y_{22} V_2(S) \quad (2)$$



Put $V_2(S) = 0$ i.e. Short circuit the port 22'.

$$\gamma_{11} = \frac{I_1(S)}{V_1(S)} \quad |_{V_2(S)=0}$$

Driving Point Admittance func.

$$Y_{21} = \frac{I_2(s)}{V_1(s)} \quad | \quad V_1(s) = 0$$

Forward Transfer Admittance

Now, put $V_1(s) = 0$ i.e. Short Circuit the port 1'


$$Y_{12} = \frac{I_1(s)}{V_2(s)} \quad | \quad V_2(s) = 0$$

Reverse Transfer Admittance

$$Y_{22} = \frac{I_2(s)}{V_2(s)} \quad | \quad V_1(s) = 0$$

Output Admittance
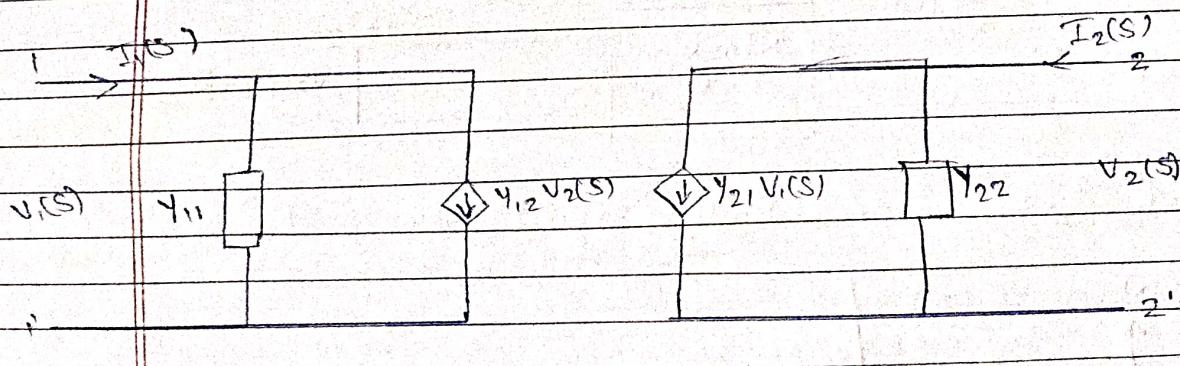
$$[Y] = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix}$$



(i) $\gamma_{12} = \gamma_{21} \Rightarrow$ Condition for Reciprocity


(ii) $\gamma_{11} = \gamma_{22} \Rightarrow$ Condition for Symmetry

T-Parameters / Chain / ABCD Parameters

$$(V_1, I_1) = f(V_2, -I_2)$$

$$V_1 = A V_2 + B (-I_2)$$

$$I_1 = C V_2 + D (-I_2)$$

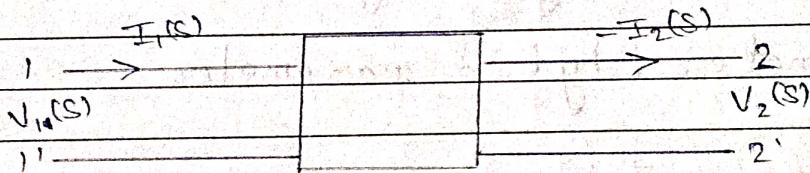

Put, $-I_2 = 0$ i.e. Open Circuit port 22'

$$A = \frac{V_1}{V_2} \quad \text{unitless}$$

$$C = \frac{I_1}{V_2} \quad (v)$$

Put, $V_2 = 0$ i.e. Short circuit port 22'

$$B = \frac{V_1}{-I_2} \quad | \quad V_2 = 0$$

Reverse Transfer Impedance

$$D = \frac{I_1}{-I_2} \quad | \quad V_2 = 0$$

(ii) Condition for Reciprocity : $AD - BC = 1$


(iii) Condition for Symmetry : $A = B$

h -Parameters / hybrid parameters

$$(V_1, I_2) = f(I_1, V_2)$$

$$V_1 = h_{11}I_1 + h_{12}V_2$$

$$I_2 = h_{21}I_1 + h_{22}V_2$$

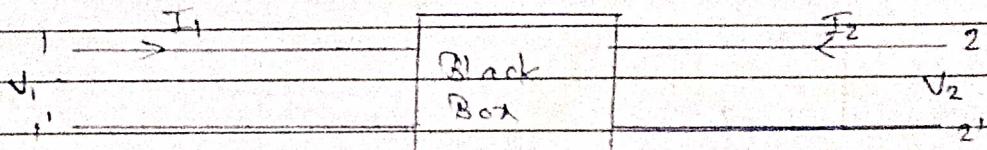

Put, $V_2 = 0$ i.e. Short Circuit port 22'

$$h_{11} = \frac{V_1}{I_1} \quad | \quad V_2 = 0 \quad (\Omega)$$

Driving Point Impedance

$$h_{21} = \frac{I_2}{V_1} \quad | \quad V_2 = 0 \quad (\text{unitless})$$

Current gain

Put, $I_1 = 0$ i.e. Open Circuit port 11'


$$h_{12} = \frac{V_1}{V_2} \quad | \quad I_1 = 0 \quad (\text{unitless})$$

Reverse Voltage Gain


$$h_{22} = \frac{I_2}{V_2} \quad | \quad I_1 = 0 \quad (\Omega)$$

Output Admittance

h_{11}


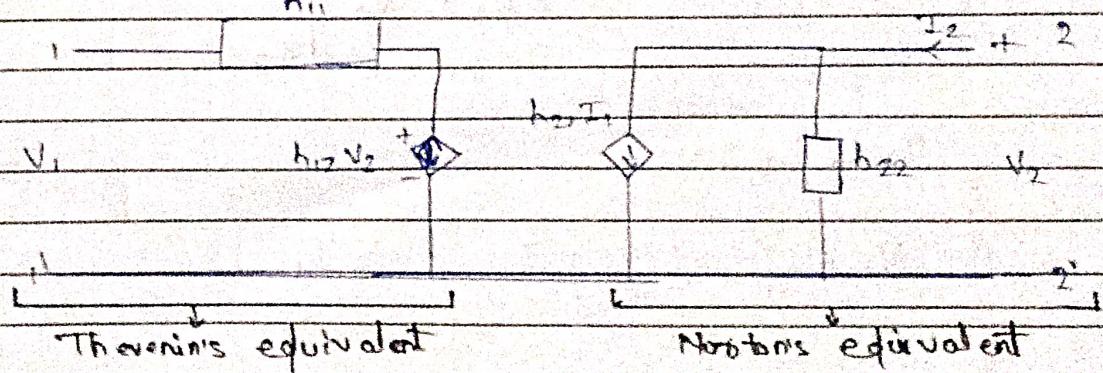


Inverso T & 6₋ Assignment
parameters

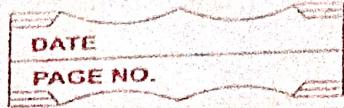

(i) $h_{12} = -h_{21} \Rightarrow$ Reciprocity

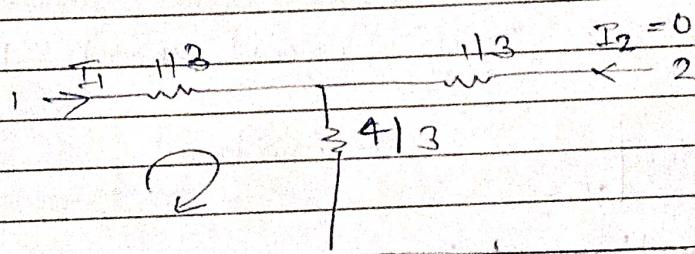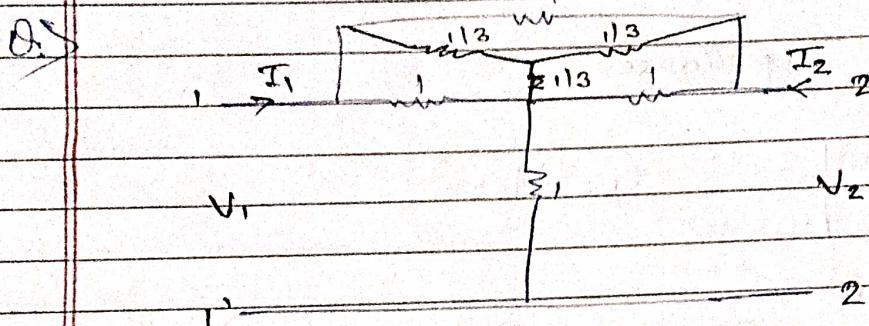(ii) $h_{11}h_{12} - h_{21}h_{22} = 1 \Rightarrow$ Symmetry



Z-Parameters: $Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0}$

$Z_{21} = \frac{V_2}{I_2} \Big|_{I_1=0}$

Put, $I_2 = 0$;

$V_1 = \left(1 + \frac{4}{3}\right) I_1 = \frac{7}{3} I_1$


$$Z_{11} = \frac{V_1}{I_1} = \frac{5\Omega}{\frac{3}{3}} = \frac{5}{3} \Omega$$

$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}$$

$$V_2 = \frac{4}{3} I_1$$

$$Z_{21} = \frac{V_2}{I_1} = \frac{4}{3} \Omega$$

Now, Put $I_1 = 0$

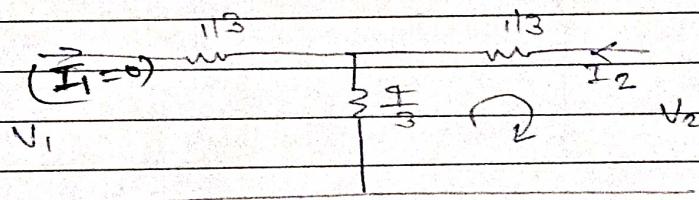

$$V_2 = \left(\frac{4}{3} + \frac{1}{3} \right) I_2$$

$$\therefore Z_{22} = \frac{V_2}{I_2} = \frac{5}{3} \Omega$$

$$V_2 = \frac{4}{3} I_2$$


$$Z_{12} = \frac{V_1}{I_2} = \frac{4}{3} \Omega$$



$$[2] = \begin{bmatrix} 5 & \frac{4}{3} \\ 3 & 3 \end{bmatrix}$$

Below the matrix, there is handwritten text: "4/3" on the left and "5/3" on the right, aligned with the respective columns of the matrix.

Method II:

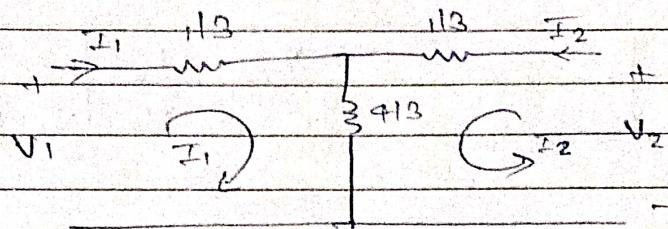

$$V_1 = \frac{1}{3} I_1 + \frac{4}{3} (I_1 + I_2)$$

$$= \frac{5}{3} I_1 + \frac{4}{3} I_2 = (1)$$

$$V_2 = \frac{1}{3} I_2 + \frac{4}{3} (I_1 + I_2)$$

$$= \frac{4}{3} I_1 + \frac{5}{3} I_2 = (2)$$

On Comparing :

$$Z_{11} = \frac{5}{3}, \quad Z_{12} = \frac{4}{3}$$


$$Z_{21} = \frac{4}{3}, \quad Z_{22} = \frac{5}{3}$$

$$[Y] = [Z]^{-1}$$

For Y-parameters

$$Y_{11} = \frac{I_1}{V_1} \quad V_2 = 0$$
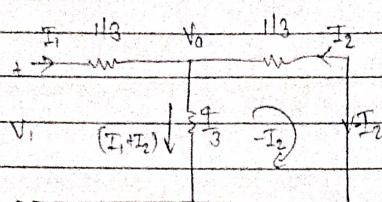
$$Y_{21} = \frac{I_2}{V_1} \quad V_1 = 0$$




$$I_1 = \frac{V_0 - I_2}{4/3}$$

$$= \frac{3V_0 - I_2}{4}$$

$$V_0 = \frac{1}{3}I_1 + \frac{(I_1 + I_2)}{4}$$

$$V_0 = V_1 - \frac{1}{3}I_1$$

ii) Find Y-Parameters.

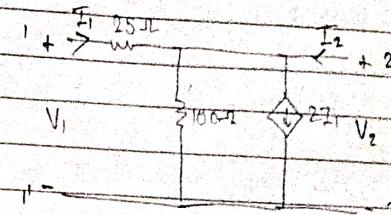


Soln: Put $V_2 = 0$:

$$I_1 = Y_{11}V_1 + Y_{12}V_2$$


$$I_2 = Y_{21}V_1 + Y_{22}V_2$$

$$Y_{11} = \frac{I_1}{V_1} \quad V_2 = 0$$
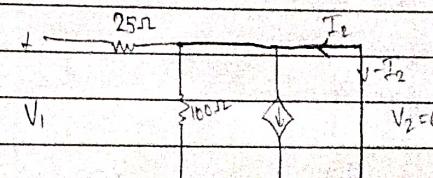
$$Y_{21} = \frac{I_2}{V_1} \quad V_2 = 0$$



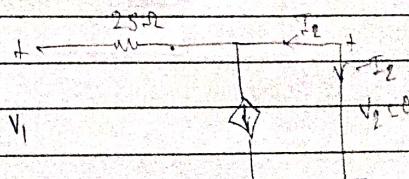100 ohms is removed because of some potential



$$-V_1 + 25I_1 + 0 = 0$$

$$\Rightarrow V_1 = 25I_1 \quad (i)$$

~~$$V_1 = 25I_2 \quad Y_{11} = I_1 = \frac{1}{25} V_1$$~~

KCL at node 1:

$$I_1 = 2I_2 + I_3$$

$$\Rightarrow -I_1 = -I_2 \Rightarrow I_1 = I_2 \quad (ii)$$


From (i) & (ii):

$$V_1 = 25I_1$$

$$\Rightarrow V_1 = 25I_2$$

$$Y_{21} = \frac{I_2}{V_1} = \frac{1}{25}$$

Now put $V_1 = 0$:

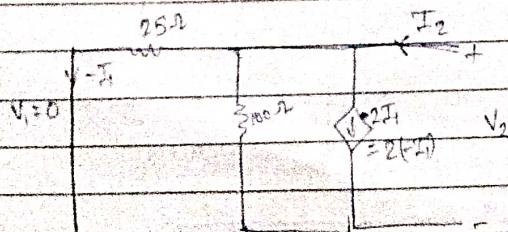

$$I_2 = -27 + \frac{V_2}{100} + \frac{V_2}{25} \quad (iii)$$


$$-I_1 = \frac{V_2}{25} \quad (iv)$$

$$Y_{12} = \frac{1}{25} \left(\frac{I_1}{V_2} \right)$$

$$I_2 = \frac{2V_2}{25} + \frac{V_2}{25} + \frac{V_2}{100}$$

$$\frac{I_2}{V_2} = \frac{13}{100} = Y_{22}$$

2) BE[Y]

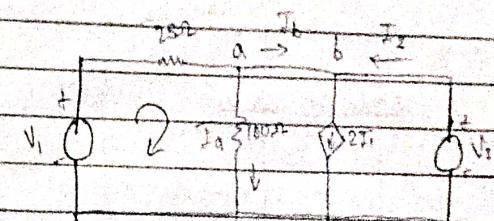

KCL at node b:

$$I_3 + I_2 = 2I_1$$

$$\Rightarrow I_3 = 2I_1 - I_2 \quad (v)$$

KCL at node a:

$$I_1 = I_a + I_b$$

$$\begin{aligned} \Rightarrow I_a &= I_1 - I_b \\ &= I_1 - (I_1 - I_2) \\ \Rightarrow I_a &= -I_1 + I_2 \quad (1) \end{aligned}$$


KVL in loop 1:

$$\begin{aligned} V_1 &= 25I_1 + 100(I_1 + I_2) \\ &= -75I_1 + 100I_2 \quad (1) \end{aligned}$$

loop 2:


$$V_2 = 100(I_1 + I_2) \quad (2)$$

8.5

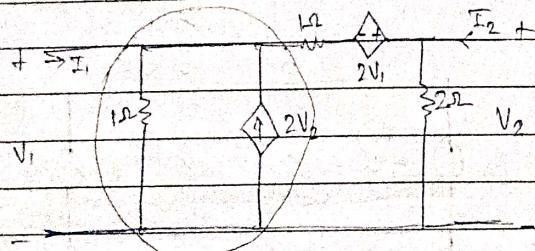

Soln:

Method I:

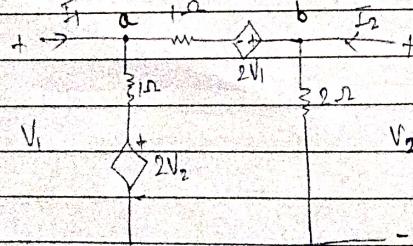

KCL at node a:

$$I_1 = \frac{V_1 - 2V_2}{1} + \frac{V_1 + 2V_1 - V_2}{1} \quad \cancel{\text{I}}$$

$$\begin{aligned} \Rightarrow I_1 &= V_1 - 2V_2 + V_1 + 2V_1 - V_2 \\ \Rightarrow I_1 &= 4V_1 - 3V_2 \quad (1) \end{aligned}$$

KCL at node b:


$$I_2 = \frac{V_2 + V_2 - 2V_1 - V_1}{2} \quad \cancel{\text{I}}$$


$$= -3V_1 + 1.5V_2 \quad (2)$$

$$\begin{bmatrix} 4 & -3 \\ -3 & 1.5 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

Method II:

$$V_2 = 0$$

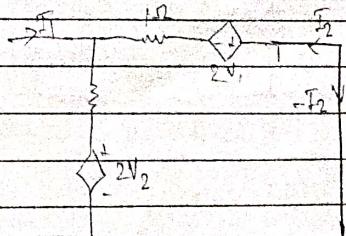

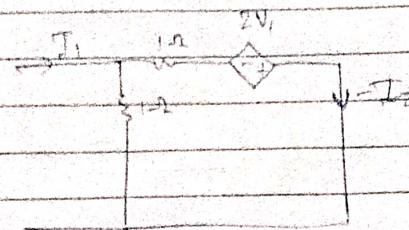

$$-I_2 = V_1 + 2V_1$$


$$I_1 = \frac{V_1 + V_1 + 2V_1}{1}$$

$$\Rightarrow \frac{I_2}{V_1} = -3V_1 = Y_{21} \quad Y_{11} = \frac{I_1}{V_1} = 4V_1$$


$$-I_2 = V_1 + 2V_1$$

$$\Rightarrow Y_{21} = \frac{I_2}{V_1} = -3V_1$$

Now, $V_1 = 0$

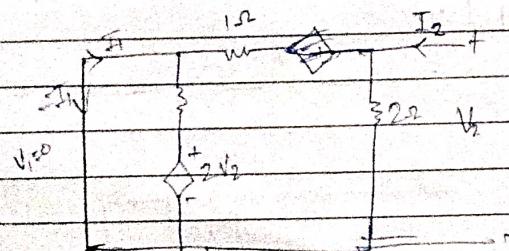

[With Conditions]

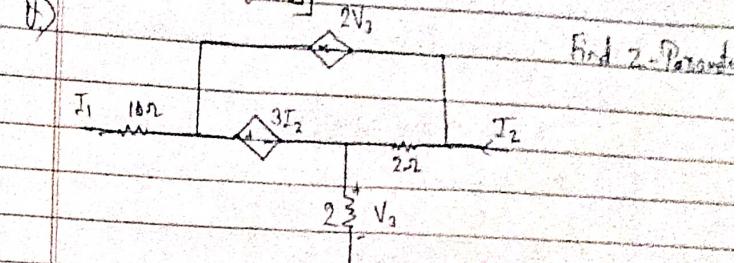

Sol:


$$V_1 = Z_{11}I_1 + Z_{12}I_2$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

$$Z_{11} = \frac{V_1}{I_1} \quad |_{I_2=0}$$

$$Z_{21} = \frac{V_2}{I_1} \quad |_{I_2=0}$$

Put, $I_2 = 0$

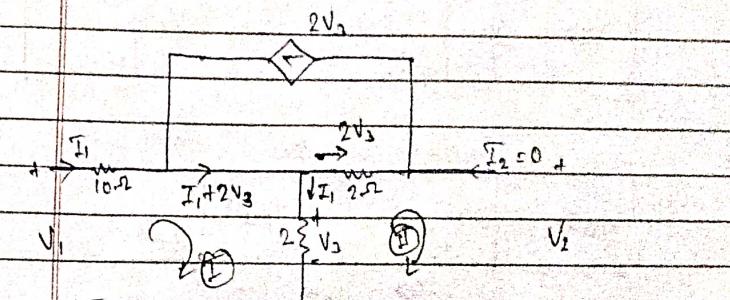

KVL in loop (1):

$$-V_1 + 10I_1 + 9I_1 = 0$$

$$\Rightarrow V_1 = 12I_1$$

$$\therefore Z_{11} = \frac{V_1}{I_1} = 12\Omega$$

KVL in loop II:

$$-2I_1 + 2(2V_3) + V_2 = 0$$

$$\Rightarrow V_2 = 2I_1 - 4V_3$$

And also, $V_2 = 2I_1$


$$\text{So, } V_2 = 2I_1 - 4 \times 2I_1$$

$$\Rightarrow V_2 = -6I_1$$

$$\therefore Z_{21} = \frac{V_2}{I_1} = -6\Omega$$

For Second half:

$$Z_{12} = \frac{V_1}{I_2} \quad | \quad I_1 = 0 \quad , \quad Z_{22} = \frac{V_2}{I_2} \quad | \quad I_1 = 0$$

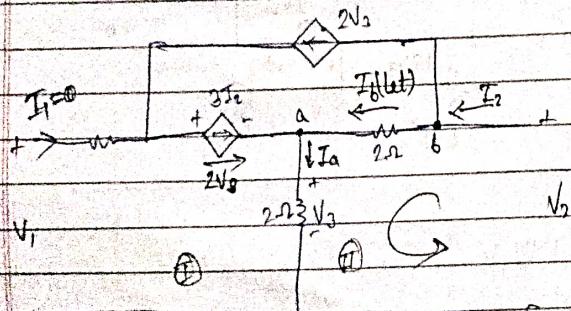

$$\text{KCL at } b: I_2 = \frac{V_2}{2\Omega} + 2V_3$$

$$\Rightarrow I_2 = (I_2 - 2V_3)$$

$$\text{Now, KCL at } a: 2V_3 + I_2 = I_a$$

$$\Rightarrow 2V_3 + (I_2 - 2V_3) = I_a$$

$$\Rightarrow I_a = I_2$$

KVL in Ind loop:

$$-V_2 + 2I_2 + 2 \times I_a = 0$$

$$\Rightarrow V_2 = 2(I_2 - 2V_3) + 2(I_2)$$

$$\Rightarrow V_2 = 4I_2 - 4V_3$$

But, $V_2 = 2I_a = 2I_2$

$$\text{So, } V_2 = 4I_2 - 4 \cdot 2I_2 = -4I_2$$

$$\therefore Z_{22} = \frac{V_2}{I_2} = -4\Omega$$


Now, KVL in 1st loop:

$$-V_1 + 3I_2 + 2I_2 = 0 \quad (\because I_a = I_2)$$

$$\Rightarrow \frac{Z_{12}}{I_2} = \frac{V_1}{I_2} = 5\Omega$$

$$\therefore Z = \begin{bmatrix} 12 & 5 \\ -6 & -4 \end{bmatrix} \quad \& \quad Y = [2]^{-1}$$

Without Conditions

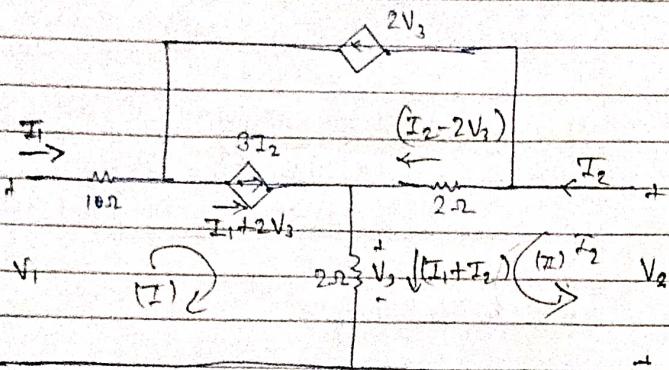

KVL in loop (I) :-

$$-V_1 + 10I_1 + 3I_2 + 2(I_1 + I_2) = 0$$

$$\Rightarrow V_1 = 12I_1 + 5I_2$$

KVL in loop (II) :-

$$-V_2 + 2(I_2 - 2V_3) + 2(I_1 + I_2) = 0$$

$$\Rightarrow I_2 = 2(I_1 + I_2)$$

$$\text{But, } V_3 = 2(I_1 + I_2)$$

$$V_2 = 2I_2 - 8(I_1 + I_2) + 2(I_1 + I_2)$$

$$= -6I_1 - 4I_2$$

$$\therefore [Z] = \begin{vmatrix} 12 & 5 \\ -6 & -4 \end{vmatrix}$$

$$8) \quad 1 + \frac{I}{R} \rightarrow \frac{I}{R} \leftarrow I_2 \downarrow 2$$

$$V_1 \quad V_2$$

$$i' - \quad - 2i$$

Sol? :

Since Open Circuit, Single loop \Rightarrow So, same current flows through 1 loop.

$$\text{When, } I_1 = 0 \Rightarrow I_2 = 0$$

$$I_2 = 0 \Rightarrow I_1 = 0$$

\therefore 7 parameters does not exist / not defined

$$\text{Also, } I_1 = -I_2$$

$$V_1 = I_1 R$$

$$I = \frac{I_1}{R} = \frac{V_1}{R}$$


$$I_1 = Y_{11}V_1 + Y_{12}V_2$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2$$

$$Y_{11} = \frac{I_1}{V_1} \quad V_1, V_2 \neq 0$$

$$Y_{21} = \frac{I_2}{V_1} \quad V_1, V_2 \neq 0$$

$$Y_{21} = -\frac{1}{R}$$

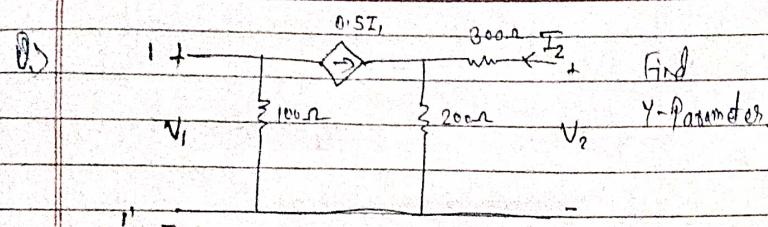


Soln: $I_1 = Y_{11}V_1 + Y_{12}V_2$

$I_2 = Y_{21}V_1 + Y_{22}V_2$

$$\left. \begin{aligned} Y_{11} &= \frac{I_1}{V_1} & V_2 &= 0 \\ & V_1 & V_2 &= 0 \end{aligned} \right\}, \quad \left. \begin{aligned} Y_{21} &= \frac{I_2}{V_2} & V_1 &= 0 \\ & V_2 & V_1 &= 0 \end{aligned} \right\}$$

Put, $V_2 = 0$:

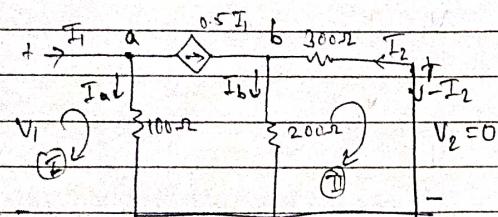

KCL at node a:

$$I_1 = I_a + 0.5I_1$$

~~$\Rightarrow I_a = 0.5I_1$~~

KCL at node b: $0.5I_1 = I_b - I_2$
 $\Rightarrow I_b = 0.5I_1 + I_2$

KVL in loop (I):

$$-V_1 + 100I_a = 0$$

$$\Rightarrow V_1 = 100 \times 0.5I_1 = 50I_1$$

$$\therefore \underline{\underline{Y_{11}} = \frac{I_1}{V_1} = \frac{1}{50}}$$

KVL in loop (II):

$$-I_b \times 200 + 300(I_2) = 0$$

$$\Rightarrow -6.5I_1 + I_b(200) + 300(I_2) = 0$$

$$\Rightarrow -100I_1 - 200I_2 - 300I_2 = 0$$

$$\Rightarrow -100I_1 = 500I_2$$

$$\text{But, } \underline{\underline{Y_{11}} = \frac{I_1}{V_1} = \frac{1}{50}}$$




$$\text{So, } \underline{\underline{-100 \times \frac{V_1}{50} = 500I_2}}$$

$$\therefore \underline{\underline{Y_{21}} = \frac{I_2}{V_1} = -\frac{1}{250}}$$

Now for second half:

$$\underline{\underline{Y_{12}} = \frac{I_1}{V_2} \Big|_{V_1=0}}, \quad \underline{\underline{Y_{22}} = \frac{I_2}{V_2} \Big|_{V_1=0}}$$

Put, $V_1 = 0$:

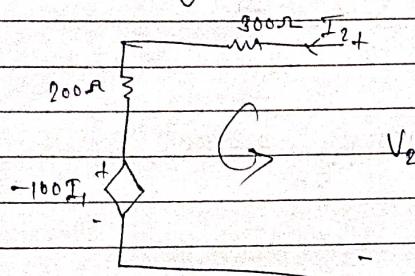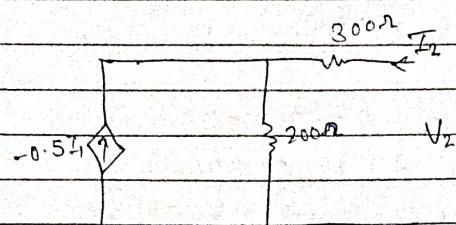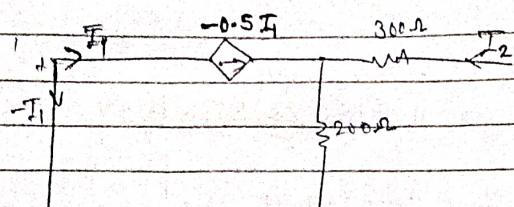


$$-V_2 + 500I_2 - 100I_1 = 0$$

$$\Rightarrow N_2 = 500I_2 - 100I_1$$



$$Y_{22} = \frac{I_2}{V_2} = \frac{1}{500}$$

$$Y_{12} = 0$$

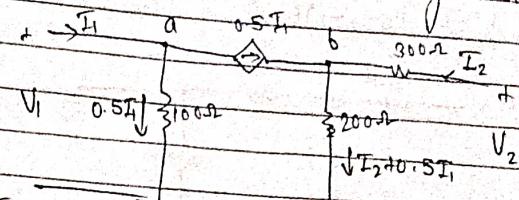
Alternate Method: (without using condition)



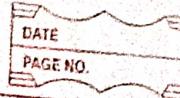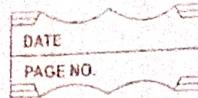A, B, C, D parameters \rightarrow always Ave)




Q) Find T-Parameter.

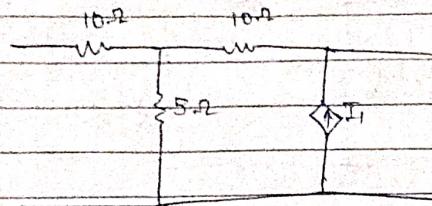

$$\text{Sol: } \begin{cases} V_1 = AV_2 + B(I_2) \\ I_1 = CV_2 + D(-I_2) \end{cases}$$

Put, $V_2 = 0$;

$$\begin{cases} B = \frac{V_1}{-I_2} & |_{V_2=0} \\ D = \frac{I_1}{-I_2} & |_{V_2=0} \end{cases}$$

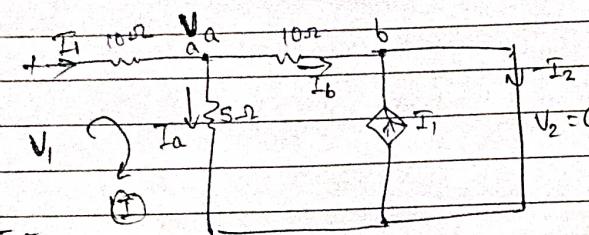

KCL at a:

$$\frac{V_0 - V_1}{10} + \frac{V_0 - 0}{5} + \frac{V_0 - 0}{10}$$

KCL at b:

$$\begin{aligned} I_b + I_1 &= -I_2 \\ \Rightarrow I_b &= -I_1 - I_2 - CII \end{aligned}$$

KCL at a:

$$\begin{aligned} I_1 &= I_a + I_b \\ \Rightarrow I_a &= I_1 - I_b = I_1 + I_1 + I_2 \\ \Rightarrow I_a &= 2I_1 + I_2 \end{aligned}$$

KVL in outer path:

$$\begin{aligned} -V_1 + 10I_1 + 10I_b &= 0 \\ \Rightarrow -V_1 + 10I_1 + 10(-I_1 - I_2) &= 0 \\ \Rightarrow V_1 &= -10I_2 \end{aligned}$$

$$\frac{B = V_1}{-I_2} = 10\Omega$$

KVL in loop I: $-V_1 + 10I_1 + 5I_a = 0$

$$\Rightarrow -10I_2 + 10I_1 + 5(2I_1 + I_2) = 0$$

$$\Rightarrow -5I_2 + 20I_1 = 0$$

$$\Rightarrow \frac{I_1}{I_2} = \frac{15}{20} = \frac{3}{4}$$

$$\therefore D = \frac{3}{4}$$

~~Put, $-I_2 = 0$~~


$$V_1 = A V_2 + B(-I_2)$$

$$I_1 = C V_2 + D(-I_2)$$

Put, $-I_2 = 0$:

$$A = \frac{V_1}{V_2} \quad \left| -I_2 = 0 \right.$$

$$C = \frac{I_1}{I_2} \quad \left| -I_2 = 0 \right.$$

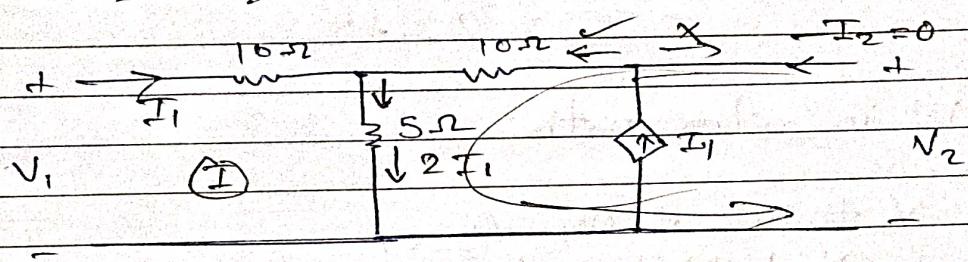

KVL in (I) loop: $-V_1 + 10I_1 + 10I_1 = 0$

$$\Rightarrow V_1 = 20I_1$$

$$\Rightarrow \frac{V_1}{I_1} = 20\Omega \quad (A)$$


KVL in loop (II): $-V_2 + 10I_1 + 10I_1 = 0$

$$\Rightarrow \frac{V_2}{I_1} = 20\Omega$$

$$\Rightarrow \frac{I_1}{V_2} = \frac{1}{20} \quad (B)$$

from (A) & (B) $\therefore A = 1$

Method II: Without Condition

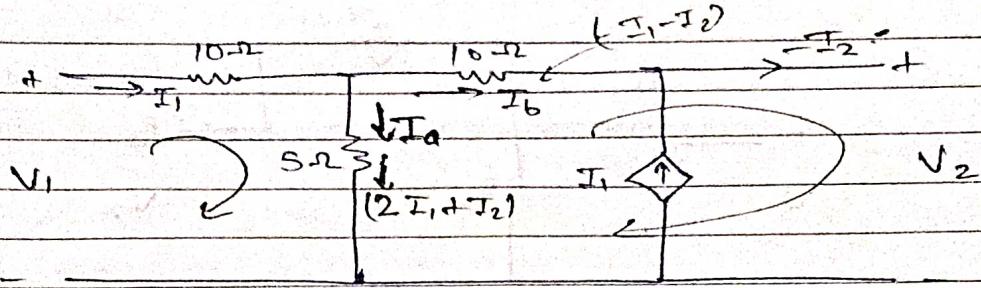

$$V_1 = 10I_1 + 5(2I_1 + I_2)$$

$$\Rightarrow V_1 = 20I_1 + 5I_2 \quad \text{--- (1)}$$

~~$$V_2 = V_2 - 5I_a + 10I_b = 0$$~~

~~$$\Rightarrow V_2 = 5(2I_1 + I_2) \pm -10(I_1 - I_2)$$~~

~~$$\Rightarrow V_2 = 20I_1 + 15I_2 \quad \text{--- (2)}$$~~

$$V_1 = A V_2 + B(-I_2)$$

$$I_1 = C V_2 + D(-I_2)$$

$$I_1 = \frac{V_1 - 5I_2}{20} \quad V_2 - 15I_2$$

~~$$V_2 = 20$$~~


$$V_1 = 20 \left(\frac{V_2 - 15I_2}{20} \right) + 5I_2$$

$$\Rightarrow V_1 = V_2 - 10I_2$$

$$20I_1 = V_2 - 15I_2$$

b) Calculate H-Parameters.

DATE
PAGE NO.

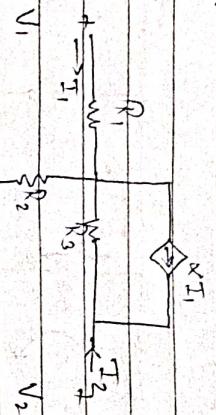


SOL:

$$\begin{aligned} V_1 &= h_{11}I_1 + h_{12}V_2 \\ &= V_1 \bullet + I_1 R_1 + I_2 R_2 = 0 \end{aligned}$$

$$V_2 = h_{21}I_1 + h_{22}V_2$$

Put, $V_2 = 0$:

$$h_{11} = \frac{V_1}{I_1}, V_2 = 0 \quad | \quad h_{21} = \frac{I_2}{I_1}, V_2 = 0$$

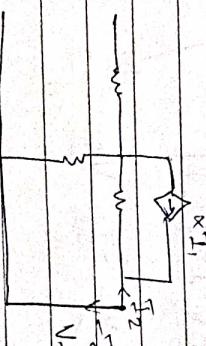

KVL in loop II:

$$-I_2 R_2 - \alpha R_3 I_1 - I_2 R_3 = 0$$

$$(-R_2 + \alpha R_3) R_2 - \alpha R_3 I_1 - R_2 I_2 = 0$$

$$\Rightarrow (-R_2 - R_3) I_2 + (-R_2 - R_3) I_2 = 0$$

$$\Rightarrow \frac{I_2}{I_1} = -\frac{(R_2 + \alpha R_3)}{R_2 + R_3} \quad (1)$$

$$\Rightarrow I_2 = -\frac{I_1 (R_2 + \alpha R_3)}{R_2 + R_3}$$

$$\textcircled{1} \Rightarrow V_1 = (R_1 + R_2) I_1 + R_2 \frac{(R_2 + \alpha R_3) I_1}{R_2 + R_3}$$

$$= (R_1 + R_2)(R_2 + \alpha R_3) I_1 - R_2 (R_1 + \alpha R_3) I_1$$


$$= \frac{(R_1 R_2 + R_1 \alpha R_3 + R_2^2 + R_2 \alpha R_3) I_1}{R_2 + R_3}$$

$$\Rightarrow V_1 = \frac{(R_1 R_2 + ((1-\alpha) R_2 + R_1) \alpha) I_1}{(R_1 + R_2)}$$

$$\Rightarrow \underline{\underline{V}} = \underline{\underline{R}}_1 + \underline{\underline{L}} \underline{\underline{R}}_2 \underline{\underline{R}}_3 \underline{\underline{R}}_1$$

Q) The h-Parameter of a 2-Port network shown in figure are $h_{11} = 1000 \Omega$, $h_{12} = 0.003$, $h_{21} = 100$, $h_{22} = 50 \times 10^{-6} \text{ V}$. Find V_2 & 2-Parameter of the network if $V_s = 10^{-12} L^{\circ} \text{ V}$.

Solⁿ:

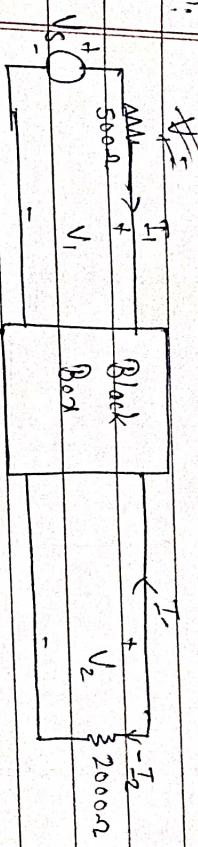

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

$$-V_s + 500 I_1 + V_1 = 0$$

$$\Rightarrow V_1 = V_s - 500 I_1$$

$$\Rightarrow V_s - 500 I_1 =$$

DATE 10/8/23
PAGE NO.

Inter-relationships between different Parameters

Express Z-Parameters in terms of Y-Parameters

Z Parameters are:

$$V_1 = Z_{11} I_1 + Z_{12} I_2 \quad (1)$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2 \quad (2)$$

Y-Parameters are :

$$I_1 = Y_{11} V_1 + Y_{12} V_2 \quad (3)$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2 \quad (4)$$

$$\text{from eqn 4: } V_2 = \frac{I_2 - Y_{21} V_1}{Y_{22}} \quad (5)$$

Using eqn 5 in 3:

$$I_1 = Y_{11} V_1 + Y_{12} \left(\frac{I_2 - Y_{21} V_1}{Y_{22}} \right)$$

$$\Rightarrow Y_{22} I_1 = Y_{22} Y_{11} V_1 + Y_{12} I_2 - Y_{21} Y_{11} V_1$$

$$\Rightarrow (Y_{11} Y_{22} - Y_{12} Y_{21}) V_1 = Y_{22} I_1 - Y_{12} I_2$$

$$V_1 = \frac{Y_{22}}{\Delta Y} I_1 - \frac{Y_{12}}{\Delta Y} I_2 \quad (6)$$

$$Z_{21} = -\frac{Y_{21}}{\Delta Y}, \quad Z_{22} = \frac{Y_{11}}{\Delta Y}$$

where, $(\Delta Y = Y_{11}Y_{22} - Y_{12}Y_{21})$

Comparing (1) & (6) :-

$$Z_{11} = \frac{Y_{22}}{\Delta Y}, \quad Z_{12} = -\frac{Y_{12}}{\Delta Y}$$

From eqn 3 :-

$$V = \frac{I_1 - Y_{12} V_2}{Y_{11}} \quad (7)$$

Using eqn (7) in (4) :-

$$I_2 = Y_{21} \left(\frac{I_1 - Y_{12} V_2}{Y_{11}} \right) + Y_{22} V_2$$

$$\Rightarrow Y_{11} I_2 - Y_{21} I_1 = (Y_{11} Y_{22} - Y_{12} Y_{21}) V_2$$

⇒ Cascade Connection (only T-parameters is used)

$$\Rightarrow \Delta Y V_2 = -Y_{21} I_1 + Y_{11} I_2$$

$$V_2 = -\frac{Y_{21}}{\Delta Y} I_1 + \frac{Y_{11}}{\Delta Y} I_2 \quad (8)$$


$$V_2 = V_3$$

$$I_2 = -I_1$$



$$T = [T_a] [T_b]$$

Connections of 2-Port Network System

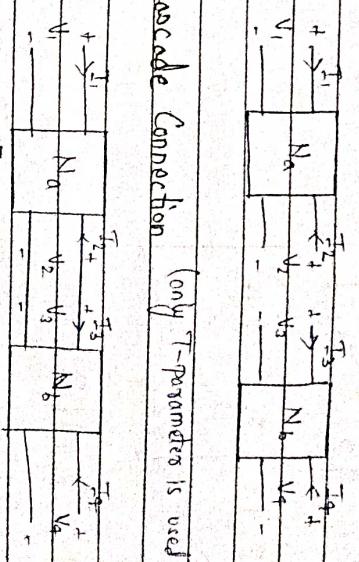1. Cascade Connection
2. Series "
3. Parallel "
4. Series-Parallel "
5. Parallel-Series "



2) Series Connection

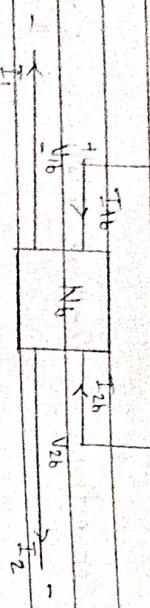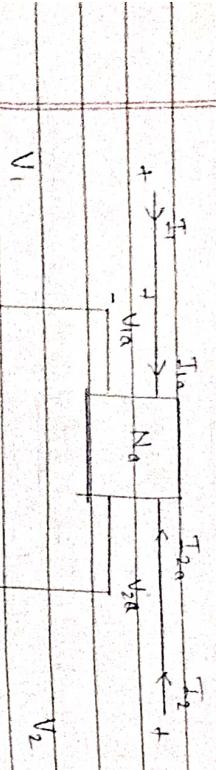

$$V_1 = V_{1a} + V_{1b}$$

$$V_2 = V_{2a} + V_{2b}$$

$$I_1 = I_{1a} = I_{1b}$$

$$I_2 = I_{2a} = I_{2b}$$

$$[Z_o] = \begin{bmatrix} Z_{11a} & Z_{12a} \\ Z_{21a} & Z_{22a} \end{bmatrix}$$

$$[Z] = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix}$$



$$Y_{11} = Y_{11a} + Y_{11b}$$

$$Y_{12} = Y_{12a} + Y_{12b}$$

$$Y_{21} = Y_{21a} + Y_{21b}$$

$$Y_{22} = Y_{22a} + Y_{22b}$$

3) Parallel Connection

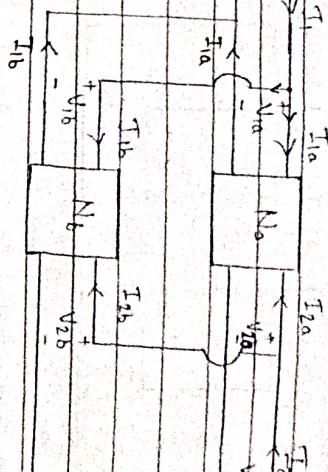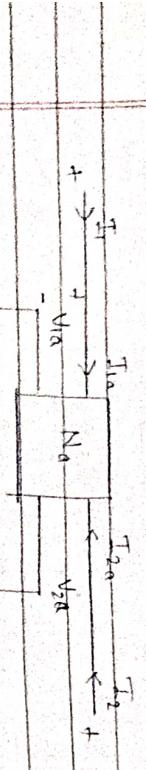

$$V_1 = V_{1a} = V_{1b}$$

$$I_1 = I_{1a} + I_{1b}$$

$$V_2 = V_{2a} \neq V_{2b}$$

$$I_2 = I_{2a} + I_{2b}$$

$$= \begin{bmatrix} Z_{11a} + Z_{11b} & Z_{12a} + Z_{12b} \\ Z_{21a} + Z_{21b} & Z_{22a} + Z_{22b} \end{bmatrix}$$

$$\begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} Z_{11a} + Z_{11b} & Z_{12a} + Z_{12b} \\ Z_{21a} + Z_{21b} & Z_{22a} + Z_{22b} \end{bmatrix}$$

$$h_{22} = h_{21a} + h_{21b}$$

$$h_{21} = h_{21a} + h_{21b}$$

$$h_{12} = h_{12a} + h_{12b}$$


$$h_{11} = h_{11a} + h_{11b}$$

$$I_1 = I_{1a} = I_{1b}$$

$$I_2 = I_{2a} + I_{2b}$$

I_1

V_1

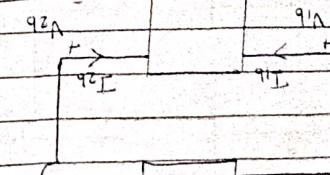


$$V_1 = V_{1a} + V_{1b}$$

$$I = I_{1a} + I_{2a}$$

$$I_2 = I_{2a} + I_{2b}$$

$$V_1 = V_{1a} = V_{1b}$$

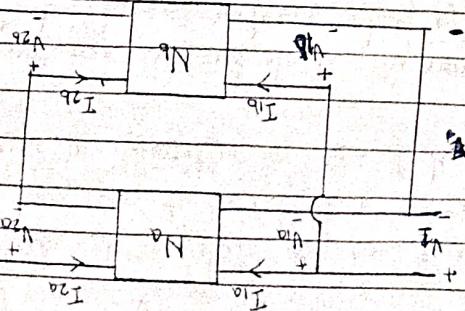


$$V_2 = V_{2a} = V_{2b}$$

$$I_1 = I_{1a} + I_{1b}$$

$$V_1 = V_{1a} + V_{1b}$$

V_2

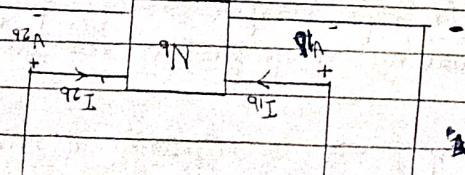

5) Parallel-Series Connection

4) Series-Parallel Connection

Reciprocity and Symmetry of 2 Port Network


* A 2-Port network is said to be Reciprocal if

ratio of response to excitation remains invariant to the change in position of the two

* A 2-Port network is said to be Symmetrical if ports can be interchanged without changing the current and voltage.

Adapting the changes in eqn 1 & 2.
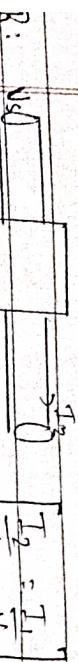
$$V_s = Z_{11} I_1 - Z_{12} I_2 \quad (3)$$




$$R: \quad \begin{array}{c} V_s \\ \parallel \\ \text{Block} \\ \parallel \\ I_2 \end{array} \quad \left[\frac{I_2}{V_s} = \frac{Z_1}{Z_2} \right]$$

$$\therefore \begin{array}{c} I_1 \\ \parallel \\ \text{Block} \\ \parallel \\ I_2 \end{array} \quad \left[\frac{V_1}{I_1} = \frac{V_2}{I_2} \right]$$

$$\text{from eqn 4: } I_1 = \frac{Z_{22} I_2}{Z_{21}} \quad (5)$$
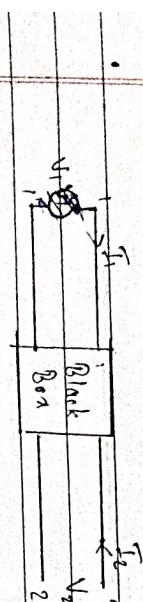
$$V_s = Z_{11} \left(\frac{Z_{22} I_2}{Z_{21}} \right) - Z_{12} I_2$$




$$\Rightarrow V_s = \frac{Z_{21}}{Z_{11} Z_{22} - Z_{12} Z_{21}} \quad (6)$$

Now, interchange the position of response & excitation.

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

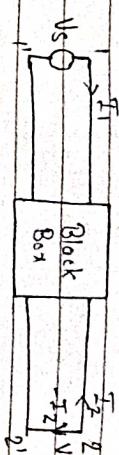

Let, V_s is the excitation voltage applied at 1st and Z_2 is the response obtained after short circuiting the 2nd port.

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

$$\text{So, } 0 = -Z_{11} I_1 + Z_{12} I_2$$

$$V_s = -Z_{21} I_1 + Z_{22} I_2$$



$$V_s = h_{11} I_1 + 0 \Rightarrow I_1 = \frac{V_s}{h_{11}}$$

$$-I_2 = h_{21} I_1 \Rightarrow -I_2 = \frac{h_{21} V_s}{h_{11}}$$

$$\Rightarrow \frac{I_2}{V_s} = \frac{-h_{21}}{h_{11}}$$

Now, Interchange Response & Excitation

h -Parameters

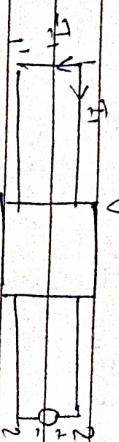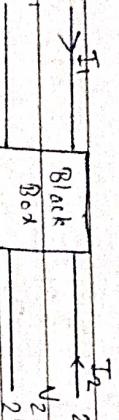

Connect V_s at 22' and short circuit 11' i.e. $V_1 = 0$

$$V_s = h_{11} I_1 + h_{12} V_2 \quad (1)$$

$$0 = -h_{11} I_1 + h_{12} V_2 \quad (2)$$




Symmetry



$$V_1 = Z_{11} I_1 + Z_{12} I_2 \quad (1)$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2 \quad (2)$$

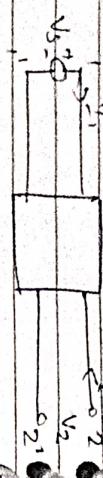Connect a voltage source ' V_s ' at '11' and make '22'' open.




Hence, eqn (1) becomes:-

$$V_s = Z_{11} I_1$$

$$\Rightarrow \frac{V_s}{Z_{11}} = I_1 \quad (3)$$

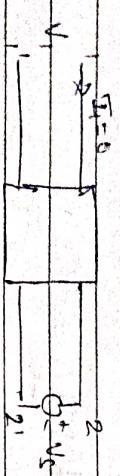Now, connect V_s at '22'' & open circuit '11'.



$$I_1 = Y_{11} V_s + Y_{12} V_2 \quad (3')$$

$$0 = Y_{21} V_s + Y_{22} V_2 \quad (4)$$


$$\text{from } 4: V_2 = -\frac{Y_{21} V_s}{Y_{22}}$$

$$I_1 = Y_{11} V_s - \frac{Y_{21} Y_{12} V_s}{Y_{22}}$$

$$\text{from eqn 2: } V_s = Z_{22} I_2$$

$$\text{Hence, } \frac{V_s}{Z_{22}} = Z_{22} I_2 \quad (4)$$

Y-Parameters

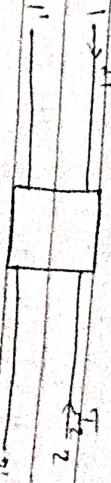

$$I_1 = Y_{11} V_1 + Y_{12} V_2 \quad (1)$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2 \quad (2)$$

Connect V_s at '11' & open circuit '22'.



$$I_1 = Y_{11} V_s + Y_{12} V_2 \quad (3)$$

$$0 = Y_{21} V_s + Y_{22} V_2 \quad (4)$$

$$\text{from } 4: V_2 = -\frac{Y_{21} V_s}{Y_{22}}$$

$$I_1 = Y_{11} V_s - \frac{Y_{21} Y_{12} V_s}{Y_{22}}$$

$$= \left(Y_{11} Y_{22} - Y_{12} Y_{21} \right) V_s$$

$$\frac{V_s}{Z_{22}} \Rightarrow \frac{V_s}{I_1} = \frac{V_{22}}{Y_{11} Y_{22} - Y_{12} Y_{21}}$$



$$V_s = Y_{11}V_1 + Y_{12}V_2 \quad (6)$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2 \quad (7)$$


$$\text{From eqn 6 : } V_1 = -\frac{Y_{12}}{Y_{11}}V_s$$

$$I_2 = Y_{21} \left(-\frac{Y_{12}}{Y_{11}}V_s \right) + Y_{22}V_s$$

$$\text{So, } V_s = b_{11}I_2 + b_{12} \cdot \left(-\frac{b_{21}}{b_{11}}I_2 \right)$$

$$\Rightarrow \frac{V_s}{I_2} = \frac{Y_{11}}{Y_{11}Y_{22} - Y_{12}Y_{21}} \quad (8)$$

H-Parameters

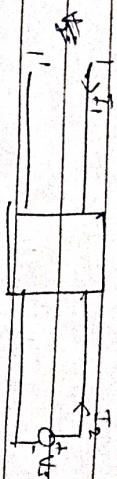

$$V_1 = h_{12}V_s$$

$$I_2 = h_{21}V_s$$


$$V_s = h_{11}I_2 + h_{12}V_2 \quad (9)$$

$$V_s = h_{21}I_1 + h_{22}V_2 \quad (10)$$

$$\Rightarrow \frac{V_s}{I_2} = \frac{h_{21}}{h_{22}}$$

DATE 14/18/23
PAGE NO.

DATE _____
PAGE NO. _____

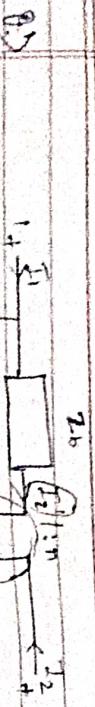

$$V_1 = 2_a (T_1 - T_2')$$

$$= 2_a T_1 + n T_2' 2_a \\ = 2_a T_1 + n 2_a T_2 \quad (3)$$

$$V_2' + (T_2' - T_1) 2_a + T_2' Z_b = 0$$

Soln: $a = \frac{1}{n}$ (given)

$$\rightarrow \frac{T_1'}{T_2} = \frac{V_1}{V_2} = \frac{1}{n}, \quad \frac{T_2'}{T_1} = -n$$

$$V_1$$

$$V_2$$

$$\frac{V_1}{V_2} = \frac{1}{n}$$

$$n$$

④

$$\Rightarrow V_2 = n 2_a T_1 + n^2 (2_a + 2_b) T_2 \quad (4)$$

Q.) Find 2-Parameter (Symmetrical Lattice Network)

$$+ \xrightarrow{T_1} A \xleftarrow{T_2} -$$

$$\rightarrow T_2' = -n T_2 \quad (1)$$


$$\frac{V_1'}{V_2} = \frac{1}{n} \Rightarrow V_1' = \frac{V_2}{n} \quad (2)$$

$$V_1' = \frac{V_2}{n}$$

$$V_2' = \frac{V_2}{n}$$

Soln:
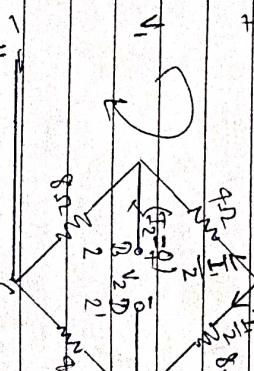
$$+ \xrightarrow{T_1} A \xleftarrow{T_2} -$$



Put, $I_2 = 0 \therefore$

$$-\sqrt{1} + \frac{9}{2} I_1 + \frac{8}{2} I_2 = 0$$

$$\Rightarrow -\sqrt{1} + 2 I_1 + \frac{9}{2} I_2 = 0$$

$$\Rightarrow \frac{\sqrt{1}}{I_1} = \frac{6}{2} \Omega = Z_{11}$$

$$\text{Now, } -\sqrt{2} - \frac{I_1}{2} \times 9 + \frac{I_1}{2} \times 8 = 0$$



$$\frac{I_1}{2} = 2$$

$$\Rightarrow \sqrt{2} = -I_1 + \frac{9}{2} I_1 = \frac{7}{2} I_1$$

$$\therefore Z_{21} = \frac{V_2}{I_1} = \frac{2}{2} \Omega$$

Put, $I_1 = 0 \therefore$

$$I_1 = 0$$

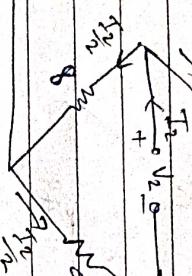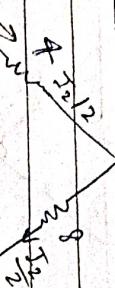

$$\sqrt{2} + \frac{9}{2} I_2 + \frac{8}{2} I_1 = 0$$

$$\frac{I_2}{2} + \frac{I_1}{2} = 0$$

$$\Rightarrow 2 Z_{22} = \frac{V_2}{I_2} = \frac{6}{2} \Omega$$

$$-\sqrt{1} - \frac{9}{2} \frac{I_2}{2} + \frac{8}{2} \frac{I_1}{2} = 0$$

$$\Rightarrow \frac{\sqrt{1}}{I_2} = 2 \Omega = Z_{22}$$

$$\therefore [2] = \begin{bmatrix} 6 & 2 \\ 2 & 6 \end{bmatrix}$$


Q)

$$\begin{array}{|c|c|c|c|} \hline & R_{a1} & R_{a2} & R_{b1} \\ \hline R_{a1} & 3 & 3 & 3 \\ \hline R_{a2} & 3 & 3 & 3 \\ \hline R_{b1} & 3 & 3 & 3 \\ \hline \end{array}$$

Twin-T Parallel Circuit
[$(T+T)$ network combination]

OR

(T)

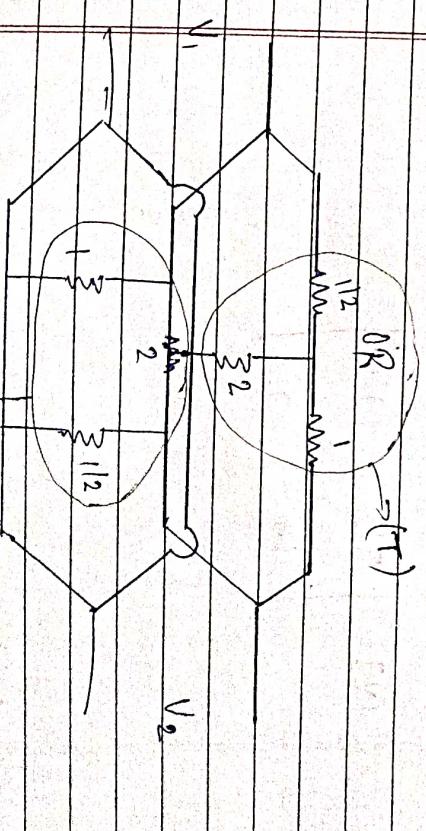

(T)

DATE 14/8/23
PAGE NO. 1

DATE 14/8/23
PAGE NO. 1



Network Function

$$H(s) = \frac{V_2(s)}{V_1(s)} \propto \frac{\text{Zero State Response}}{\text{Excitation}}$$

Response = Zero Input Response + Zero State Response

\downarrow \downarrow \downarrow
d.p. No Excitation All the initial
conditions are zero.

Complete Solution No input

1. Driving Point Impedance Function
(Impedance + Admittance)

$$[Z] = \begin{bmatrix} 5/2 & 2 \\ 2 & 5/2 \end{bmatrix}$$


$$2. \text{ Forced T.F. Impedance} = \frac{V_2(s)}{I_1(s)}$$

Transfers

$$3. \text{ Reverse Transfer Impedance} = \frac{V_1(s)}{I_2(s)}$$


$$4. \text{ Voltage T.F. function} = \frac{V_2(s)}{V_1(s)}$$
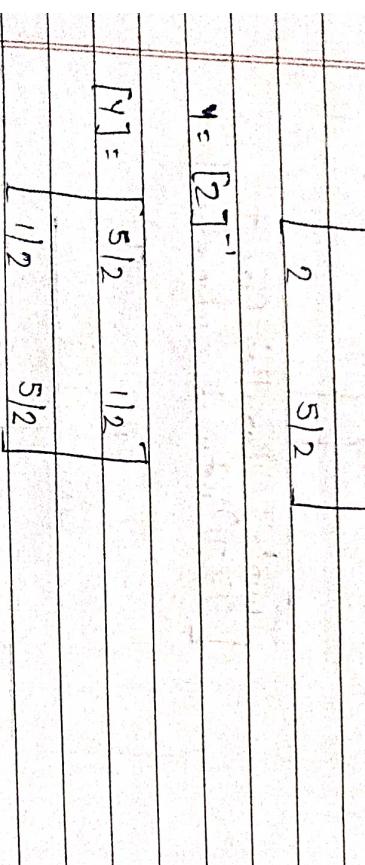
$$5. \text{ Current T.F. function} = \frac{I_2(s)}{I_1(s)}$$




Input Impedance


for

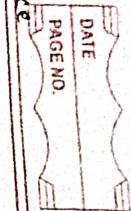

2H

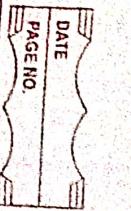


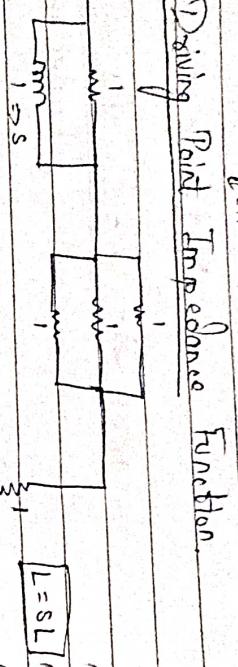B) Find out Driving Point Impedance Function.




Solⁿ:

↓ Transformed network

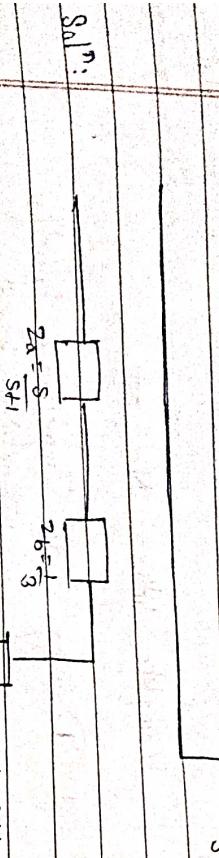

Using Star:

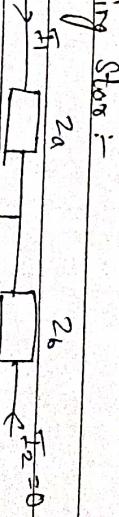

$$Z_{11} = V_1 / I_1 = 2a + 2b + 2c$$

$$V_1(s) \quad | \quad Z_{11}$$

$$= \frac{S}{S+1} + \frac{1}{S}$$

$$= \frac{3S^2 + 3S + 1}{3S(S+1)} = \frac{(S+1)(3S+1)}{3S(S+1)}$$

$$Z_b = \frac{1}{2+2S}$$

$$Z_c = \frac{1 \times 2S}{2+2S} = \frac{S}{S+1}$$

Find $V_2(S)$

$\frac{V_2(S)}{V_1(S)}$

$$H(S) = \frac{a_n S^n + a_{n-1} S^{n-1} + a_{n-2} S^{n-2} + \dots + a_0}{b_m S^m + b_{m-1} S^{m-1} + b_{m-2} S^{m-2} + \dots + b_0}$$


$$= K \prod_{i=1}^n (S - Z_i)$$

$$\prod_{j=1}^m (S - P_j)$$

$$K \text{ is a Scaling Factor : } K = \frac{a_n}{b_m}$$

S is a Complex Frequency

$j\omega$

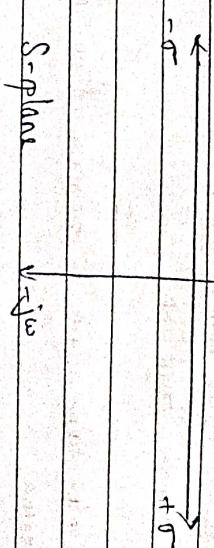

S-plane

$$S = \sigma \pm j\omega \rightarrow \text{angular frequency (rad/sec.)}$$

Attenuation factor
having unit "Neper"

Note:

- * When each factors of Numerator is equated to zero, their frequency obtained is called as Zeros of Network Function.

1.

$$S \cdot 2_1 = 0, \quad S - 2_2 = 0, \quad S^2 -$$

$$\Rightarrow S = 2_1, \quad \Rightarrow S = 2_2$$

- * If factor of denominator is equated to zero, then freq. obtained is called Poles of New function.

$$S - P_1 = 0, \quad S - P_2 = 0$$

$$\Rightarrow S = P_1, \quad \Rightarrow S = P_2$$

$$K = \frac{(S-2_1)(S-2_2)}{(S-P_1)(S-P_2) \dots (S-P_n)}$$

$$\text{Ex: } H(S) = \frac{S(S+1)}{(S^2 + 2S + 2) \cdot (S^3)}$$

- * Zeros & Poles are called as Critical Frequency of Network Function.

* In a new func., no. of zeros & no. of poles are same.

* Multiplicity \rightarrow repetition

$$= \frac{S(S+1)}{(S+1-j)(S+1+j) \cdot S^3}$$

Numerator: $S(S+1) = 0$

$$\Rightarrow S = 0, \quad S = -1$$

2 Zeros

$$\text{Denominator: } (S+1-j)(S+1+j).S^3 = 0$$

$$S^3 = 0$$

$$\Rightarrow S = 0, 0, 0$$

$$S+1-j1=0 \quad S+1+j1=0$$

$$\Rightarrow S=j1-1 \quad \Rightarrow S=-j1-j1$$

$\therefore 5$ Poles i.e. $0, 0, 0, -1 \pm j1$

$$\text{Poles - Zeros} = 5-2=3$$

$\therefore 3$ zeros are present at ∞

Representation of Poles and Zeros in S-Plane

Zeros - 0 Poles - X

If any one pole is present in right half of S Plane \Rightarrow Unstable

$$H(S) = \frac{(S+2)(S+3)}{(S+1)(S+4)(S+5)(S-7)}$$

Let, $S=7$, then find k.

$$(7+1)(7+4)(7+5) = 74$$

The location of zeros doesn't decide Stability all

If 1 Pole are present in left half of S Plane

\Rightarrow Stable


If any one pole is present in right half of S Plane \Rightarrow Unstable


$$H(S) = \frac{1}{S} \rightarrow \text{Unit Step func. in S-domain}$$

$$H(S) = \frac{1}{S^2} \rightarrow \text{Unit ramp func. in S-domain}$$

$$H(S) = \frac{1}{S+1}$$


$$H(S) = \frac{1}{(S+1)(S+2)}$$

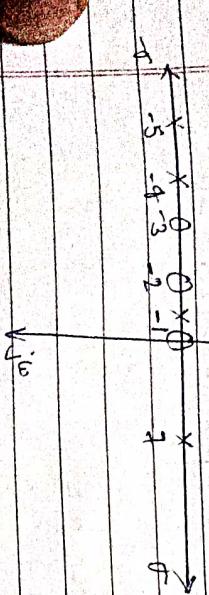


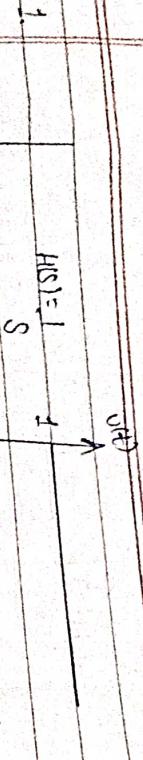


$$u(t) = 1 ; \text{ for } t \geq 0 \\ = 0 ; \text{ for } t < 0$$

$$H(S) = \frac{1}{S^2}$$

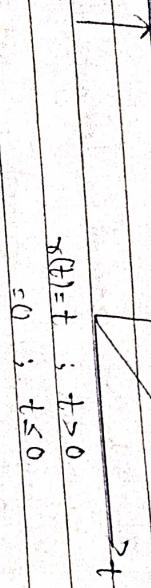

$$H(S) = \frac{1}{(S-1)^2}$$

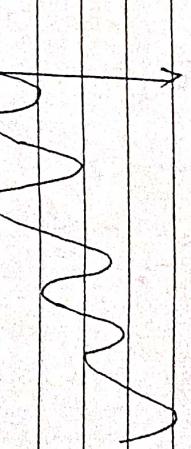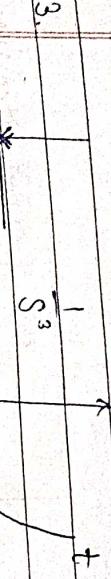

Some Important Laplace Transform and its Inverse

$$\mathcal{X} f(t) = F(s)$$

$$F(s) = \int_0^\infty f(t) e^{-st} dt$$

$$\text{in } e^{-at} \xrightarrow{\quad} \frac{1}{s-a}$$

$$= \int_0^\infty e^{-at} e^{-st} dt$$

$$= 1$$

$$(iii) e^{at} \xrightarrow{\quad} s-a$$

$$(iv) e^{at} \sin \omega t \xrightarrow{\quad} \frac{\omega}{(s-a)^2 + \omega^2}$$

(Damped Sine wave func.) $\frac{(s+2)^2 + 3^2}{(s+2)^2 + (\sqrt{3})^2}$

$$e^{-at} \sin \omega t = \frac{\omega}{(s+a)^2 + \omega^2}$$

$$vii) e^{-at} \cos \omega t \xrightarrow{\quad} \frac{s-a}{(s+a)^2 + \omega^2}$$

$$e^{-t} \cos 4t = \frac{s+1}{(s+1)^2 + 16}$$

$$viii) Impulse : \mathcal{L} S(t)=1$$


ix)

$$\begin{aligned} \text{sin at} &\xrightarrow{\quad} \frac{\omega}{s^2 + \omega^2} \\ \text{sin at} &\xrightarrow{\quad} \frac{\omega}{s^2 + \omega^2} \end{aligned}$$

$$\sin 3t = \frac{3}{s^2 + 9}$$

$$(v) \cos \omega t \xleftrightarrow{\quad} \frac{s}{s^2 + \omega^2}$$

S-Har

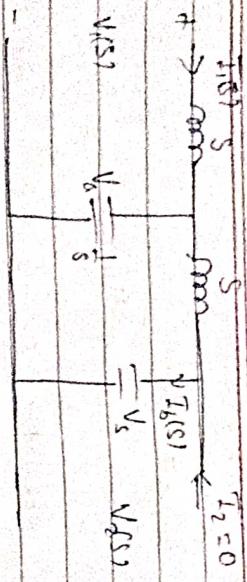

$$T_b(s) = \frac{V_o(s)}{1/s} = sV_2(s) = 0 \quad (1)$$

$$\text{KVL: } -V_o(s) + sT_b + V_2(s) = 0$$

$$\Rightarrow V_o(s) = (s^2 + 1) \cdot V_2(s) \quad (2)$$

$$T_a(s) = \frac{V_a}{1/s} = sV_a = s(s^2 + 1) \cdot V_2(s) \quad (3)$$

$$\text{But, } T_a(s) = T_o(s) + T_b(s)$$

$$= (s^3 + s) \cdot V_2(s) + s \cdot V_2(s) \quad (4)$$


$$-V_o(s) + T_o(s) \times s + V_a = 0$$

$$\Rightarrow V_o(s) = (s^3 + 2s) \cdot s V_2(s) + (s^4 + 1) \cdot V_2(s)$$


$$V_o(s) = (s^4 + 3s^2 + 1) \cdot V_2(s)$$

$$\therefore \frac{V_o(s)}{V_s(s)} = \frac{1}{s^4 + 3s^2 + 1} \quad (\text{Voltage gain})$$

(b)

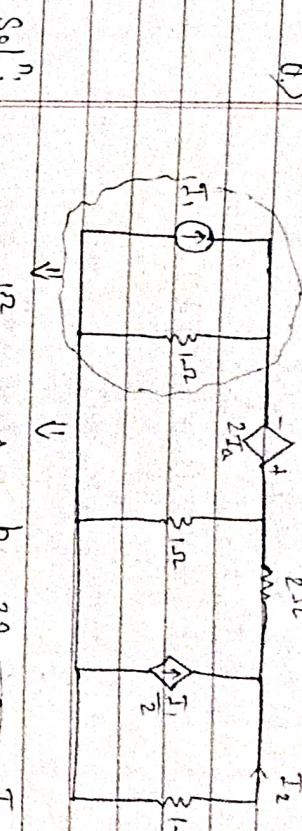

Soln.

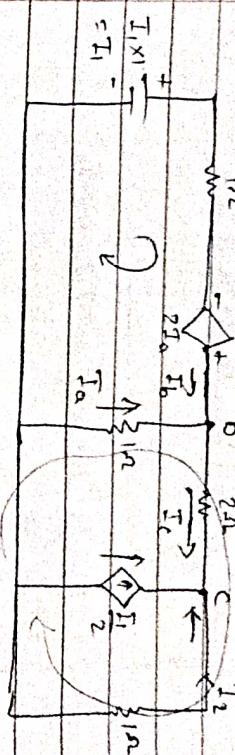

$$\text{KCL at C: } T_c + T_a + T_1 = 0$$

$$\Rightarrow T_c = -\left(T_2 + \frac{T_a}{2}\right)$$

$$\text{KCL at B: } T_b + T_a = T_c$$

$$\Rightarrow T_b = T_c - T_a = -\left(\frac{T_1}{2} + T_2 + T_a\right)$$

$$\text{KVL at B: } T_1 + T_b \times 1 - 2T_a - T_2 = 0$$

$$\Rightarrow T_b = -T_1 - T_2 - T_a - 3T_a$$

$$\Rightarrow T_1 + T_a = -T_2 - 4T_a$$

$$KVL: T_a \times 1 + 2T_c - T_2 = 0$$

$$\begin{aligned} \Rightarrow T_a &= -2T_c + T_2 \\ &= +2\left(T_2 + \frac{T_1}{2}\right) + T_2 \\ \therefore T_a &= 3T_2 + T_1 \end{aligned}$$

$$S.E. \frac{3}{2}T_1 = -T_2 - 2(3T_2 + T_1)$$

$$\Rightarrow \frac{3}{2}T_1 = -T_2 - 12T_2 - 2T_1$$

$$\boxed{T_2 = \frac{-11}{26}}$$

∴ \Rightarrow

$$\begin{aligned} T_4 &= T_5 + T_6 = (1+s).V_2 \\ -V_a + T_4 \times s + V_2 &= 0 \\ \Rightarrow V_a &= \{1+s\}s+1 \cdot V_2 \\ \therefore V_a &= (s^2+s+1).V_2 \end{aligned}$$

$$\begin{aligned} T_3 &= \frac{V_a}{1/s} = SV_a = S(s^2+s+1).V_2 \\ &= (s^3+s^2+s).V_2 \end{aligned}$$

$$\begin{aligned} T_2 &= T_3 + T_4 = (S^3+S^2+s+1+s)V_2 \\ &= (S^3+S^2+2s+1).V_2 \end{aligned}$$

$$-V_1 + T_2 \times s + V_a = 0$$

$$\begin{aligned} \Rightarrow V_1 &= S \times (S^3+S^2+2s+1)V_2 + (S^2+s+1)V_2 \\ &= (S^4+S^3+2s^2+s+1)V_2 \end{aligned}$$

$$\frac{V_2}{V_1} = \frac{1}{S^4+S^3+2s^2+s+1}$$

