
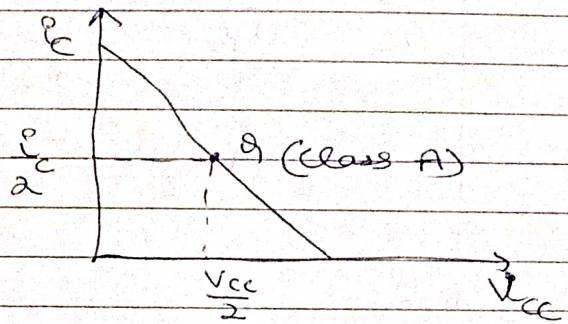


L-Module - 2

8/9

1) Class A Power Amp :-

Full
Swing
(0 - 360°)

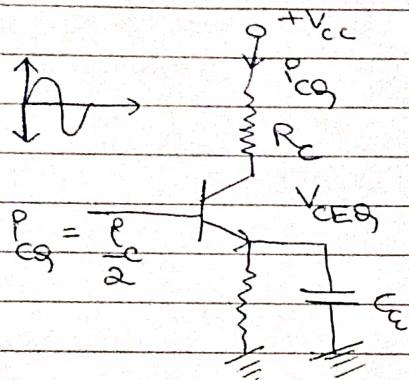


$$\text{Efficiency} = \frac{P_{o\ AC}}{P_{o\ DC}} \quad . \quad P_{o\ DC} = V_{cc} \times \frac{I_c}{2}$$

$$P_{o\ AC} = \frac{V_{rms} \times I_{rms}}{2}$$

$$\text{So, } P_{o\ AC} = \frac{V_{cc} \times I_c}{8}, \quad P_{o\ DC} = \frac{V_{cc} \times I_c}{2}$$


$$\eta = \frac{V_{cc} \times I_c \times 2}{8 \times V_{cc} \times I_c} = 25\%$$

2) Class A Push Pull Config :-

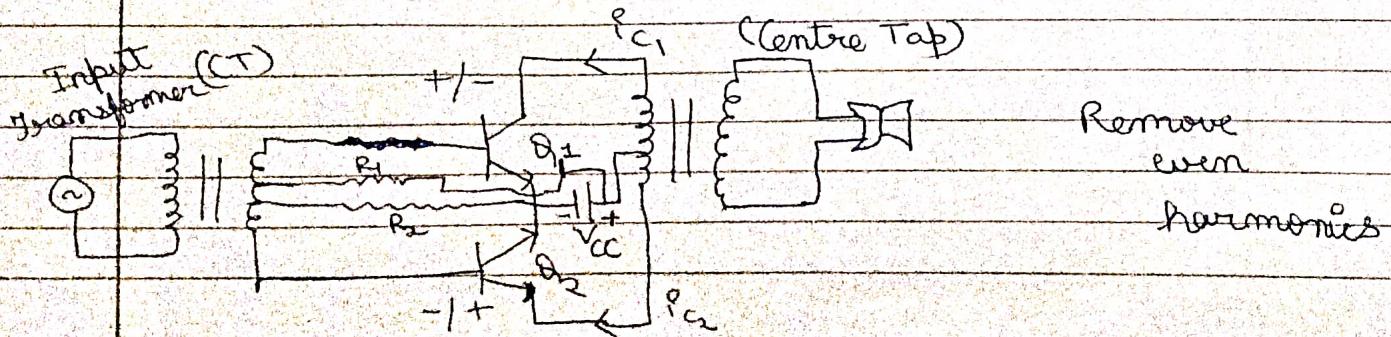

Push-Pull increases quality of ckt & decrease distortions but never efficiency.

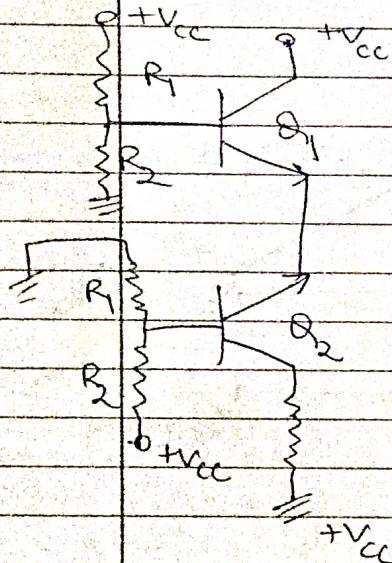→ It is just a combo of two class A transformer ~~stage~~



→ Harmonic distortions is less here.
→ No dc components are available hence the energy will be utilized in ac components.

→ No even harmonics are present we get max. swing in this cases.

→ i_{c1} & i_{c2} are equal & opposite so $i_c = i_{c1} + (-i_{c2})$

$$\rightarrow i_{b1} = i_b \sin \omega t$$

$$\rightarrow i_{b2} = i_b \sin(\omega t + \pi)$$


$$i_{c1} = i_c \sin \omega t \Rightarrow P_c + i_{c1}^2 \sin^2 \omega t + i_{c2}^2 \sin^2 \omega t + \dots$$

$$i_{c2} = i_c \sin(\omega t + \pi) \Rightarrow P_c + i_{c1}^2 \sin(\omega t + \pi) + i_{c2}^2 \sin(\omega t + \pi), \dots$$

$$\text{Now, } i_c = i_{c1} - i_{c2}$$

$$P_c = 2P_c \sin^2 \omega t + 2P_c \sin^3 \omega t + 2P_c \frac{\sin^5 \omega t}{5}, \dots$$

Class B Power Amp :-

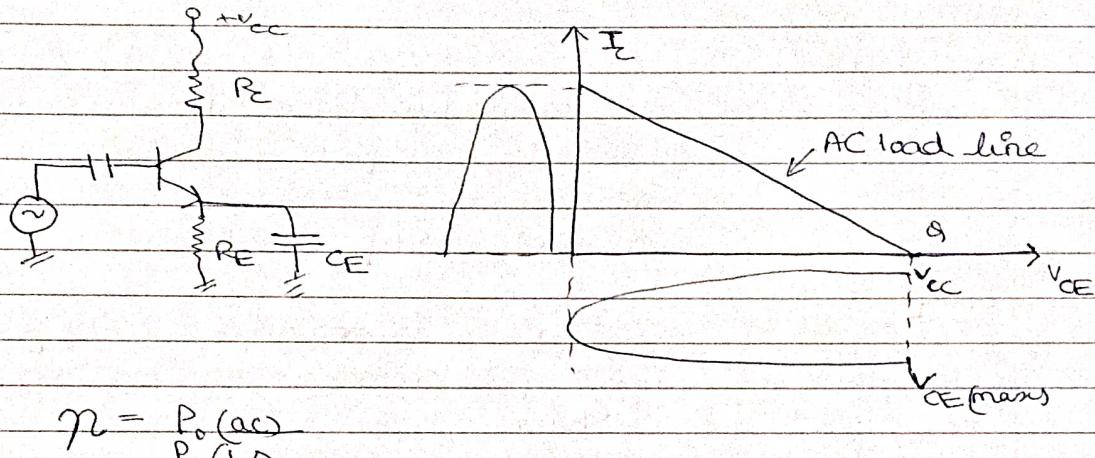

$$\eta = \frac{P_o(\text{ac})}{P_o(\text{dc})}$$

- It conducts only for half P/P cycle
- No P/P biasing ckt are required
- Q point is always at cut-off as \$I_b = 0\$ for ~~no P/P~~
hence \$I_C = 0\$


$$P_o(\text{ac}) = V_{\text{oms}} I_{\text{oms}} = V_{CE} \frac{I_C(\text{max})}{4} \quad \text{Song I less than class A's}$$

$$P_o(\text{dc}) = V_{CC} I_{Q\text{dc}} = V_{CC} I_{\text{avg}} \quad \left\{ I_{\text{avg}} = \frac{1}{2\pi} \int_0^{\pi} i_{\text{max}} \sin \theta d\theta \right\}$$


$$= V_{CC} \frac{i_{\text{c max}}}{\pi}$$

$$\eta = \frac{V_{CE} \times I_{C(\text{max})} \times \pi}{4 \times V_{CC} \times I_{\text{c max}}} \Rightarrow \frac{\pi}{4} \Rightarrow 78.5\%$$

Class B Push Pull Config :-

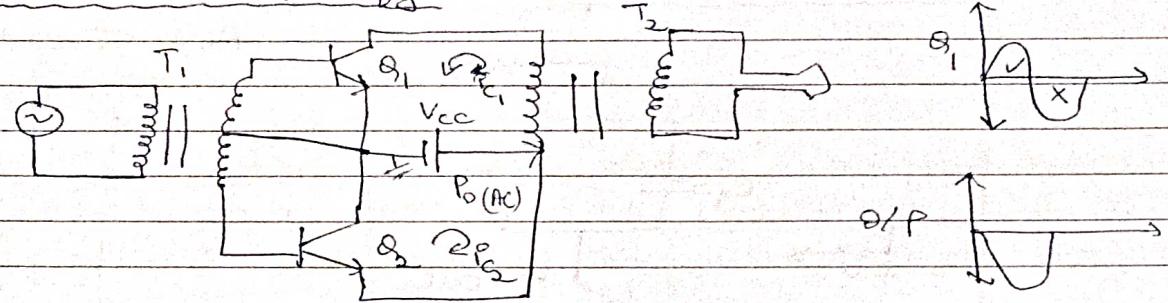

$$E_C = P_{C_1} - P_{C_2}$$

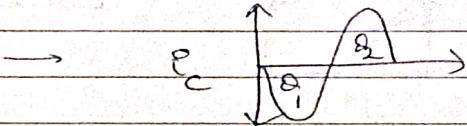

$$\eta = \frac{P_{O\text{ ac}}}{P_{P\text{ in ac}}}$$

→ No biasing circuit IPhe R_f & B₂ is needed at O/P

→ For first cycle Q₁ as positive peak appear at base so pf work as

→ Counter process is done through Q₂ & hence a full sinusoidal signal got 180° out of phase is observed at O/P side. Hence a negative amplifier of amplifier.


$$P_{O\text{ (AC)}} = V_{\text{rms}} \times I_{\text{rms}} = V_{CC} \times \frac{I_{C(\text{max})}}{2}$$

$$P_{P\text{ in (AC)}} = \frac{2V_{CC} \times I_{C(\text{max})}}{\pi}$$

$$\eta = \frac{V_{CC} \times I_C \times \pi}{2 \times 2 \times V_{CC} \times I_C} \Rightarrow \frac{\pi}{4} = 78.5\%$$

Class C Power Amp :-

Angle of conduction

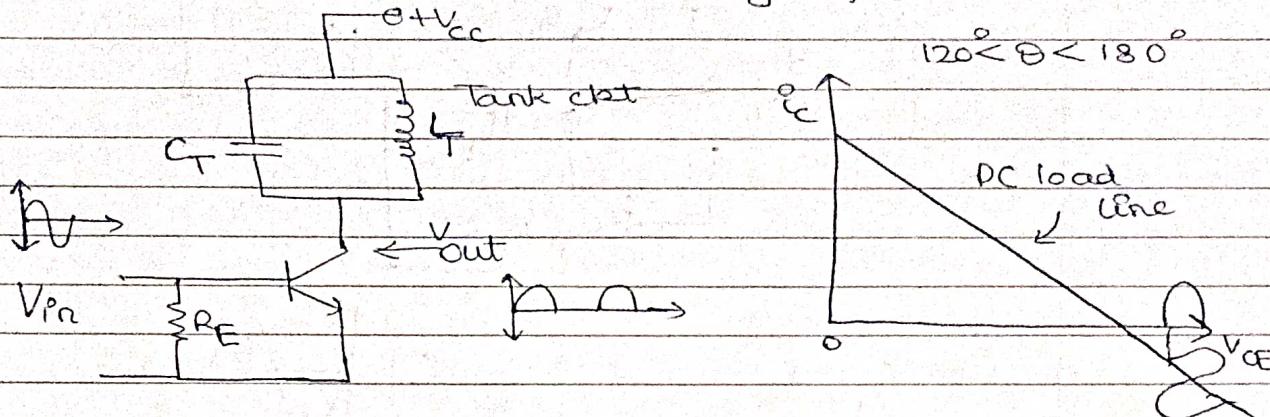

Class C amp^x is one in which the operating point is chosen so that Q/P current or voltage is 0 for more than one half of P/P sinusoidal signal. Its bandwidth is lesser than other amp^x. They are used for high freq operation. Their eff $> 90\%$, but they are heavily distorted hence not for audio amp^x.

- Advantage → High eff
- Excellent in RF Amplification
- Lowest physical size for power o/p

- Disadvantages → Lower efficiency
- Not used in audio apps
- Create a lot of RF interference.
- Difficult to obtain ideal inductor & capacitor for tank circ.

Multistage Amp :-

→ Freq Response of Amp :-

Distortions in Amp :- These result from the production of mixed freq due to freq not present in I/P but appear in O/P. They are also called Amplitude distortions.

Freq; distortions :- These dist. exist when similar component of diff freq amplify differently

Hedge shape distortion :- Result from unequal phase shift of different freq.

Fidelity of reproduction is one of criteria to compare one amp to other. Any signal can be broken into its respective Fourier spectrum. Let's take sinusoidal signal $v = V_m \sin(\omega t + \phi)$. If the voltage gain is A & signal suffer a phase change of θ° then O/P is

$$AV_m \sin\left(\omega t + \frac{\theta}{\omega}\right) + \phi$$

Hence if A is independent of freq at θ° is proportional to freq. then amp will preserve the form of I/P signal.

— / —

In an amp^x stage freq. state can be divided in 3 parts

- Middle Band freq. :- Having gain = 1
- Low Band freq. :- High pass filter
- Upper Band freq. :- Low pass filter

$$f_1 = \frac{1}{2\pi R_1 C_1}, f_2 = \frac{1}{2\pi R_2 C_2}$$

Band pass of Cascaded stages :-

The high 3 dB freq. of a cascaded stages is f_H^+ & equal the freq. for which overall voltage gain falls 3dB to $\frac{1}{\sqrt{2}}$ of its feedback value.

To obtain transfer func. the individual gain are multiplied,

$$\sqrt{\frac{1}{1 + \left(\frac{f_{H1}^+}{f_{H1}}\right)^2}} \times \sqrt{\frac{1}{1 + \left(\frac{f_{H2}^+}{f_{H1}}\right)^2}} \times \sqrt{\frac{1}{1 + \left(\frac{f_{H3}^+}{f_{H1}}\right)^2}} = \frac{1}{\sqrt{2}}$$

For n stages with identical upper 3 dB freq we have

$$f_{H1} = f_{H2} = f_{H3} = f_{Hn} = f_H$$
$$\sqrt{1 + \left(\frac{f_H^+}{f_H}\right)^2} = \frac{1}{\sqrt{2}}$$

— / —

Final response

$$\frac{f_H^*}{f_H} = \sqrt{2^n - 1}$$

↓ Individual response

For $n=2$, $\frac{f_H^*}{f_H} = 64$

Hence two cascade stage each with a bandwidth $10\text{kHz} = f_H$ has an overall bandwidth (cascade) of 640kHz . & f_L is 5.1kHz if $n=3$.


Hence we can conclude that by cascading diff stages the bandwidth gets reduced.

For Low 3dB freq. = f_L^*

$$\frac{f_L^*}{f_L} = \sqrt{\frac{1}{2^n - 1}}$$

Hence for cascade of ~~changes~~ stages a lower f_H & higher f_L results sharping in B.W.

RC coupled Amp :-

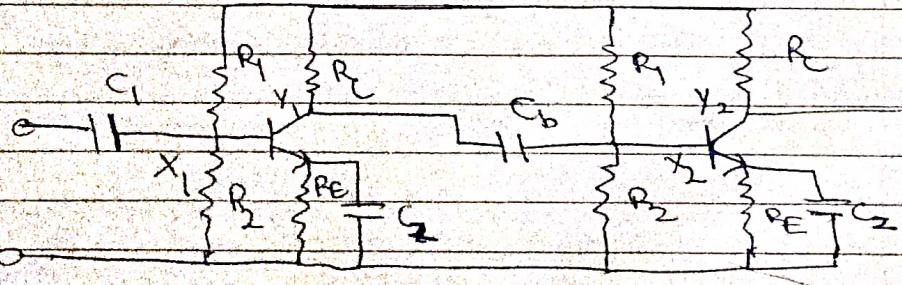


11

O/p of Y_1 of one stage is coupled to the i/p X_2 of next stage by a capacitor C_b which is used to keep DC component of o/p voltage at Y_1 from reaching the i/p X_2 .

Resistance R_E , R_1 , R_2 are used to bias the circuit whereas C_2 is bypass capacitor used to prevent the loss of amp. due to -ve feedback.

Hybrid π Model : (CE)

Transistor at high freq:-

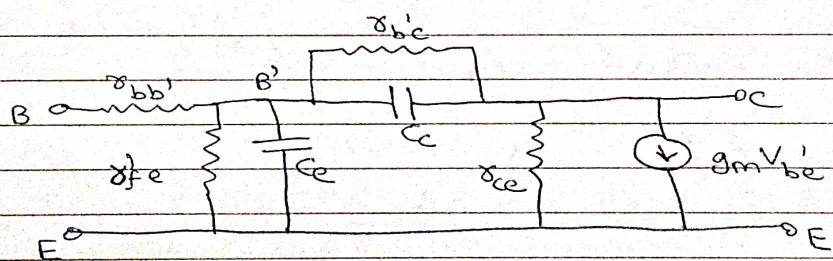

r_{bb}' → Base Spreading Resistance

r_{be} → Excess carrier conc.

r_{bc}' → early effect

C_c → overlap diode capacitance


C_e → Excess minority carrier

$g_m V_{be}'$ → V_{ccs}

$C_e \& C_c \downarrow$ \Rightarrow Hybrid Model.
 $R_{B'C} \uparrow$

— / —

Hybrid II Capacitance :-

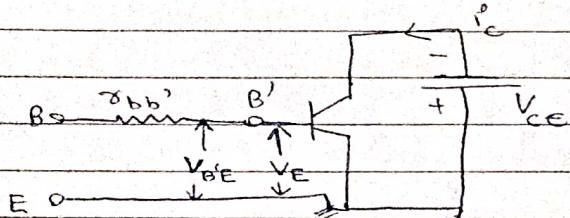

$$g_m = \frac{i_C^o}{V_{B'E}}$$

In active region i_C^o is given by $i_C^o = i_{CO} - g_o i_E$

$$\text{Hence } g_m = \frac{i_C^o}{V_{B'E}} = -g_o \frac{\partial i_E}{\partial V_{B'E}} = g_o \frac{\partial i_E}{\partial V_E}$$

For a PNP transistor, $V_E = -V_{B'E}$. If emitter resistance r_e then $r_e = \frac{\partial V_E}{\partial i_E}$

$$g_m = \frac{g_o}{r_e} \quad \text{Dynamic resistance of forward biased diode} = \frac{V_T}{i_C^o} = 26 \text{ mV}$$

$$g_m = \frac{g_o i_C^o}{V_T} = \frac{i_{CO} - i_C^o}{V_T} \quad \left\{ \begin{array}{l} g_m \text{ is always} \\ +ve \end{array} \right\}$$

and $i_{CO} \ll i_C^o$

$$g_m = \frac{i_C^o}{V_T} \quad \& \quad V_T = 26 \text{ mV}$$



g_m at room temp \Rightarrow

$$g_m = \frac{L i_C^o}{26} \text{ mA}$$

$$g_m \propto \frac{i_C^o}{V_T}$$

11

Input Conductance :- $\{g_{b'e}\}$

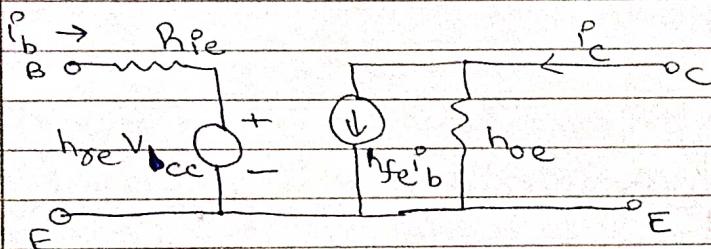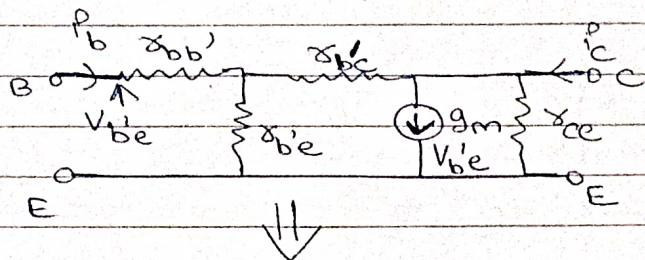

As we know,

$$r_{bc} \rightarrow r_{b'e}$$

Hence i_b will flow only in $r_{b'e}$, $V_{be} = i_b r_{b'e}$

Short ckt current $i_c = g_m V_{be}$

$$i_c = g_m i_b r_{b'e}$$

Shoot ckt current gain, $h_{fe} = \frac{i_c}{i_b}$

So, $h_{fe} = g_m r_{b'e}$

$$r_{b'e} = \frac{h_{fe}}{g_m}$$

$$r_{b'e} = \frac{h_{fe}}{|i_c|} V_T$$

— / —

$$g_{b'e} = \frac{1}{\gamma_{b'e}} = \frac{g_m}{h_{fe}} = \frac{|I_{c1}|}{V_T \times h_{fe}} = \frac{|I_{c1}| \text{ mA}}{26 \times h_{fe}}$$

$\gamma_{b'e} \propto T$ and $\propto \frac{1}{|I_{c1}|}$

With P/P open circuit h_{re} is defined as reverse voltage gain.

$$h_{re} = \frac{V_{be}}{V_{ce}} = \frac{\gamma_{be}}{\gamma_{be} + \gamma_{bc}}$$

$$\gamma_{be} (1 - h_{re}) = h_{re} \gamma_{bc}$$

As $h_{re} \ll 1$

As $h_{re} = 10^{-4}$

$$\gamma_{be} = h_{re} \gamma_{bc}$$

$\gamma_{bc} \gg \gamma_{be}$

$$g_{bc} = h_{re} g_{be}$$

Base spreading factor :-

P/P resistance with o/p shorted is h_{ie} . Under these conditions $\gamma_{be} \parallel \gamma_{bc} \approx \gamma_{be}$.

$$\text{Hence } h_{ie} = \gamma_{bb'} + \gamma_{be}$$

$\gamma_{bb'} = h_{ie} - \gamma_{be}$
 h_{ie} varies with temp & current as,

$$h_{ie} = \gamma_{bb'} + \frac{h_{fe} V_T}{|I_{c1}|} \Rightarrow h_{ie} = h_{fe} \frac{V_T}{|I_{c1}|}$$

11

I/P Conductance :-

With I/P open ckt this conductance is equal to h_{oe} . For $i_b = 0$ we have

$$I_c = \frac{V_{ce}}{\gamma_{ce}} + \frac{V_{ce}}{\gamma_{b'e} + \gamma_{b'e}} + g_m V_{b'e}$$

$$\text{with } i_b = 0 \Rightarrow V_{be} = h_{re} V_{ce}$$

$$h_{oe} = \frac{P}{V_{ce}} = g_{ce} + g_{bc}' + g_{b'e} \frac{h_{fe}}{g_{bc}'} - g_{bc}'$$

$$g_{ce} = h_{oe} - (1+h_{fe}) g_{bc}' \quad \text{if } h_{fe} \gg 1$$

$$g_{ce} = h_{oe} - g_m h_{re}$$

$$g_m = \frac{|I_c|}{V_T}, \quad \gamma_{be} = \frac{h_{fe} V_i}{|I_c|} \quad \text{or} \quad g_{be} = \frac{g_m}{h_{fe}}$$

$$\gamma_{bb'} = h_{re} - \gamma_{be}$$

$$\gamma_{bc} = \frac{\gamma_{be}}{h_{re}} \quad \text{or} \quad g_{bc}' = \frac{h_{oe}}{\gamma_{be}}$$

$$g_e = h_{oe} - (1+h_{fe}) g_{bc}' = \frac{1}{\gamma_{ce}}$$

— / —

Hybrid π Capacitance :-

- Collector junction capacitance :- This is measured C_{CB} o/p capacitance with Q/P open circuit i.e. $I_C = 0$. It is denoted by C_{CJ} by manufacturers.

$$C_c = C_{CJ} e$$

The capacitance C_c depends on $V_{CB}^{-n} \propto C_c$ where
 $n = 1$ for abrupt junction.
 $n = \frac{2}{3}$ for gradient junction.


$$C_c = C_{DE} + C_{TE} \approx C_{DE}$$

$\downarrow \quad \downarrow$
Emitter Emitter
Diffusion Junction.

$C_{DE} \gg C_{TE}$

C_{DE} & I_c & independent on temp.

Diffusion Capacitance :-

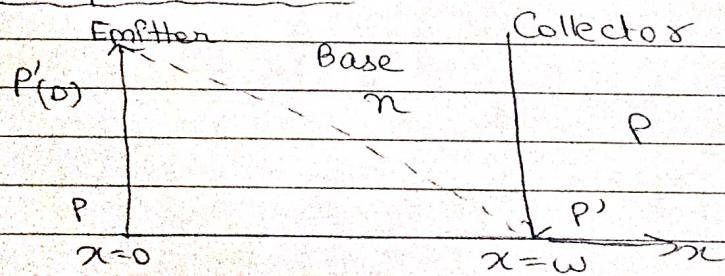

- Consider a p-n-p transistor base width w assume to be very small than diffusion length L_B of minority carrier.

11

Injected charge conc. p' at collector is 0
If $w < L_B$ then p' varies almost linearly
from $p'_{(0)}$ at emitter func to 0 ~~at~~ collector
func. Hence stored base charge Q_B

$Q_B = \frac{1}{2} p'_{(0)} A w q$ ~~where~~ Now the diffusion
current is given as

$$I = -A q D_B \frac{dp'}{dx} = A q D_B \frac{p'(0)}{w}$$

D_B = diffusion constant.

$$Q_B = \frac{i w^2}{2 D_B}$$

$$\text{Now setting } C_{DE} = \frac{dQ_B}{dV} = \frac{w^2}{2 D_B} \frac{dt}{dx}$$
$$= \frac{w^2}{2 D_B} \frac{1}{x_e}$$

$$\text{Again } x_e = \frac{V}{|I_{C0}|}$$

$$C_{DE} = \frac{w^2 I_e}{2 D_B V_T} = g_m \frac{w^2}{2 D_B}$$

-/-

which indicates that C_{DB} or emitter current i_e^o

$$\text{So, } G_e = \frac{g_m}{2\pi f_T}$$

$f_T = f_{req}$ at which CE short circuit gain drops to unity.

	$ I_{C1}^o $	$ V_{CE} $	T
g_m	$ I_{C1}^o $	Independent	$\frac{1}{T}$
τ_{bb}^o	Decrease	—	Increase
$\frac{\partial I}{\partial V_{BE}}$	$\frac{i}{ I_{C1}^o }$	Increase	$\frac{T}{2}$ Decrease
C_e	$ I_{C1}^o $	Decrease	—
C_c	Independent	Decrease	Independent
h_{FE}	—	Increase	Increase
h_{RE}^o	$\frac{P}{ I_{C1}^o }$	Increase	Increase

Gain Bandwidth Product :- The GBP for Voltage & Current for simplified hybrid π model load R_L & P/P impedance $\{R_s + \tau_{bb}^o\}$ given by,

$$A_v = \frac{g_m}{2\pi C} \frac{R_L}{R_s + \tau_{bb}^o} = \frac{f}{f_T} \frac{1}{1 + 2\pi f_T C R_s} \frac{R_L}{R_s + \tau_{bb}^o}$$

— 11 —

$$A_f = \left(\frac{f_T}{1 + 2\pi f_T C_{RL}} \right) \left(\frac{R_s}{R_s + s_{bb}} \right)$$

The voltage gain is 0 if all R_s is ∞ & band width is highest for lowest R_s .

Voltage gain Bandwidth Product increase with R_s & decreases with R_L .

If any one changes the gain also changes generally gain bandwidth product will no longer stay same as it had been.