
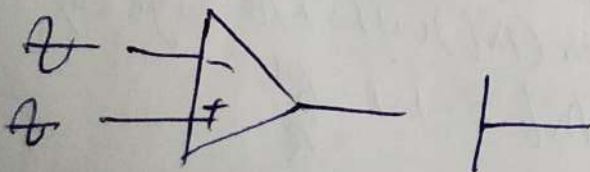
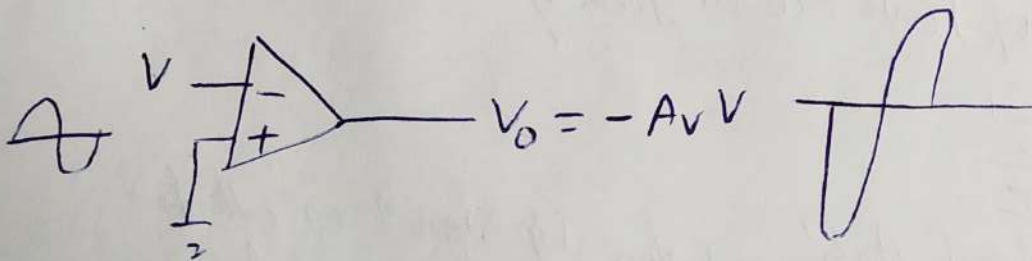
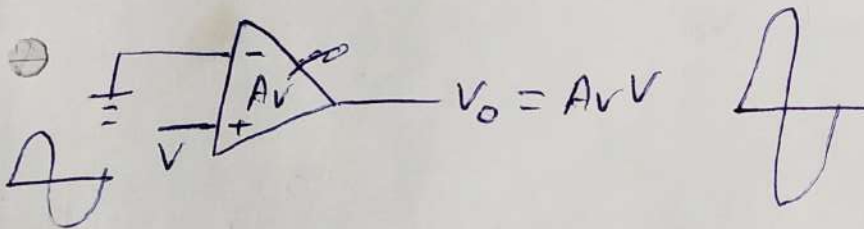


Operational Amplifiers (OP-Amp)

Introduction

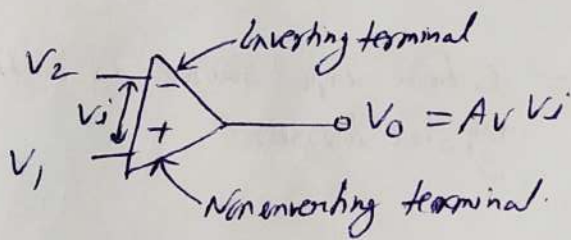
- An operational Amp^x or OP-Amp is a high gain direct coupled electronic voltage amp^x, having differential input and usually a single ended o/p.
- Having different advantages like small size, high reliability, predictably lower cost, temp. tracking and low offset volt. and current.



Ideal characteristics

- Input Resistance $R_i = \infty$
- O/P Resistance $R_o = 0$
- VOLT. gain $A_v = -\infty$
- Bandwidth $BW = \infty$
- $V_o = 0$ when $V_1 = V_2$ independent of magnitude of V_1 .
- Characteristic do not drift with temp.
- Having CMRR - Common mode Rejection Ratio $= \infty$
- Slew rate $= \infty$.

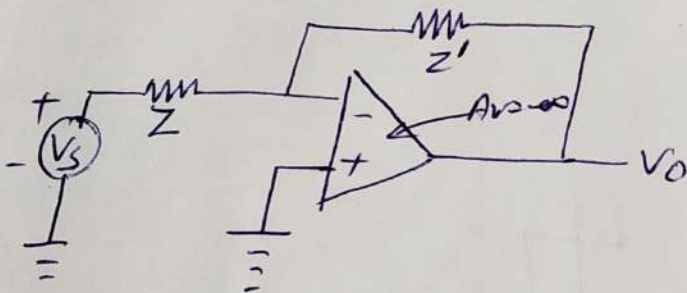
Inverting operational Amp^r :- When input source is with negative terminal.



Voltage gain (A_{vf}) with FIB is given by

$$A_{vf} = -\frac{Z'}{Z}$$

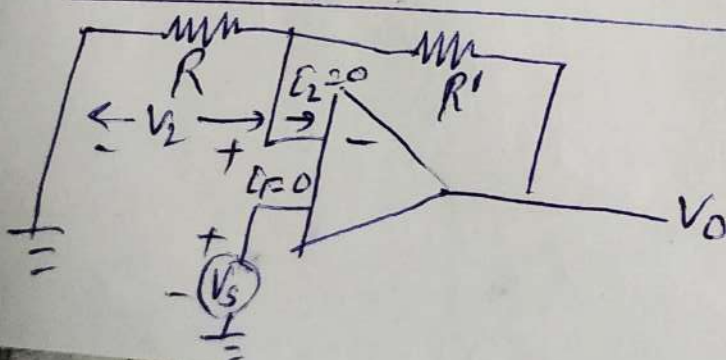Non Inverting operational Amp^r :- When i/p signal is attached with +ve terminal.



VOLT. gain (A_{vf}) with FIB is given by.

$$A_{vf} = 1 + \frac{R'}{R}$$

The Differential Amp

- This amp^r is used to amplify difference between two signals.


$$V_o = A_d (V_1 - V_2) \quad \text{--- (I)}$$

A_d — Gain of the differential amp^r

- In differential amp^r o/p is not only depending upon eq(I) but also upon the average level, called common-mode signal V_c .

$$V_d = V_1 - V_2 \text{ and } V_c = \frac{1}{2}(V_1 + V_2) \quad \text{--- (II)}$$

Common Mode Rejection Ratio (CMRR):

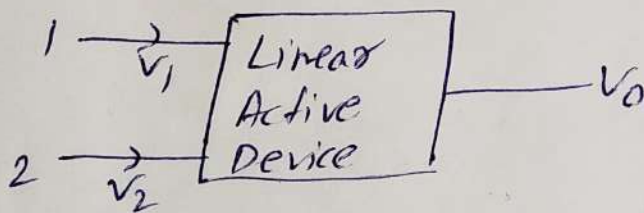

$$V_o = A_1 V_1 + A_2 V_2 \quad \text{--- (III)}$$

where A_1 is voltage amplification from i/p 1 when i/p 2 is grounded.

A_2 is vlt amp^m for i/p 2 when i/p 1 is grounded.

From eq (III) we have

$$V_1 = V_c + \frac{1}{2} V_d \text{ and } V_2 = V_c - \frac{1}{2} V_d \quad \text{--- (IV)}$$

Putting (IV) in (III) we have

$$V_o = A_d V_d + A_c V_c; \text{ where } A_d = \frac{1}{2}(A_1 - A_2) \text{ \& } A_c = A_1 + A_2 \quad \text{--- (V)}$$

- Ideally A_d should large & A_c should zero.
- CMRR $\rho = \left| \frac{A_d}{A_c} \right|$ ——— (VI)

from eqn (IV) & (V) we have.

$$\boxed{V_o = A_d V_d \left(1 + \frac{1}{\rho} \frac{V_c}{V_d} \right)} \text{ ——— (VII)}$$

- CMRR reflects the merit of differential amp.

The Emitter - Coupled Differential Amplifier

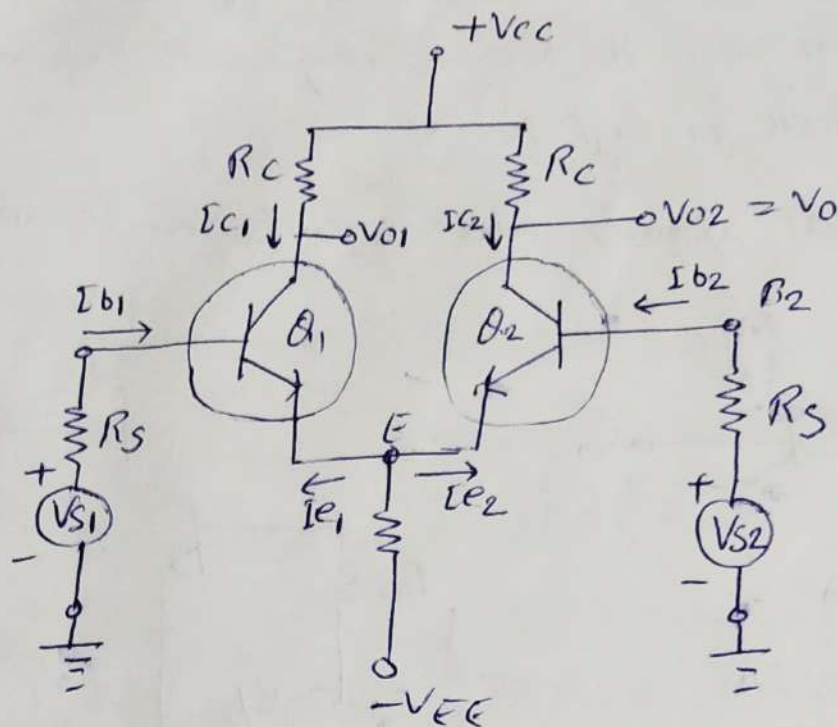


Fig. 1 - Symmetrical Emitter coupled difference amp^r.

The above figure shows emitter coupled difference amp^r, having two different but similar transistors Q_1 & Q_2 connected through emitter. Input signal in terms of voltage are fed through base of both transistors.

- The circuit can be used as a difference amp^r if and only if emitter resistance R_E should be very high.

- Consider $V_{S1} = V_{S2} = V_S$ then $V_d = V_{S1} - V_{S2} = 0$ and $V_O = A_C V_d \approx A_C V_S$

- If $R_e = \infty$ then $I_e = 0$, hence $I_{C1} = I_{C2} = 0$. Now if $V_{B2} \ll V_{C2}$ then $V_{C2} \approx V_{E2}$ and it follows $V_O \approx 0$. Hence common mode gain A_C becomes very small and resulting a high CMRR for high R_e .

- Now due to symmetry above circuit can be broken up as follows

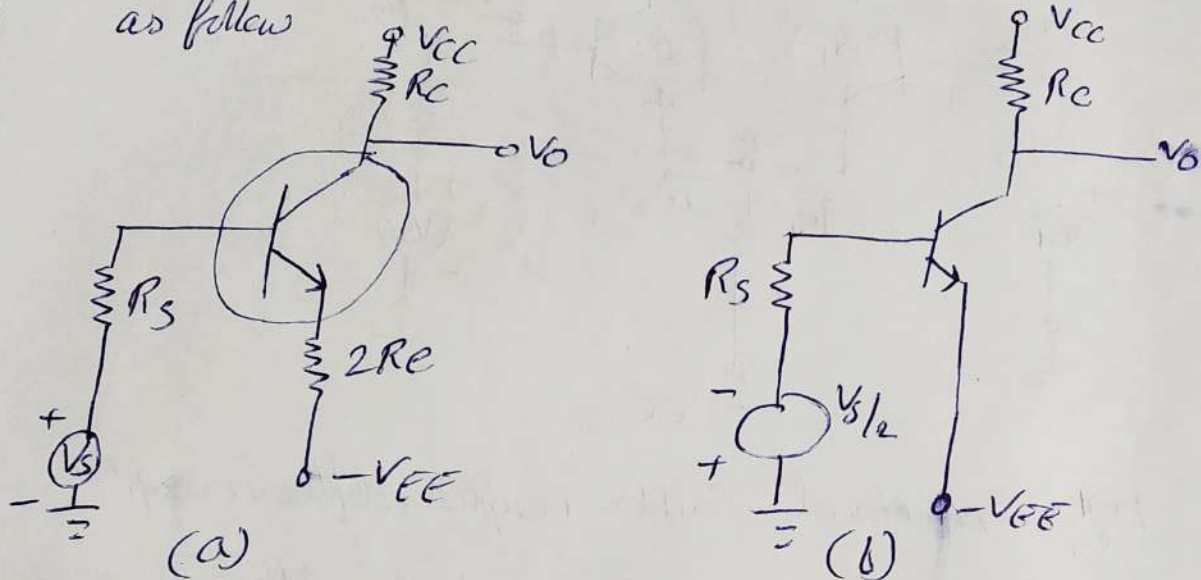


Fig. Equivalent circuit for a symmetrical differential amp for determining
(a) The common mode gain A_C (b) difference gain A_d .

$$\text{Now } A_C = \frac{V_O}{V_S} = \frac{(2h_{oe}R_e - h_{fe})R_C}{2R_e(1+h_{fe}) + (R_S+h_{ie})(2h_{oe}R_e+1)} \quad \text{--- (VII)}$$

(neglecting h_{oe} and
considering $h_{oe}R_e \ll 1$).

Setting $V_{S1} = -V_{S2} = V_S/2$, from fig 1 we have if $V_{S1} = -V_{S2}$ then $I_{C1} = -I_{C2}$, drop across R_e is zero and E is grounded for small-signal operation.

Hence diffn gain A_d throught Fig 2(b) can be given by.

$$A_d = \frac{V_o}{V_s} = \frac{1}{2} \frac{h_{fe} R_c}{R_s + h_{ie}} \quad \text{--- (IX) (provided } h_{oe} R_c \ll 1)$$

- Again if operating current of transistors are allowed to decrease, results higher h_{ie} & lower h_{fe} and finally decreases CMRR.
- To maintain Q point at the proper point on load line, if R_c got increased than at the same time V_{EE} must become larger, hence Q point can't be shifted.

⇒ Differential Amp^r Supplied with a Constant Current

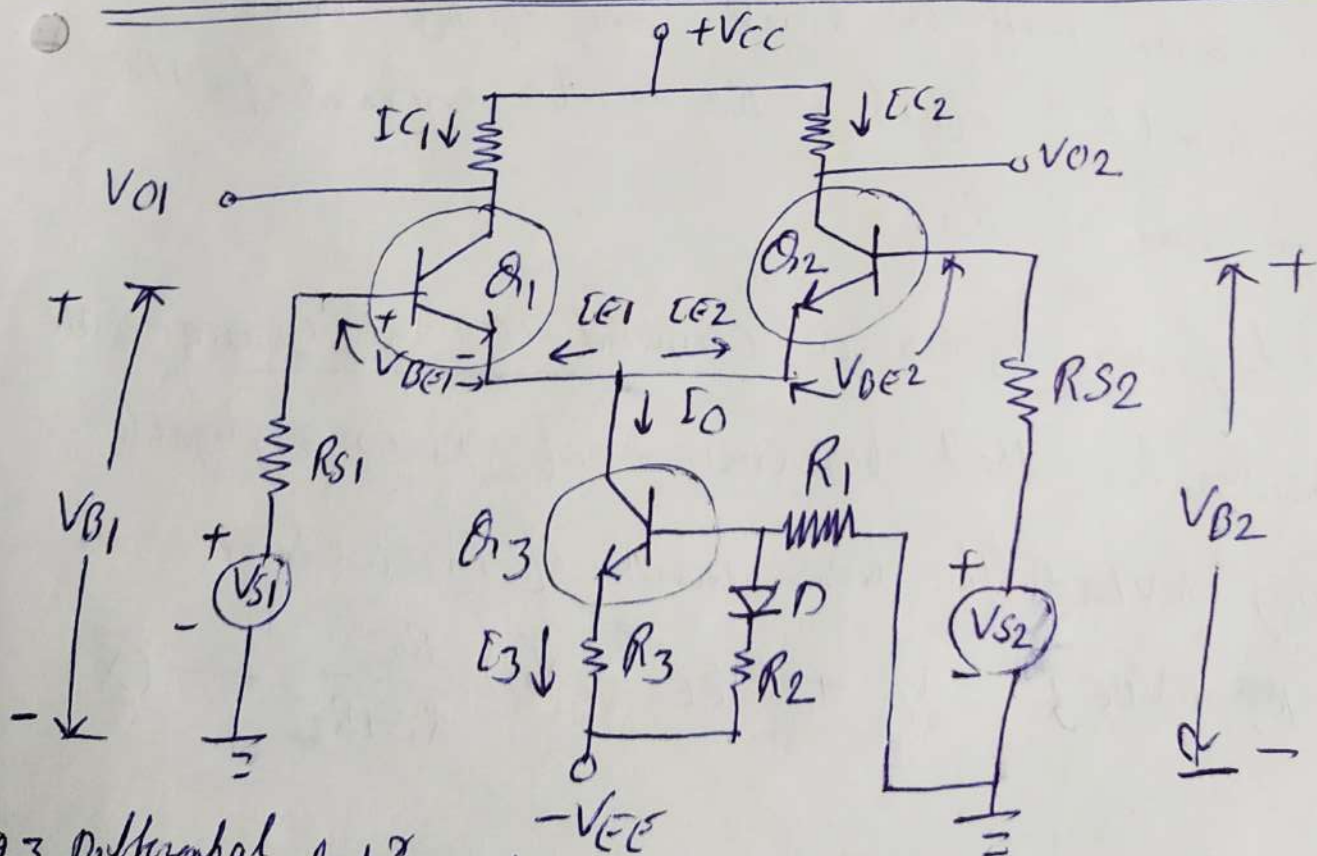


Fig 3 Differential Amp^r with constant current stage in emitter circuit.

- As we know for an ideal OP-Amp CMRR should be ∞ , for the same A_c (common mode gain) should be minimum, eg as $CMRR = \left| \frac{A_d}{A_c} \right|$. Now for the previous discussion we found that higher the value of R_e reflects lower A_c and hence finally higher CMRR.

- In this continuation 'Re' is generally replaced by a transistor circuit as shown in Fig 3.

- In the Fig 3 R_1, R_2 and R_3 are adjusted in such a fashion that the same quiescent condition for Q_1 & Q_2 as the original circuit is obtained.

- Due to operation of circuit overall 'Re' shows a higher value for Q_1 & Q_2 with a small value of R_3 . Hence it can be concluded that effectively Re can be increased for the lesser value of R_3 .

- Now to fix Q_3 as a constant current source with a consideration that base current of Q_3 is negligible. Applying KVL to the base circuit of Q_3 we have

$$I_3 R_3 + V_{BE3} = V_D + (V_{EE} - V_D) \frac{R_2}{R_1 + R_2} \quad \text{--- (X)}$$

Where $V_D \rightarrow$ diode volt.

Hence, $I_0 \approx I_3 = \frac{1}{R_3} \left(\frac{V_{BE} R_2}{R_1 + R_2} + \frac{V_D R_1}{R_1 + R_2} - V_{BE3} \right)$ — (X1)

If the circuit parameters are chosen such that

$$\frac{V_D R_1}{R_1 + R_2} = V_{BE3}$$

then $I_0 = \frac{V_{BE} R_2}{R_3 (R_1 + R_2)}$ — (X11)

— Now current I_0 is independent of signal voltages V_{S1} & V_{S2} than Q_3 acts to supply the difference Amp^r consisting of Q_1 & Q_2 with constant current I_0 .

— Due to diode D, I_0 is independent of temp. change, ~~in~~ due to the absence of D, V_{BE3} decreases approximately $2.5 \text{ mV}/^\circ\text{C}$ and hence a effective change in I_0 can be reflected. Hence diode make eqn X11 to be as a const. current source.

— Also $\frac{R_1}{R_1 + R_2}$ is chosen experimentally so that I_0 (ineqn X11) is almost independent of T.

— As under the above condition $A_c = 0$. Assume that $V_{S1} = V_{S2} = V_S$. So due to symmetry of circuit $I_{C1} = I_{C2}$ and $I_{C1} + I_{C2} = 0$ if $I_0 = \text{const}$, also $I_{C1} = I_{C2} = 0$ and $A_c = V_{O2}/V_S = -I_{C2} R_c / V_S \approx 0$.

Practical Considerations

- Differential amp^s are often used as in DE application. As it is known fact that β_{FE} , V_{BE} & τ_{CB} are temp. dependent quantity. So a little change in characteristics can effectively change the overall behaviour. Hence it is required to construct a difference amp^s with Q_1 & Q_2 having almost identical characteristics. Hence effective change in any one parameter of one transistor can be countered by the other one.
- Differential amp^s can be cascaded to obtain larger amplification for the difference signal.
- The differential amp^s may be used as an emitter-coupled phase inverter. For this one base is excited whereas other is not. The o/p volt from collectors are equal in magnitude and 180° out of phase.

Practical Considerations

- Differential amp^s are often used as a diff. application. As it is known fact that β_{FE} , V_{BE} & τ_{CB} are temp. dependent quantity. So a little change in characteristics can effectively change the overall behaviour. Hence it is required to construct a difference amp^s with Q_1 & Q_2 having almost identical characteristics. Hence effective change in any one parameter of one transistor can be countered by the other one.
- Differential amp^s can be cascaded to obtain larger amplification for the difference signal.
- The differential amp^s may be used as an emitter-coupled phase inverter. For this one base is excited whereas other is not. The o/p volt from collectors are equal in magnitude and 180° out of phase.

Transfer characteristics of a Differential Ampⁿ

- This is graph between I_C & $V_{B1} - V_{B2}$ or normalized value of both i.e. I_C/I_0 and $V_{B1} - V_{B2}/V_T$
- Consider Fig 3, when $V_{B1} < V_{B1 \text{ cutoff}}$ then Q_1 would be OFF and all the current I_0 will flow through Q_2 for V_{B1} .
- As V_{B1} increases than cutoff value then Q_1 will conduct and flow of current through Q_2 will decrease, but the overall sum up current will be I_0 .
- The total range of volt. for which the conduction take place may be denoted by $\Delta V_0 = R_C I_0$, can be adjusted through an adjustment of I_0 .

- now from Fig 3

$$I_{E1} + I_{E2} = -I_0$$

$$V_{B1} - V_{B2} = V_{BE1} - V_{BE2}$$

} - (XIII)

- Now $I_E = I_S e^{V_{BE}/V_T}$ — (XIV)

where I_S — Term of Ebers-Moll parameters.

- If Q_1 & Q_2 are matched then from (XIII) & (XIV)

$$I_{C2} - I_{E1} = \frac{I_0}{1 + \exp[-(V_{B1} - V_{B2})/V_T]} \quad \text{--- (XV)}$$

$$\text{Also } I_{C2} = -I_{C1} = \frac{I_0}{1 + \exp[-(V_{B2} - V_{B1})/V_T]} \quad \text{--- (XVI)}$$

So in graph (XV) & (XVI) can be shown as

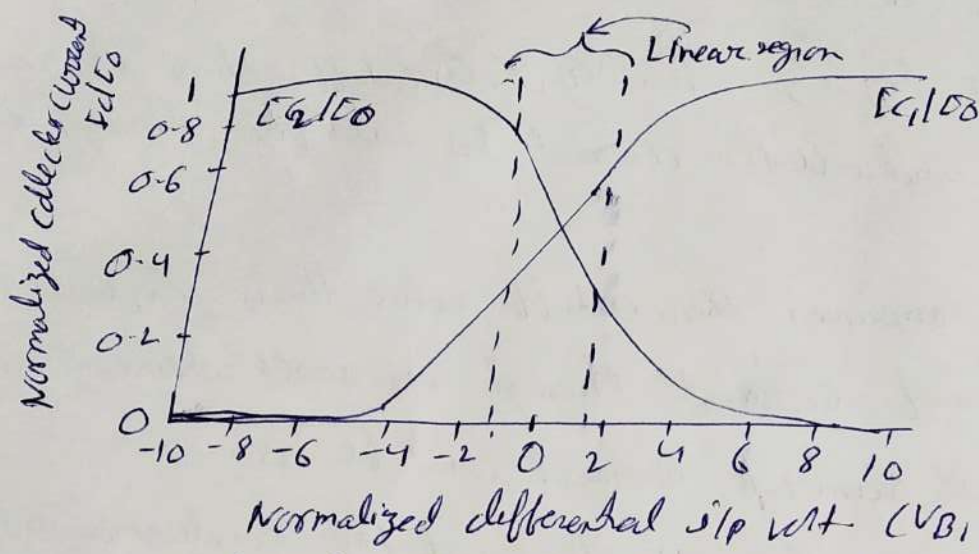


Fig 1:- Transfer characteristic of basic differential amp^r ckt.

Now differentiate (XVI) w.r.t $V_{B1} - V_{B2}$ we get transconductance g_{md} of the differential amp^r.

$$\frac{dI_{C1}}{d(V_{B1} - V_{B2})} = g_{md} = \frac{I_0}{4V_T} \quad \text{--- (XVII)}$$

where g_{md} is evaluated at $V_{B1} = V_{B2}$. From (XVII) we can conclude that for same value of I_0 the effective transconductance of differential amp^r is one forth that of a single transistor.