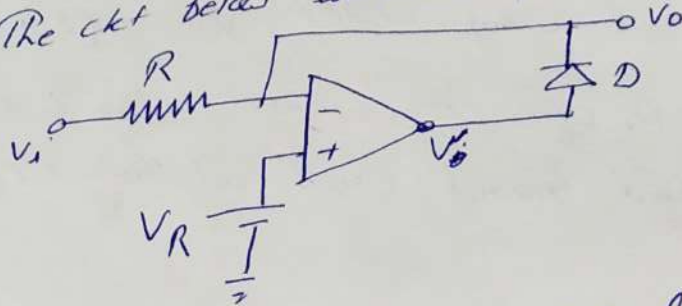


## Precision clamp

The ckt below illustrate precision clamp ckt.



- If  $V_i < V_R$  then  $V'$  is +ve and D conduct and

$$V_o = V_R$$

- If  $V_i > V_R$  then  $V'$  is -ve and D is OFF then

$$V_o = V_i$$

- Hence the o/p follows the i/p for  $V_i > V_R$  and  $V_o$  is clamped to  $V_R$  if  $V_i < V_R$  by about 0.1 mV.

## Fast Half-wave Rectifier

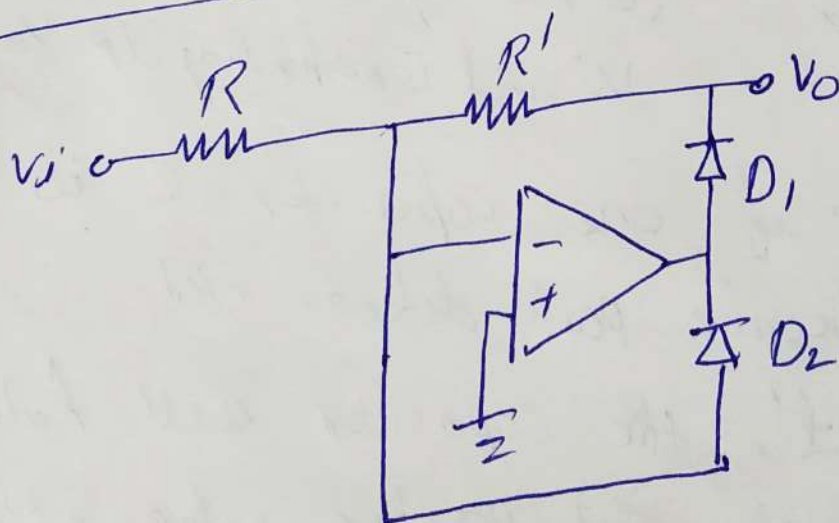


Fig:- A half wave Rectifier

- The fast half wave rectifier is shown above.
- For  $v_i$  to be  $-ve$   $D_1$  conduct and  $D_2 = OFF$  and ckt behaves as an inverting OPAMP,  $V_o = -(R'/R)v_i$ .
- For  $v_i$  to be  $+ve$   $D_1$  OFF  $D_2$  CONDUCT, due to FFB through  $D_2$  a virtual ground exists at the i/p and  $V_o = 0$ .
- A rectification upto 100MHz is possible.

### Active Peak Detector


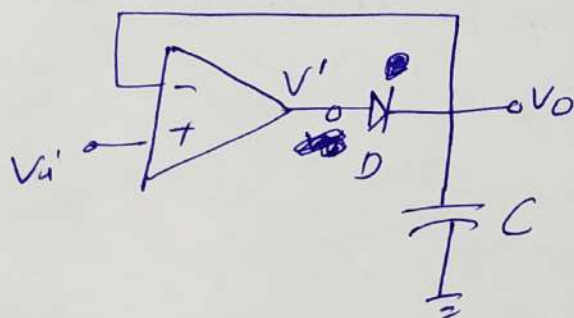


Fig a) +ve peak detector

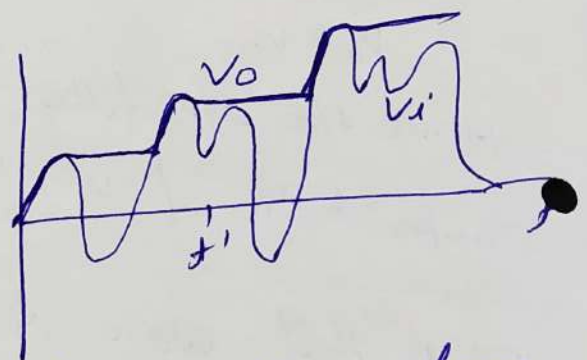

(v) Arbitrary i/p waveforms  $v_i$  and corresponding op  $V_o$ .

- In the Precision diode if one capacitor  $C$  is added then the circuit became peak detector ckt.
- Consider the point at  $t'$ , the capacitor will hold the O/P at  $t = t'$  to the most positive value attained by the i/p  $v_i$  prior to  $t'$ .



- The ckt is a voltage follower ckt and also can be consider to a special case of sample and hold ckt
- if  $V_i > V_o$ , OPAMP o/p  $V_o = +ve$  and D conducts. The capacitor C is charged through D by the O/P current of amp<sup>r</sup>.
- As  $V_i$  falls below capacitor volt, the OPAMP got -ve and diode become reverse biased. Thus the capacitor gets charged to the most +ve value of the i/p. Hence called peak detector.

## Logarithmic Amplifiers


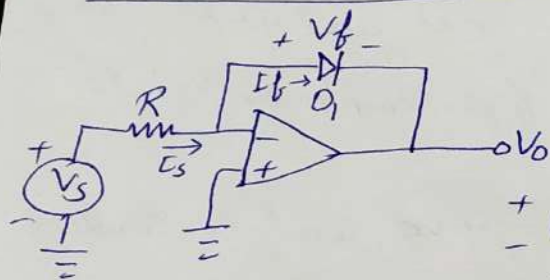


Fig (a) Logarithmic Amp<sup>r</sup>

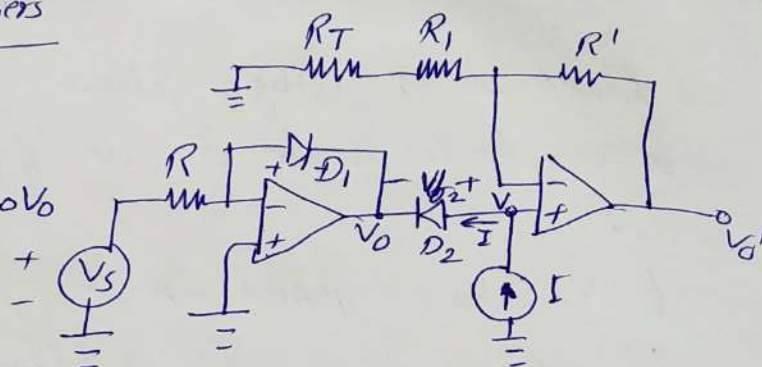

(b) Temp. - Compensated Amp<sup>r</sup>

- In the logarithmic amp<sup>r</sup>, feedback resistor  $R$  is replaced by diode  $D_1$  and also it gives logarithmic value of i/p volt at the o/p volt.

- Now as we know, volt-amp. diode characteristic

$$I_f = I_0 (e^{V_f / \eta V_T} - 1) \approx I_0 e^{V_f / \eta V_T}$$

$$\text{also, } V_f / \eta V_T \gg 1 \text{ or } I_f \gg I_0$$

$$\text{Hence } V_f = \eta V_T (\ln I_f - \ln I_0) \quad \text{--- (1)}$$

Now due to virtual ground at the amp<sup>r</sup> i/p we have

$$V_o = -V_f = -\eta V_T \left( \ln \frac{V_s}{R} - \ln I_0 \right) \quad \text{--- (2)}$$

$I_f = I_s = V_s / R$

Now eq<sup>n</sup> (2) reflects  $V_o$  is temp. dependent due to scale factor  $\eta V_T$  and also due to saturation current  $I_0$ . This effect can be reduced by Fig (b) arrangement.



From Fig (1) and from eq (11) we have

$$V = V_{f2} + V_0$$

$$= \eta V_T (\ln I - \ln I_0 - \ln \frac{V_0}{R} + \ln I_0) - \eta V_T \ln \frac{V_S}{R_I}$$


(11)

Thus o/p volt  $V_0'$  becomes

$$V_0' = - \frac{R_T + R_I + R'}{R_I + R_T} \eta V_T \ln \frac{V_S}{R_I} \quad (12)$$

Hence in eq (12)  $R_T$  will be selected in accordance to compensate the effect of  $\eta V_T$ .
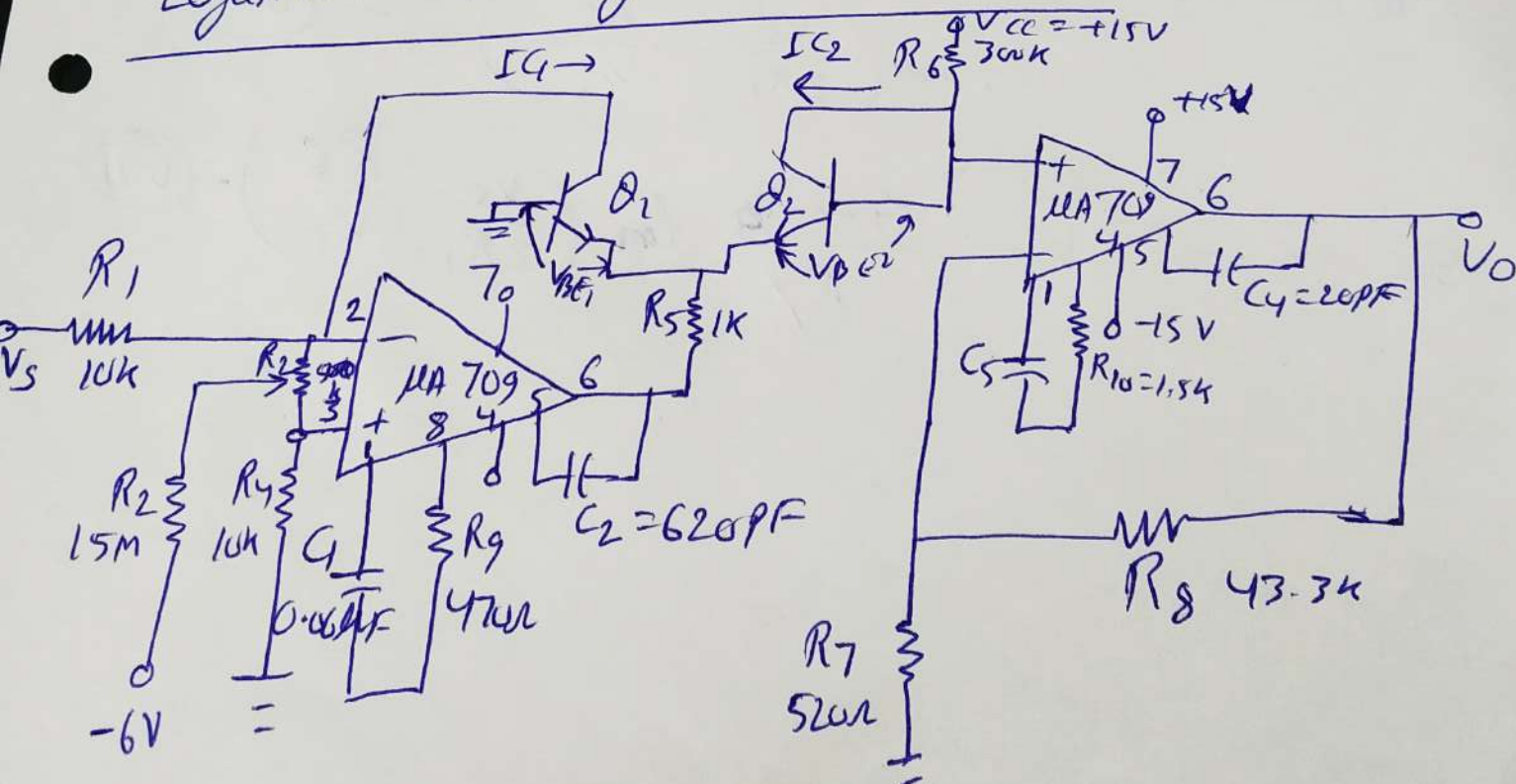
### Logarithmic Amp<sup>r</sup> using Matched Transistor



### Logarithmic Amp<sup>r</sup> using Transistor

- In the previous equation of  $V_O'$ , term  $\eta$  was present, whose value depends on the current flowing through diode. To get rid of that term matched transistor pair are used.

-  $Q_1$  is FIB amp<sup>r</sup> and  $Q_2$  acts as temp. compensator.

- If we neglect  $V_{BE1} - V_{BE2}$  wr.t to  $V_{CC}$  and as  $I_{C2} \ll I_{C1}$  then

$$I_{C2} \approx \frac{V_{CC}}{R_6} \quad \text{and} \quad I_{C1} = \frac{V_S}{R_1 + R_4} \approx \frac{V_S}{2R_1} \quad \text{--- (V)}$$

Now as we know

$$\begin{aligned} V_{BE1} - V_{BE2} &= V_T \ln I_{C1} - V_T \ln I_{C2} \\ &= V_T \ln \left( \frac{V_S}{2R_1} \cdot \frac{R_6}{V_{CC}} \right) \quad \text{--- (VI)} \end{aligned}$$

$$\text{So } V_O = -V_T \frac{R_1 + R_6}{R_7} \ln \left( \frac{V_S}{2R_1} \cdot \frac{R_6}{V_{CC}} \right) \quad \text{--- (VII)}$$



## Antilog Amplifier

Mod 4 (16)

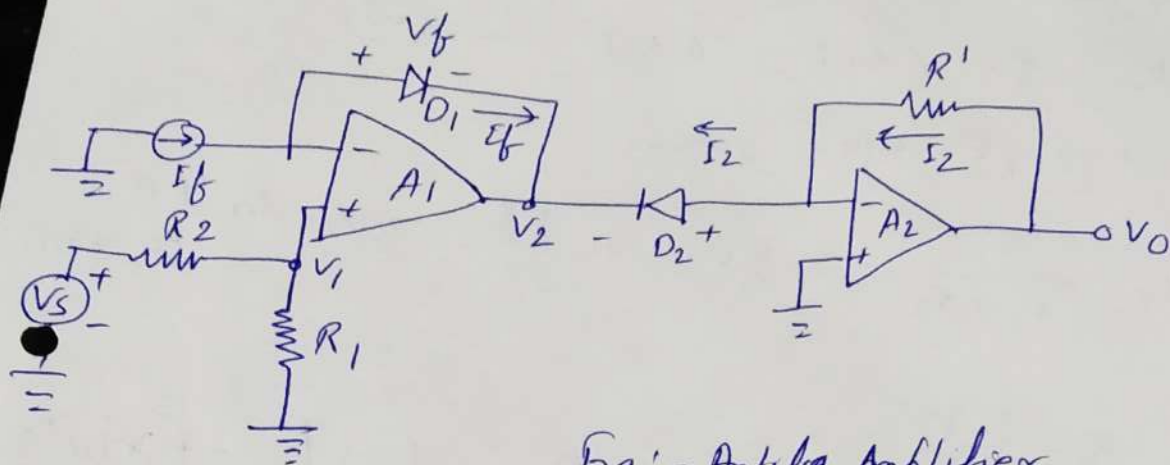


Fig:- Antilog Amplifier.

- The above diagram shows the circuit with OPAMP for antilog amplification.

• In the antilog amp<sup>r</sup> we can find antilog of i/p  $V_i$  signal at the O/p as  $V_o$ .

- In logarithmic amp<sup>r</sup>  $V_o \propto (\ln) V_i$  or  $V_o = k_1 \ln k_2 V_i$  — (viii)

-  $V_o = k_3 \ln^{-1} k_4 V_i$  or  $V_o \propto (\ln^{-1}) V_i$  — (ix)

Consider infinite i/p resistance for  $A_1$  &  $A_2$  as well as zero differential i/p volt. for each OPAMP we have

$$V_2 = -V_f + V_1 = \eta V_T (\ln I_f - \ln I_o) + \frac{R_1}{R_1 + R_2} V_s \quad \text{--- (x)}$$

As  $V_2$  is the negative of voltage across  $D_2$

$$V_2 = -\eta V_T (\ln I_2 - \ln I_0) \quad \text{--- (X)} \quad \text{--- (XI)}$$

Combining (X) & (XI) yields.

$$V_S \frac{R_1}{R_1 + R_2} = \eta V_T \ln \frac{I_f}{I_2} = \eta V_T \ln \frac{I_f R'}{V_0} \quad \text{--- (XII)}$$

as  $V_0 = I_2 R'$

$$V_0 = R' I_f \ln^{-1} \left[ -V_S \left( \frac{R_1}{R_1 + R_2} \frac{1}{\eta V_T} \right) \right] \quad \text{--- (XIII)}$$

## Logarithmic Multipliers

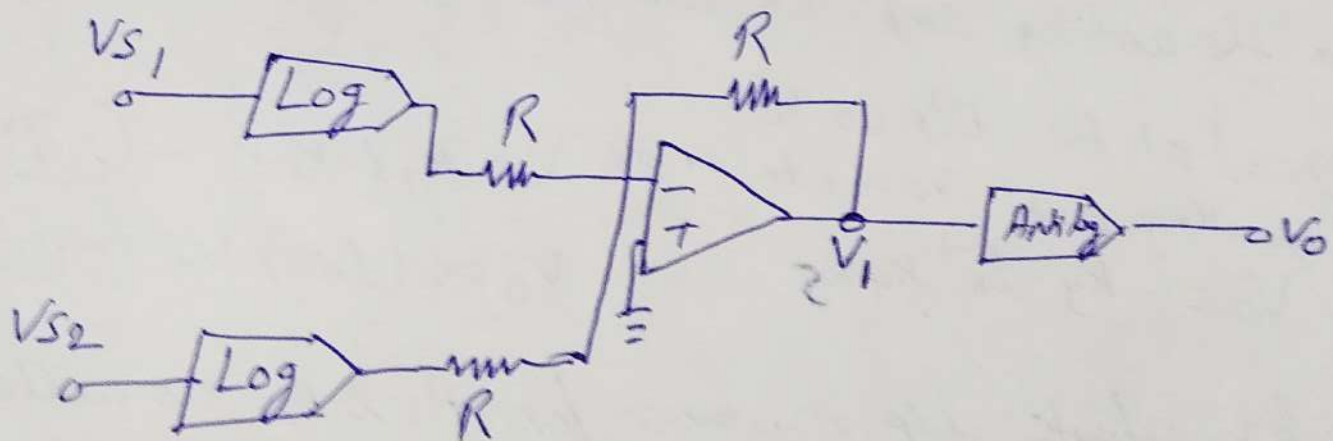


Fig Logarithmic multiplier of two signal  $V_{S1}$  &  $V_{S2}$

The log and anti-log can be used for multiplication or division of two analog signal  $V_{S1}$  &  $V_{S2}$ .



$$\begin{aligned} \text{Now } V_1 &= K_1 \ln V_{S1} + K_1 \ln V_{S2} \\ &= K_1 \ln V_{S1} V_{S2} \quad \text{--- (XN)} \end{aligned}$$

$$\begin{aligned} \text{and } V_0 &= K_2 \ln^{-1} K_3 V_1 \\ &= K_2 \ln^{-1} (K_3 K_1 \ln V_{S1} V_{S2}) \quad \text{--- (XV)} \end{aligned}$$

If  $K_3 K_1 = 1$  then

$$V_0 = K_2 V_{S1} V_{S2} \quad \text{--- (XVI)}$$

— For the division operation subtraction of  $\log V_{S1}$  from  $\log V_{S2}$  to be done and then antilog to be performed.

— Logarithmic multiplication & or division is useful for unipolar inputs only. Hence it is called as one-quadrant operation.

## Differential Amplifier Multiplier

— As we know o/p volt. of a differential amp<sup>r</sup> depends on source current  $I$ .

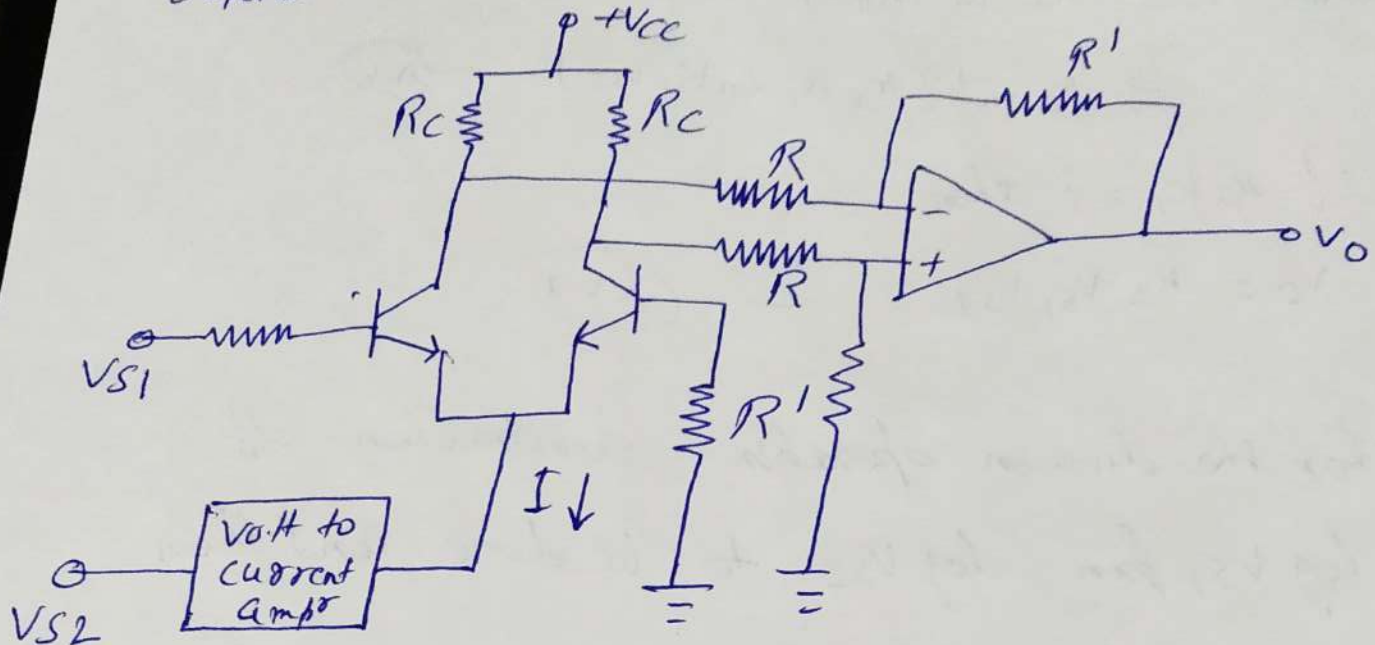



Fig: — Variable transconductance multiplier  
( $V_O = k V_{S1} V_{S2}$ )

— If  $V_{S1}$  is applied to one i/p and  $V_{S2}$  is used to vary  $I$  as shown above, the o/p will be proportional to the product of two signals  $V_{S1} V_{S2}$ .



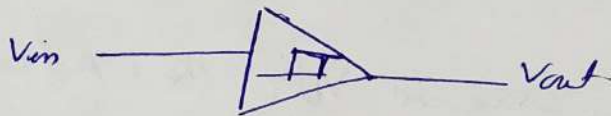
## Regenerative Comparator (Schmitt Trigger)

- General comparator is not very much immune to the noise and the o/p get effected due to it. Hence Schmitt trigger is introduced. It is also known as comparator with hysteresis.



- It is also known as squaring circuit as it is use to convert any regular or irregular shaped i/p waveform into a square wave o/p volt or pulse.
  - They are also called as regenerative comparators, due to the fact that they change their o/p state when i/p signal crosses predetermined switching levels.
  - Schmitt trigger generally contain two levels namely upper limit and lower limit, and any prachle graph or volt having random behaviour can be represented by these two levels.
- In the upcoming graph one i/p signal (random volt) is shown and two threshold level namely Lower threshold ( $V_{LT}$ ) and upper threshold ( $V_{UT}$ ) is shown.

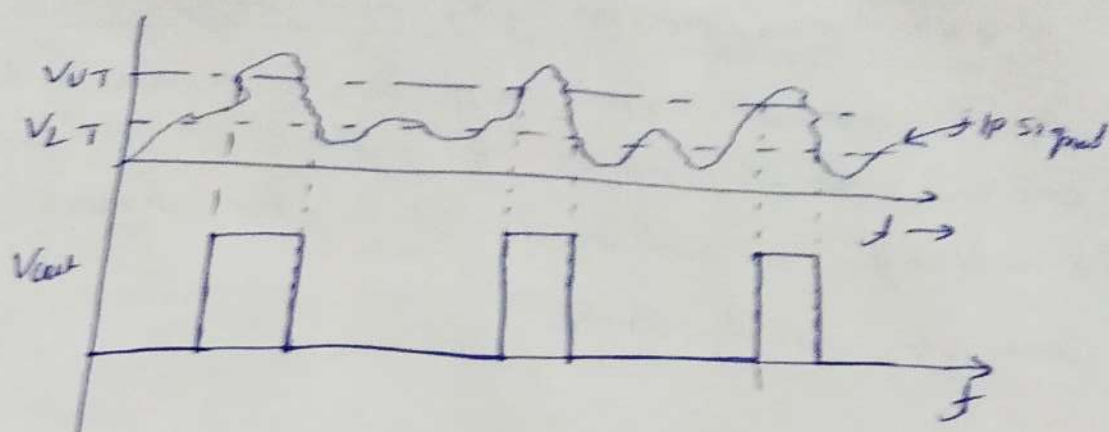

— Now as i/p signal crosses the  $V_{UT}$  the o/p from shows a upper rectangular peak and it remains in that state till the i/p signal drop below to  $V_{LT}$ . Similarly a rectangular lower pulse is indicated for the same. And as the i/p signal again cross the upper threshold ( $V_{UT}$ ) the graph goes to upper threshold till it again drop below to lower level ( $V_{LT}$ ).

— The volt. between  $V_{LT}$  &  $V_{UT}$  is known as hysteresis volt and this also define noise immunity of the circuit.



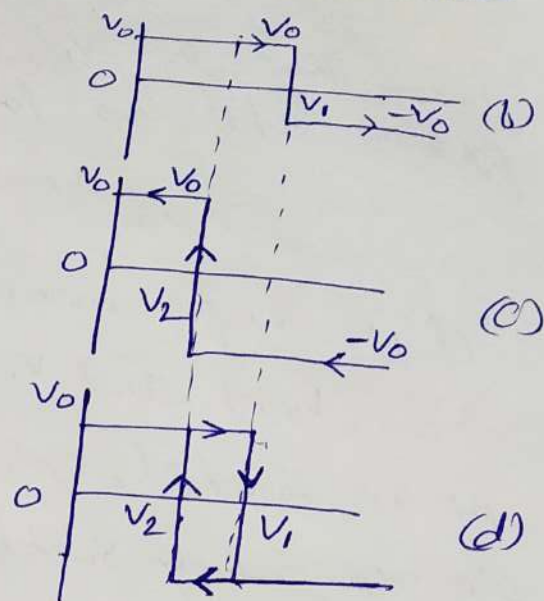
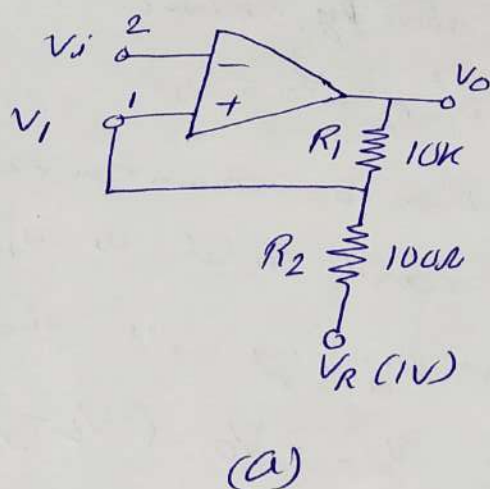


Fig (a) Schmitt trigger. The transfer characteristics (b) increasing  $V_i$  (c) decreasing  $V_i$  (d) Composite i/p - o/p curve.

- The above figure shows Schmitt trigger along with its characteristics. The i/p volt is applied to inverting terminal 2 and feedback to terminal 1.

- The feedback factor  $\beta = \frac{R_2}{R_1 + R_2}$  for  $R_1 = 10K\Omega$   
 $R_2 = 10K\Omega$

Hence  $A_v = -5,000$  the loop gain

$$- \beta A_v = 0.1 \times \frac{5000}{10.1} = 49.5 \gg 1$$

Assume that  $v_i < V_1$  so that  $v_o = +V_o (+5V)$ .  
By using superposition for the above fig we have.

$$v_i = \frac{R_1}{R_1 + R_2} V_R + \frac{R_2}{R_1 + R_2} V_o = V_1$$

- If now  $v_i$  get increased then  $v_o$  remain constant  $V_o (V_{UT})$  and  $v_i = V_1 = \text{const}$  until  $v_i = V_1$ .

At this threshold, critical or triggering volt the OP regenerative switches to  $v_o = -V_o (V_{LT})$  and remains at this value as long as  $v_i > V_1$ . The whole func<sup>n</sup> is shown in transfer characteristics.

- The volt at non-inverting terminal for  $v_i > V_1$  is

$$v_i = \frac{R_1}{R_1 + R_2} V_R - \frac{R_2}{R_1 + R_2} V_o = V_2$$

Putting values of  $R_1$  &  $R_2$  with  $V_o = 5V$  we have

$$V_1 = 1.04V \text{ \& } V_2 = 0.94V$$

- Difference between  $V_1$  &  $V_2$  is  $V_H$  called as

hysteresis. 
$$V_H = V_1 - V_2 = \frac{2R_2 V_o}{R_1 + R_2} = 0.1V$$



If  $v_i$  get decreased then the OP remains at  $-V_o$  until  $v_i$  equals the volt. terminal 1 or until  $v_i = V_2$ . At this volt a regenerative transition



takes place and o/p returns to  $+V_o$  almost instantaneously.

- As per the transfer characteristics of Schmitt trigger arrow is indicating the variation of  $v_i$ . As fig (b) denote increasing  $v_i$ , fig (c) denotes decreasing  $v_i$  and fig (d) indicate composite i/p - o/p curve.

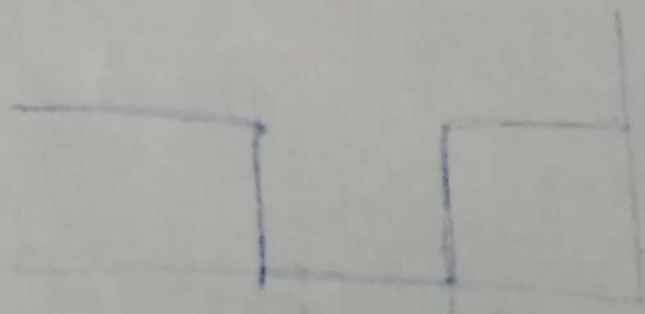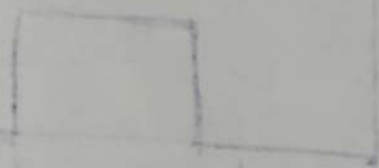- The value of  $V_H$  should be small, due to large backlash range will affect the proper function of the circuit.
- Again if peak to peak signal were smaller than  $V_H$  than in that case Schmitt trigger can't reset itself as it will continue to any one state and remain on that state only not jump from  $+V_o$  to  $-V_o$  or vice versa.




## Active Filters


- Filters are circuit that pass only a certain range of signal frequencies and attenuate unwanted frequencies.
- In accordance to band of frequencies filter can be divided as low pass, high pass, band pass and band reject (stop) filters.

Filter


(i) Low pass

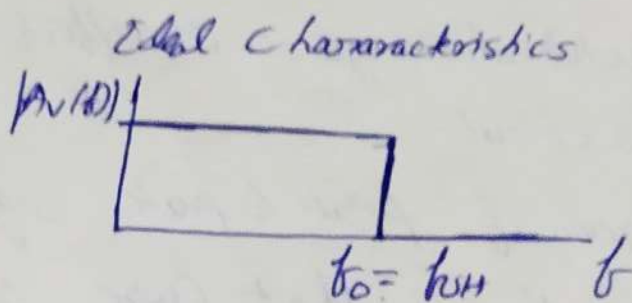


(ii) High pass

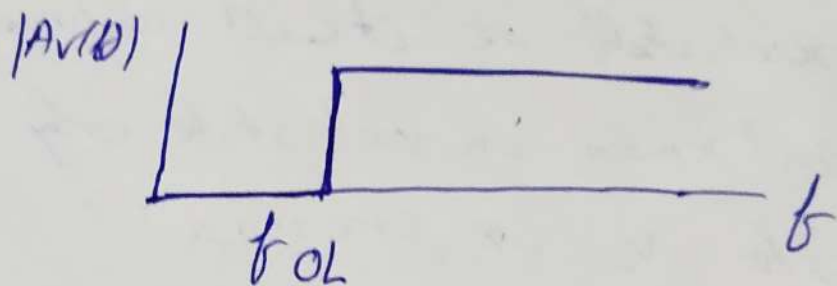

(iii) Band pass

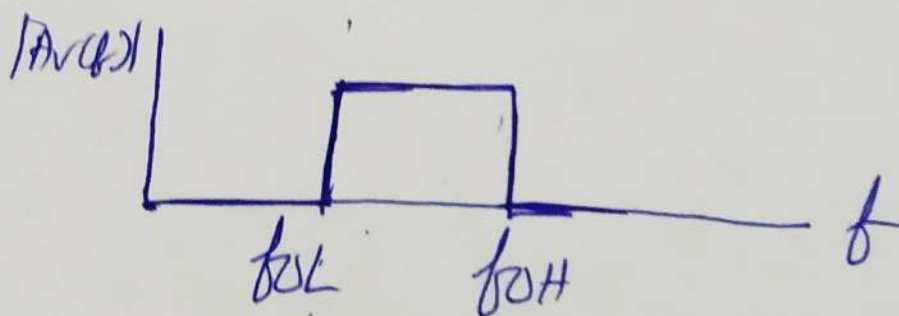

Band Reject

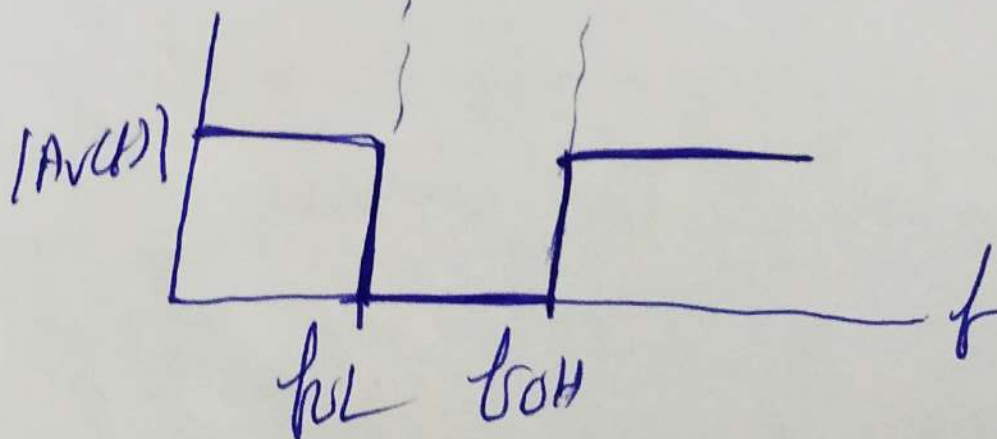



### Butterworth Filter

For an ideal low pass filter, an approximation is given in the form

$$H_1(s) = \frac{1}{P_n(s)} \quad \text{--- (i)}$$

where  $P_n(s)$  — Polynomials in the variable  $s$  with zeros in the left-hand plane.

In the Butterworth filter a little change in eq (i) is desired

$$H_1(s) = \frac{A_{V_0}}{P_n(s)} \quad \text{with } s = j\omega \quad \text{--- (ii)}$$

$$|H_1(j\omega)|^2 = H_1(s)H_1(s^*) = \frac{A_{V_0}^2}{1 + \left(\frac{\omega}{\omega_0}\right)^{2n}} \quad \text{--- (iii)}$$

Equating (i) to (iii) we have

$$|B_{ideal}| = \sqrt{1 + \left(\frac{\omega}{\omega_0}\right)^{2n}} \quad \text{--- (iv)}$$

For the realization of Butterworth filter, we have to calculate the normalized Butterworth polynomials and check on the lap returns. As we find that at higher order of  $n$ , the gain of Butterworth L-P-F is coming towards ideal condition.

Table Normalized Butterworth polynomials

$n$	Factorable polynomials $B_n(s)$
1	$(s+1)$
2	$(s^2+1.414s+1)$
3	$(s+1)(s^2+s+1)$
4	$(s^2+0.765s+1)(s^2+1.848s+1)$
5	$(s+1)(s^2+0.618s+1)(s^2+1.618s+1)$
6	$(s^2+0.518s+1)(s^2+1.414s+1)(s^2+1.932s+1)$
7	$(s+1)(s^2+0.445s+1)(s^2+1.247s+1)(s^2+1.802s+1)$
8	$(s^2+0.390s+1)(s^2+1.111s+1)(s^2+1.663s+1)(s^2+1.961s+1)$



- In the above table for  $n$  even the polynomials are product of quadratic forms and for odd there is present of an additional factor  $s+1$ .

- Damping factor  $k$  is defined as one half the coefficient of  $s$  in each quadratic factor of Table above. Like for  $n=4$  the damping factors are  $\frac{0.765}{2} = 0.383$  and  $\frac{1.848}{2} = 0.924$ .

where  $k = \cos \theta$

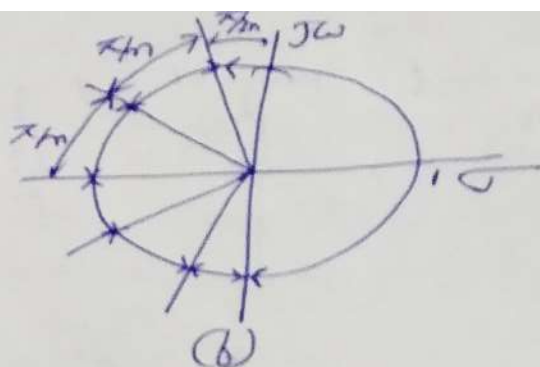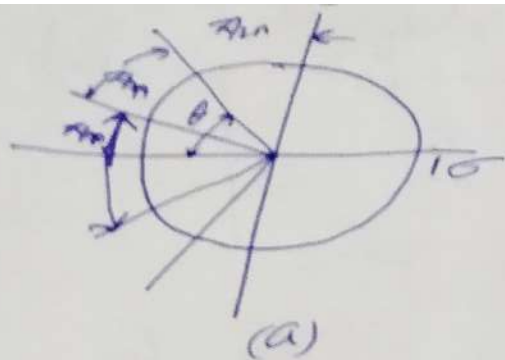$\theta \rightarrow$  defined with Butterworth circle each for even and odd shown below





The Butterworth circle for (a)  $n$  even and (b)  $n$  odd (one of zero must be at  $s = -1$ )

From the Butterworth table one can realize that

For first order filter  $\frac{AV(s)}{AV_0} = \frac{1}{s/\omega_0 + 1}$  — (v)

Second order filter  $\frac{AV(s)}{AV_0} = \frac{1}{(s/\omega_0)^2 + 2\zeta(s/\omega_0) + 1}$  — (v)

where  $\omega_0 = 2\pi f_0$  is the high freq. 3 dB point

## Practical Realization

For the practical realization let us consider a circuit of generalized active-filter prototype as shown below along with its second order low pass section and first order low pass-section

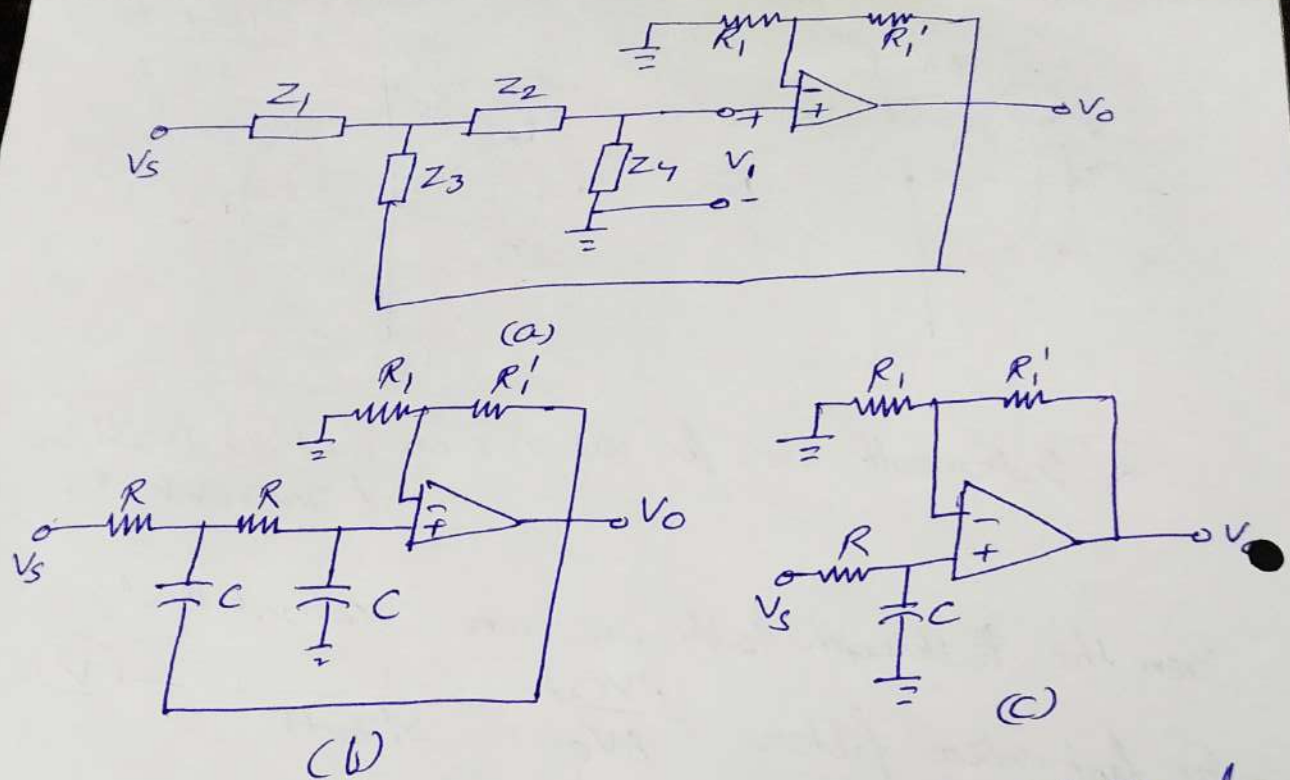


Fig:- (a) Generalized active filter type (b) second-order low pass section (c) first order LPF.

Consider Fig (a) having a stable midband gain  $\frac{V_o}{V_i} = A_{Vo} = \frac{R_1 + R_1'}{R_1}$  has to be determined - we assume that the amp<sup>r</sup> i/p current is zero hence

$$A_v(s) = \frac{V_o}{V_s} = \frac{A_{Vo} Z_3 Z_4}{Z_3 (Z_1 + Z_2 + Z_4) + Z_1 Z_2 + Z_1 Z_4 (1 - A_{Vo})} \quad \text{--- (VII)}$$

If this netw is a LPF then  $Z_1$  &  $Z_2$  are resistances and  $Z_3$  &  $Z_4$  are capacitances, having value  $R$  &  $C$  respectively.



Fig (b) illustrates the second LPP with transfer function as

$$A_v(s) = A_{V0} \frac{(1/RC)^2}{s^2 + \left(\frac{3-A_{V0}}{RC}\right)s + \left(\frac{1}{RC}\right)^2} \quad \text{--- (VIII)}$$

Comparing (VI) & (VIII)

$$\omega_0 = \frac{1}{RC}$$

• and  $2K = 3 - A_{V0}$  or  $A_{V0} = 3 - 2K$  --- (IX)

For analysing even order Butterworth filter eq (X) with identical RSC is sufficient.

But in case of odd order Butterworth filter.

it is necessary to cascade (VII) (first order) with

• Second order as shown in fig (b).

- For example a 3<sup>rd</sup> order Butterworth active filter consists of the ckt in Fig (b) in cascade of Fig (c)

with RSC chosen so that  $RC = 1/\omega_0$  with  $A_{V0}$  in

Fig (b) Selected to  $K = 0.5$  (from table  $n=3$ ) and

$A_{V0}$  in Fig C chosen arbitrarily.

## Designing consideration of other filters

### (i) High-pass Prototype:-

- In eqn (vi) interchange  $\frac{s}{\omega_s}$  with  $\frac{\omega_0}{s}$  / HPR

LPR

- Also interchange R & SC in fig (b) in a 2nd order HPR

### (ii) Bandpass Filter

- Cascade a ~~LP~~ Low Pass 2<sup>nd</sup> order having cutoff  $\omega_{HL}$  with a high pass 2<sup>nd</sup> order section whose cutoff  $\omega_{cH}$  is  $\omega_{OL}$  provided  $\omega_{HL} > \omega_{OL}$ .

### (iii) Band Reject Filter

- By paralleling a high pass section whose cutoff is  $\omega_{OL}$  with a low pass section whose cutoff  $\omega_{cH}$  is  $\omega_{HL}$  and also  $\omega_{HL} < \omega_{OL}$ .