

8.08.22
N

Circuit Theory

- ✓ Network topology is the geometry or interconnectedness of different elements in the circuit.


Incidence Matrix: The relationship between different branches incidents at a particular vertex can be represented using a matrix. This is the incidence matrix.


Sign convention:

+1 : Entry in matrix when edge current is directed away from vertex.


-1 : Edge current is directed towards vertex.

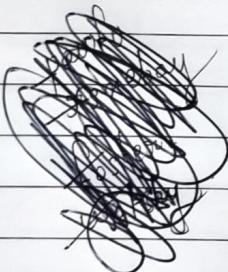0 : Edge current isn't incident on vertex.



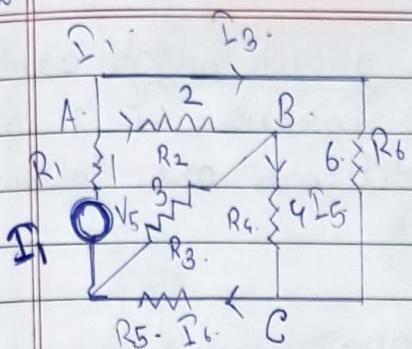

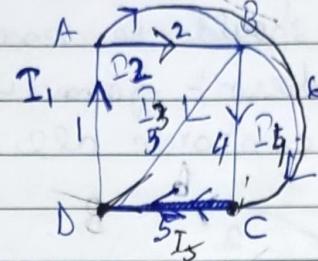Degree of vertex: The no. of edges incident to the vertex is called the degree of the vertex.



$$\bar{I}_1 = \bar{I}_2 + \bar{I}_6$$

$$\bar{I}_1 - \bar{I}_2 - \bar{I}_6 = 0 \quad \sim (1)$$

$$\bar{I}_2 = \bar{I}_4 + \bar{I}_5$$

$$\bar{I}_2 - \bar{I}_4 - \bar{I}_5 = 0 \quad \sim (2)$$

KCL at C degree of vertex:

~~$$\bar{I}_6 = \bar{I}_5 + \bar{I}_6$$~~

$$\bar{I}_4 + \bar{I}_6 = \bar{I}_5 \quad \text{At node A}$$

$$-\bar{I}_5 + \bar{I}_4 + \bar{I}_6 = 0$$

$$-I_1 + I_2 + I_6 = 0 \quad \text{--- (1)}$$

$$\Rightarrow \bar{I}_4 - \bar{I}_5 + \bar{I}_6 = 0 \quad \sim (3) \quad \text{At node B}$$

$$\bar{I}_1 = \bar{I}_3 + \bar{I}_5 \quad \text{At node C} \quad -I_2 + I_4 + I_3 = 0 \quad \text{--- (2)}$$

$$\bar{I}_1 - \bar{I}_3 - \bar{I}_5 = 0 \quad \sim (4) \quad \text{At node C}$$

$$-I_4 + I_5 - I_6 = 0 \quad \text{--- (3)}$$

$$\begin{bmatrix} 1 & -1 & 0 & 0 & 0 & -1 \\ 0 & 1 & -1 & -1 & 0 & 0 \\ 0 & 0 & 0 & 1 & -1 & 1 \\ 1 & 0 & -1 & 0 & -1 & 0 \end{bmatrix} \begin{bmatrix} \bar{I}_1 & \rightarrow \bar{I}_5 \\ \bar{I}_2 & \bar{I}_6 \\ \bar{I}_3 & \cancel{\bar{I}_6} \\ \bar{I}_4 & \end{bmatrix} = 0$$

At node D.

$$\begin{array}{c} \text{Node} \\ \text{A} \\ \text{B} \\ \text{C} \\ \text{D} \end{array} \begin{array}{c} \text{Branches} \\ 1-2 \\ 1-3 \\ 1-6 \\ 2-3 \\ 2-4 \\ 3-4 \\ 3-5 \\ 4-5 \\ 4-6 \\ 5-6 \end{array} \begin{bmatrix} \bar{I}_1 \\ \bar{I}_2 \\ \bar{I}_3 \\ \bar{I}_4 \\ \bar{I}_5 \\ \bar{I}_6 \end{bmatrix}$$

$$[A^0] = \left\{ \begin{array}{l} \text{node} \\ \text{a} \\ \text{b} \\ \text{c} \\ \text{d} \end{array} \right\} \left\{ \begin{array}{l} 1/2/3/4/5/6 \\ -1/1/0/0/0/1 \\ 0/-1/1/-1/0/0 \\ 0/0/0/-1/1/-1 \\ 1/0/-1/0/-1/0 \end{array} \right\} \left\{ \begin{array}{l} (\text{branches}) \\ 1 \\ 1 \\ 1 \\ 1 \end{array} \right\}$$

g.

* Rank of matrix is $n-1$.


* sum of the columns is 0.

* determinant of matrix is 0.

Tree

Spanning subgraph : It is the graph which contains all the vertices of the graph. It is said to be a tree if these conditions are followed:

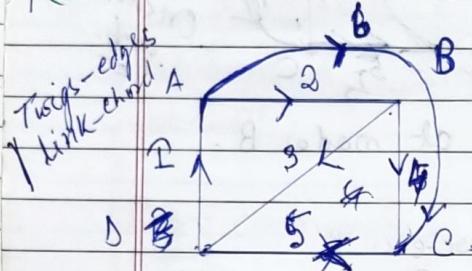- (i) It should be connected.
- (ii) It doesn't form a closed loop.
- (iii) It contains all the vertices of parent graph.



Twigs / Limbs:

The branches of the tree are called as twigs. Branches not present in trees are called limbs.

Forest:

For non-connected subgraphs, each part of the subgraph has a tree and the collection of these trees ~~is~~ is called Forest.

Co-Tree:

The complementary subgraph of a tree of the subgraph is the co-tree and the edges of the co-tree are links / chords.

No. of trees of the graph :-

$$= DC + \{ [A] [C^T] \} = 3$$


L \rightarrow reduced incidence matrix

$$[A^0] = \begin{bmatrix} -1 & 1 & 0 \\ 1 & 0 & 1 \\ 0 & -1 & -1 \end{bmatrix}$$

$$[A] = \begin{bmatrix} -1 & 1 & 0 \\ 1 & 0 & 1 \end{bmatrix}$$

$$A^T = \begin{bmatrix} 1 & 1 \\ 1 & 0 \\ 0 & 1 \end{bmatrix}$$

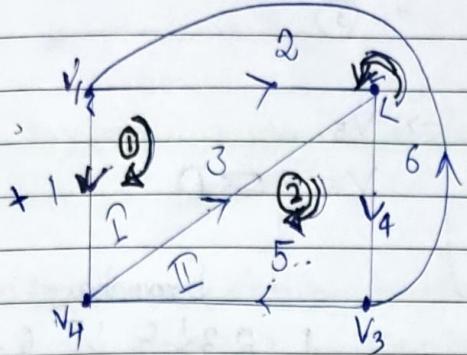* The no. of twigs = no. of nodes - 1 - (v - 1)
 $= 3 - 1 \quad (\text{e.g. } v + 1 + v - 1)$
 $= 2 \quad (\text{e.g. })$



V_1, \dots, V_6 are the branch voltage.

KVL in loop ①:

$$-V_1 + V_2 + V_3 = 0 \quad \text{--- (1)}$$

KVL in loop ②:

$$V_3 + V_4 + V_5 = 0 \quad \checkmark \quad \text{--- (2)}$$

KVL in outer loop ③:

$$-V_1 + V_2 + V_4 + V_5 = 0 \quad \text{--- (3)}$$

$$\begin{matrix} \checkmark & \begin{bmatrix} -1 & 1 & -1 & 0 & 0 & 0 \\ 0 & 0 & 1 & 1 & 1 & 0 \\ \cancel{+} & \cancel{0} & \cancel{0} & \cancel{0} & \cancel{+} & \cancel{-} \\ \checkmark & \begin{bmatrix} -1 & 1 & 0 & 1 & 1 & 0 \end{bmatrix} \end{bmatrix}$$


$$V_1 \rightarrow V_5$$

$$V_2 \rightarrow V_6 \Rightarrow [B][V_B] = 0$$

$$V_3 \rightarrow$$

$$V_4 \rightarrow$$

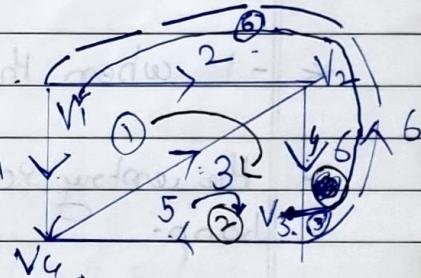$B_f \rightarrow$ fundamental loop matrix.
mental



* no. of funda. loop depends on
no. of links.

* The direction of loop current is self according
to the direction of link current.

* While forming a funda. loop, only one link is
broken at a time.


① Select the properties.

② Mark the twigs.

$$-V_1 + V_2 + V_4 + V_5 = 0 \quad \text{N } (1)$$

$$V_3 + V_4 + V_5 = 0 \quad \text{N } (2)$$
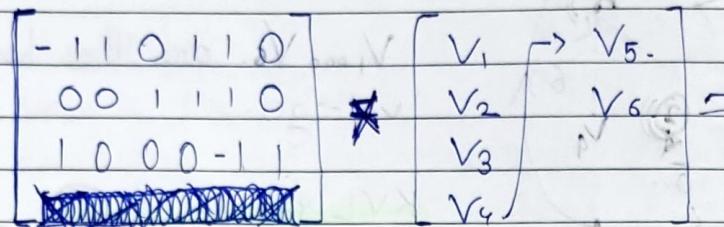
$$V_6 + V_1 - V_5 = 0 \quad \text{N } (3)$$




Branches

$$\star \star \star \star \star [B_F] = f\text{-loop } 2.$$

(1, 2, 3, 4, 5) -

1 1 1 1 1

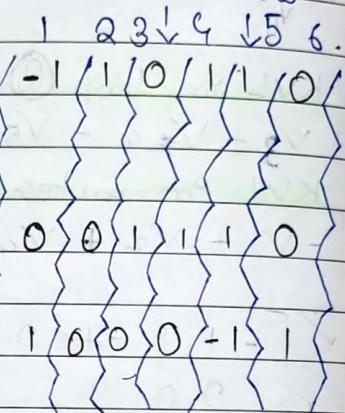f-loop 3 -
(3, 4, 5) -f-loop 4 -
(1, 6, 5) -

* If the directions of loop current and leap current coincide - matrix is + 1.


* -1 when they don't coincide.

* the entry γ_C of branch is not a part of loop.

$$B_F = \begin{bmatrix} -1 & 1 & 0 & 1 & 1 & 0 \\ 0 & 0 & 1 & 1 & 1 & 0 \\ 1 & 0 & 0 & 0 & -1 & 1 \end{bmatrix} \quad (\text{Sign Convention})$$

Def

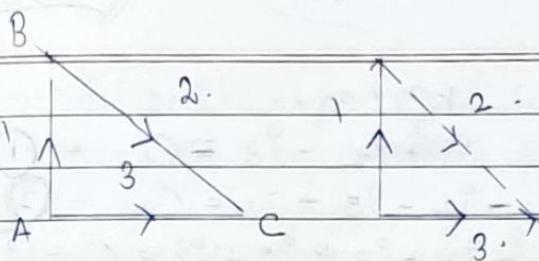Cutset Branches: Cutset is defined as the max no. of branches removal of which separates the graph into exactly 2 parts.



No. of Funda-cutset branch
chew = no. of twigs · (edges)

- * Only one twig is taken to form a fundamental cutset branch
- * direction/orientation of Funda-cutset branch depends on direction/orientation of twig

Matrix is + | ; if orientation of branch = twigs
" " - | ; if orientation ≠ twigs


$$[\Delta_F] = \begin{matrix} \text{Funda-cutset} & 1 & 2 & 3 \\ \text{f-cutset-1} & \{ & \{ & \{ \\ (1, 2) & 1 & -1 & 0 \end{matrix}$$

$$\text{f-cutset-2} \quad 0 \quad \{ \quad 1 \quad \{ \quad 1 \quad \{ \\ (3, 2) & & & & & & \end{matrix}$$

$$(\Delta_F) = \begin{bmatrix} 1 & -1 & 0 \\ 0 & 1 & -1 \end{bmatrix} \quad 2 \times 3.$$

$$\begin{matrix} 1 & 2 & 3 & 4 & 5 & 6 \\ \text{f-cutset-1} & -1 & 1 & -1 & 0 & 0 & 0 \\ (1, 2, 3) & \{ & \{ & \{ & \{ & \{ & \{ \\ \text{f-cutset-2} & 1 & 0 & 0 & 1 & 0 & 1 \\ (1, 4, 6) & \{ & \{ & \{ & \{ & \{ & \{ \\ \text{f-cutset-5} & 0 & 0 & 0 & 1 & 1 & 1 \\ (3, 5, 6) & \{ & \{ & \{ & \{ & \{ & \{ \end{matrix}$$

16.08.22

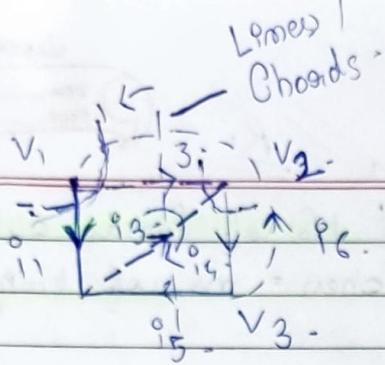

Fundamental cut set matrix

CLASSMATE
Date _____
Page _____

KCL eq.

$$i_1 + i_2 - i_6 = 0 \quad \text{--- (1)}$$

$$-i_2 - i_5 + i_4 = 0 \quad \text{--- (2)}$$

$$-i_2 - i_3 + i_5 + i_6 = 0 \quad \text{--- (3)}$$

$$\begin{bmatrix} 1 & 1 & 0 & 0 & 0 & -1 \\ 0 & -1 & -1 & 1 & 0 & 0 \\ 0 & -1 & -1 & 0 & 1 & -1 \end{bmatrix} = \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \\ i_6 \end{bmatrix} = 0.$$

$$\Rightarrow [Q_f] [I_E] = 0 \text{ or } [Q_f] [I_B] = 0$$

$$[Q_{11} \ 0] [I_E] = 0$$

$$[Q_{11} I_E + 0 I_B] = 0$$

$$Q_{11} I_E + I_B = 0 \quad \rightarrow \quad I_B = -Q_{11} I_E$$

The branch current can be expressed as
a linear combi of links / chords.

* F-loop / circuit matrix using KVL

$$-V_1 + V_2 + V_4 + V_5 = 0 \quad \text{--- (1)}$$

$$V_3 + V_4 + V_5 = 0 \quad \text{--- (2)}$$

$$V_1 - V_5 + V_6 = 0 \quad \text{--- (3)}$$

$$\begin{bmatrix} 1 & 1 & 0 & 1 & 1 & 0 \\ 0 & 0 & 1 & 1 & 1 & 0 \\ 1 & 0 & 0 & 0 & -1 & 1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \\ V_5 \\ V_6 \end{bmatrix}$$

$$[B_f] [V_c \text{ and } V_b] \Rightarrow B_f V_c = 0$$

$$\begin{bmatrix} 0 & B_{12} \\ 0 & B_{12} \end{bmatrix} \begin{bmatrix} V_c \\ V_b \end{bmatrix} = 0 \Rightarrow UV_c + B_{12} V_{eb} = 0$$

$$\Rightarrow V_c + B_{12} V_b = 0$$

$$\Rightarrow V_c = -B_{12} V_b$$

The default voltage can be expressed as the linear graph ~~voltage~~ voltage.

Relationship of Matrices :-

(1) Relation between Incidence Matrix $[A]$ and Fundamental Cut Set Matrix $[Q_f]$

From Incidence matrix $[A][I_e] = 0 \quad \text{①}$ { Use
Fundamental cutset matrix $[Q_f][I_e] = 0 \quad \text{KCL}$

↳ ②

$$\begin{array}{l} \text{Edge currents } I_e = [I_a \ I_b] \sim \text{③} \\ \text{Branch current} \end{array}$$

↳ I_e

$$[A] = [A_{11} \ A_{12}] \sim \text{④}$$

Use ③ & ④

$$[A_{11} \ A_{12}][I_e] = 0$$

$$[I_b]$$

$$A_{11}I_a + A_{12}I_b = 0$$

$$I_b = -A_{11}I_a / A_{12} \Rightarrow I_b = -A_{11}I_a A_{12}^{-1} \quad \text{⑤}$$

$$\begin{bmatrix} 0 \ Q_{11} \end{bmatrix} \begin{bmatrix} I_b \\ I_a \end{bmatrix} = 0 \Rightarrow 0I_b + Q_{11}I_a = 0$$

$$\Rightarrow I_b + Q_{11}I_a = 0$$

$$\Rightarrow I_b = -Q_{11}I_a \quad \text{⑥}$$

Equate ⑤ & ⑥

$$-Q_{11} = -A_{11}A_{12}^{-1}$$

This eq shows that rows of Fund. cutset matrix are linear combination of rows of Incidence matrix.

Relationship based on node & mesh :-

(2) Node : $[Q_f][I_e] = 0 ; [B_f][V_e] = 0$

$$[Q_{11} \ 0][I_e] = 0 \Rightarrow Q_{11}I_a = -I_b$$

$$V_e = \begin{bmatrix} V_c \\ V_b \end{bmatrix}, I_e = \begin{bmatrix} I_c \\ I_b \end{bmatrix}, B_f = \begin{bmatrix} U \\ V_b \end{bmatrix}$$

CLASSMATE

Date _____

Page _____

$$\checkmark [U \ B_{11}] \begin{bmatrix} V_c \\ V_b \end{bmatrix} = 0 \Rightarrow V_c = -B_{11} V_b \quad \checkmark$$

$$\Rightarrow V_b = B_f^T [V_c]$$

Further, V_b can be written as

From branch forms. we have;

$$\text{Branch voltage } V_b = B_f^T [V_e] \quad \checkmark$$

$$\text{" " current } I_b = Q_f^T [I_e] \quad \checkmark$$

22.08.22

$$[B_f] [Q_f] = 0 \text{ or } [Q_f] [B_f^T] = 0$$

$$\hookrightarrow [B_f] \begin{bmatrix} U \\ Q_{11}^T \end{bmatrix} = 0 \quad \hookrightarrow [B_{11} \ 0] \begin{bmatrix} V_c \\ V_b \end{bmatrix} = 0$$

$$B_{11} + Q_{11}^T = 0$$

$$[B_f^T] = -Q_f^T \quad \leftarrow B_{11} = -Q_{11}^T \quad \text{--- (1)}$$

$$[B_f] [V_e] = 0 \text{ or } [B_f] [V_b] = 0 \leftarrow \text{KVL-}A$$

$$[Q_f] [I_e] = 0 \quad \text{or} \quad [Q_f] [I_b] = 0$$

$$\text{KCL} \rightarrow [A] [I_e] = 0 \quad \text{--- (2)}$$

$$[B_f] [V_e] = 0$$

$$[B_{11} \ 0] [V_c] = 0$$

$$[B_{11} \ 0] \begin{bmatrix} V_c \\ V_b \end{bmatrix} = 0$$

$$\cancel{V_c} = B_{11} + V_{et} + V_{el} = 0$$

$$-V_{et} = -\frac{V_{el}}{B_{11}} = -B_{11}^{-1} V_{el}$$

$$e = b.$$

$$V_{eb} = Q_{11}^T V_{el}$$

$$[V_b] = [Q_{f,e}^T] [V_e]$$

Eq. (2) gives relationship between limb voltage & ac voltage.

Relationship between branch voltage & ~~ac~~ node voltage.


$$V_e = [Q_e^T] [V_T]$$

$$V_b = [A^T] [V_m] \leftarrow \text{node voltage}$$

↳ branch v. or $[V_e] = [A^T] [V_m]$

✓ Relationship between branch & loop currents
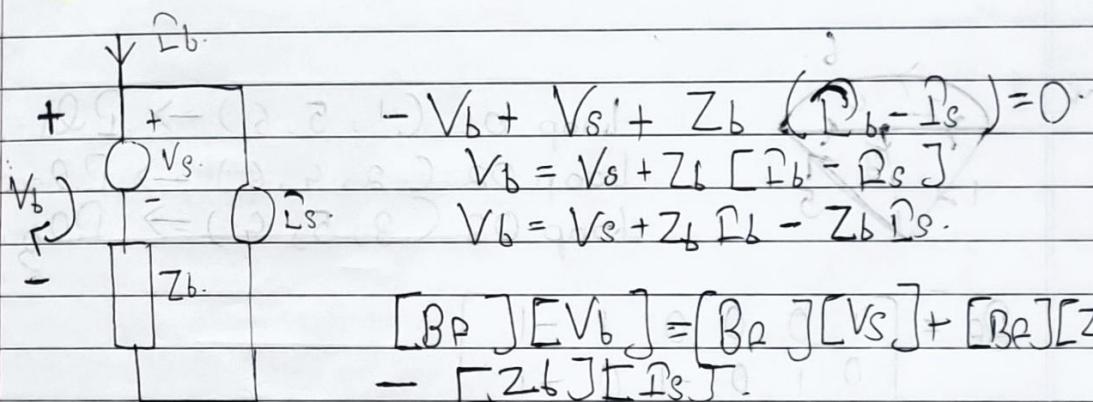
$$[I_e] = [B_F^T] [\bar{I}_e] \text{ or } [I_b] = [B_F^T] [\bar{I}_b]$$



$$\therefore [I_b] = [B_F^T] [\bar{I}_e]$$

$$[B_F^T] [V_b] = [B_F^T] [V_s] + [B_F^T] [Z_b] [B_F^T] [\bar{I}_e] -$$

$[B_F^T] [Z_b] [I_s]$

from KVL $[B_F^T] [V_b] = 0$


$$0 = [B_F^T] [V_s] + [B_F^T] [Z_b] [B_F^T] [\bar{I}_e] - [B_F^T] [Z_b] [I_s]$$

$[B_F^T] [Z_b] [B_F^T] [\bar{I}_e] = [B_F^T] [Z_b] [B_F^T] [\bar{I}_e] - [B_F^T] [V_s]$

$$[Z_b] [\bar{I}_e] = 0$$

loop impedance matrix

branch impedance matrix

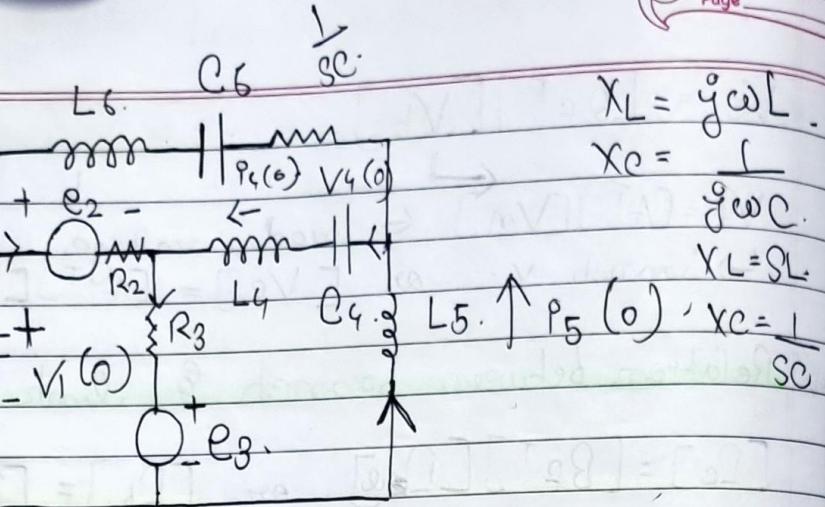


$$X_L = j\omega L$$

$$X_C = \frac{1}{j\omega C}$$

$$X_L = SL$$

$$X_C = \frac{1}{SC}$$

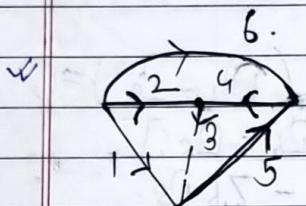

loop 01. (1, 5, 6) \rightarrow $Z_{15}L$

loop 02 (2, 4, 6) \rightarrow $Z_{26}L$

loop 03 (3, 5, 4) \rightarrow $Z_{34}L$

$$\boxed{B_P = \begin{bmatrix} 1 & 0 & 0 & 0 & 1 & -1 \\ 0 & 1 & 0 & -1 & 0 & -1 \\ 0 & 0 & 1 & 1 & 1 & 0 \end{bmatrix}}$$

23/08/22

Transform the 'E' domain into 'S' domain

$L \rightarrow SL$ \leftarrow Impedance value. $s \leftarrow$ admittance

$1/SL \leftarrow$ Admittance value.

$j\omega L \leftarrow$ admittance

$$\boxed{\del{B_P} = \begin{bmatrix} 1/SL & 0 & 0 & 0 & 0 & 0 \\ 0 & R_2 & 0 & 0 & 0 & 0 \\ 0 & 0 & R_3 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1/SC + SL & 0 & 0 \\ 0 & 0 & 0 & 0 & S & SL \end{bmatrix}}$$

$$\del{V_b = L \frac{dI(e)}{dt}}$$

$$\boxed{V(E) = \frac{1}{j} \frac{dI(E)}{dt}}$$

Differentiation theorem
in s domain.

$$\frac{dL}{dt} i(t) = L(V_s - v_{ob})$$

$$\frac{dV_s}{dt} = SL v(s) - L v_{ob}$$

$$i(s) = V_s / sL + \frac{v_{ob}}{sL}$$

 ~~$i(s)$~~

$$\rightarrow \frac{1}{sL} \downarrow \frac{v_{ob}}{s} \leftarrow \begin{array}{l} \text{initially} \\ \text{charged} \end{array}$$

$$i(t) = C \frac{dv(t)}{dt}$$

$$i(s) = C [s v(s) - v_{ob}] \quad \leftarrow \rightarrow$$

$$i(s) = sC v(s) - C v_{ob} \quad \leftarrow \rightarrow$$

$$v(s) = \frac{v(s)}{sC} + \frac{v_{ob}}{sC}$$

$$[V_s] = \begin{bmatrix} V_{1(0)} & 5 \\ e_2 & e_3 \end{bmatrix} \rightarrow \begin{bmatrix} v_q^{(+0)} / s - s v_{ob} \\ s^2 v_{ob} - 1 \end{bmatrix}$$

26.08.2022 //


Equilibrium eq. in node basis -

$$I_b = I_s + (V_b - V_s) Y$$

Multiply both sides by reduced incidence matrix

$$A I_b = A I_s + A Y (V_b - V_s) \quad ①$$

$$V_b = A T_m V_m \quad ②$$

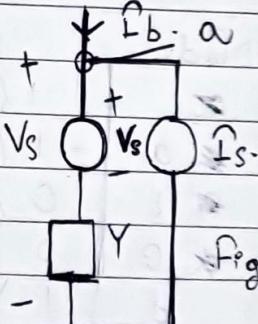

Use eq. ② in eq. ①.

$$A I_b = A I_s + A Y (A^T V_m - V_s)$$

$$[A][I_b] = [A][I_s] + [A][Y][A^T][V_m] - [A][Y][V_s]$$

By KCL $\rightarrow [A][I_b] = 0$

$$0 = [A][I_s] + [Y_m][V_m] - [A][Y][V_s]$$

$$[Y_m][V_m] = [A][Y][V_s] - [A][I_s]$$

$$[I_m] = [A][Y][V_s] - [A][I_s]$$

Multiply both sides by fundamental cutset matrix

$$Q_p I_b = Q_p I_s + Q_p Y (V_r - V_s) \quad ①$$

$$V_b = Q_F^T V_F \quad (2)$$

Use eq (2) in (1).

$$Q_F I_b = Q_F I_S + Q_F Y (Q_F^T \cdot V_F - V_S) -$$

$$[Q_F][I_b] = [Q_F][I_S] + [Q_F][Y][Q_F^T][V_F] - [Q_F][Y][V_S]$$

By KCL $[Q_F][I_b] = 0$.

$$0 = [Q_F][I_S] + [Y_F][V_b] - [Q_F][Y][V_S].$$

$$[Y_F][V_b] = [Q_F][Y][V_S] - [Q_F][I_S].$$

$$Y_F = E_{Q_F}[Y][Q_F^T].$$


→ branch admittance. $\frac{1}{s}$

$$[Y_b].$$

$$I_F = \frac{1}{s} \leftarrow \text{impedance}$$

$$s.$$

$$I_H = s. \leftarrow$$

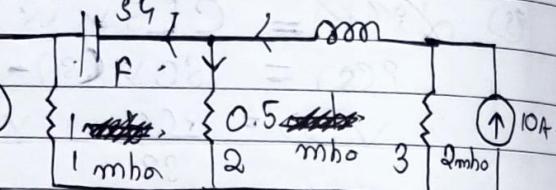

Fig(a)

~~Node~~

Oriented
Graph -

~~Node~~

Branches

~~a~~

1 { 2 { 3 { 4 { 5 {

~~b~~


-1 } 0 } 0 } 1 } 0 }

~~c~~

0 } 1 } 0 } -1 } -1 }

~~d~~

0 } 0 } -1 } 0 } 0 }

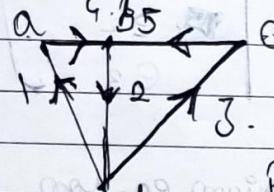

Fig(a)(b)

~~d~~

1 } -1 } 1 { 0 } 0 }

$$A = \begin{bmatrix} -1 & 0 & 0 & 1 & 0 \\ 0 & 1 & 0 & -1 & -1 \\ 0 & 0 & -1 & 0 & 0 \\ 0 & 0 & 0 & 5 & 0 \\ 0 & 0 & 0 & 0 & 1/5 \end{bmatrix}$$

~~Y~~

$$Y = \begin{bmatrix} 1 & 0 & 0 & 0 & 0 \\ 0 & -0.5 & 0 & 0 & 0 \\ 0 & 0 & 2 & 0 & 0 \\ 0 & 0 & 0 & 5 & 0 \\ 0 & 0 & 0 & 0 & 1/5 \end{bmatrix}$$

$$V_m = \begin{bmatrix} V_a \\ V_b \\ V_c \\ V_d \\ V_e \end{bmatrix}$$

$$[Y_m] = [A]^T Y [A]$$

$3 \times 5 \quad 5 \times 5 \quad 5 \times 3$

~~Y_s~~

$$B = \begin{bmatrix} 5 \\ 10 \\ 0 \\ 0 \\ 0 \end{bmatrix} \quad 5 \times 1$$

Some direction is +ve.
Different direction is -ve.

SIGN CONVENTION

$$V_2(0) \cdot i_{2G}(0)$$

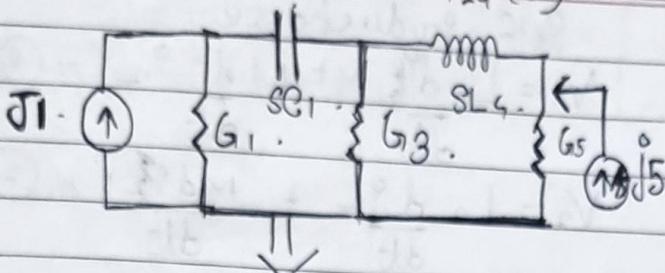


Fig 3.

Transformed N/W.


$$[Y] = \begin{bmatrix} G_1 & 0 & 0 & 0 & 0 \\ 0 & G_3 & 0 & 0 & 0 \\ 0 & 0 & G_5 & 0 & 0 \\ 0 & 0 & 0 & SC_1 & 0 \\ 0 & 0 & 0 & 0 & 1/SC_4 \end{bmatrix}$$

$$\dot{q} = C dv/dt \quad q = 1/L \int v dt$$


$$v(s) = SC_1 v(s) - q(s) \quad q(s) = 1/SC_4 v(s) + V(0^+)$$

$$M_{12} = M_{21} = M$$
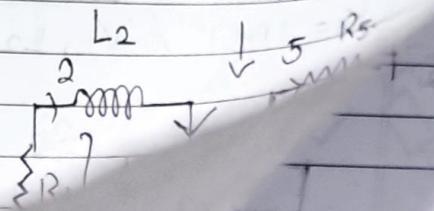
$$\begin{bmatrix} J_1 & \bar{C}V_{C_2}(0) \\ 0 & i_{L4}(0)/5 \\ J_5 \end{bmatrix}$$



Mesh / Loop Analysis \rightarrow

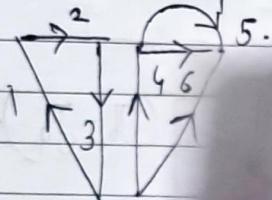

$$\begin{bmatrix} \omega & 0 & 0 \\ 0 & 1 & 1 \end{bmatrix}$$

$$= \begin{bmatrix} 1/4 & 1/3 & 1/4 & 0 & 0 \\ 0 & 0 & 1/4 & 1/4 & 1/5 \end{bmatrix} = \begin{bmatrix} 1 \\ 0 \\ 0 \\ 0 \\ 1/5 \end{bmatrix}$$

$$[Z_b] = \begin{bmatrix} R & 0 & 0 \\ 0 & 0 & 0 \\ 0 & 0 & 0 \end{bmatrix}$$

(Ans.)

Multiply
Loop -
Admittance

$$[V_L] = [Z_b] [V_B] [Y_b]. \quad \text{Loop Admittance.}$$

$$\times [V_{ba} \rightarrow V_{tb}]$$

Self Inductance.


$$V_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} \approx 0 \quad (1)$$

Take Laplace
trans. on both
sides of eqn
(2)

$$V_2 = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt} \approx 0 \quad (2)$$

$$\begin{aligned} V_1(s) &= SL_1 i_1(s) - L_1 i_2(0^+) + SMi_2(s) - Mi_2(0^+) \\ &= SL_1 i_1(s) + SMi_2(s) - L_1 i_2(0^+) - Mi_2(0^+) \end{aligned}$$
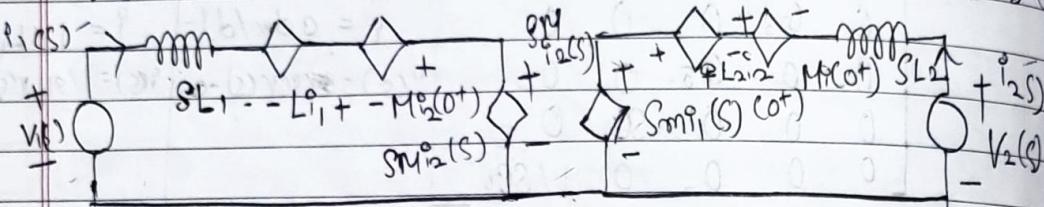
$$V_2(s) = SL_2 i_2(s) - L_2 i_1(0^+) + SMi_1(s) - Mi_1(0^+)$$




$$K = IMI / \sqrt{L_1 L_2}$$

$$Z_h = -R + 1/S_C + S_C$$

$$Y_b = G + S_C + 1/SC$$



$$V_h = V_e + [J_b - J_q] Z_h$$

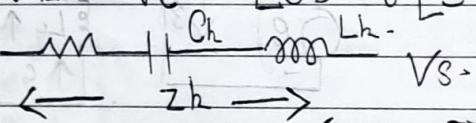

$$V_h = V_e + (J_b - J_q) R_h + \frac{1}{C_h} \int (J_b - J_q) dt + L_h \frac{d}{dt} (J_b - J_q)$$

$$2 \frac{df(t)}{dt} = 8f(s) \Rightarrow 2 \int_0^t f(t) dt = f(s) + f(0)$$

29.08.22
~

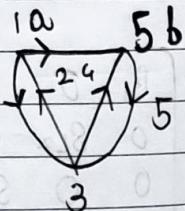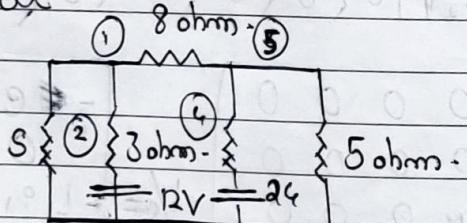

Oriental
Graph

$$(Q_F) = \begin{bmatrix} -1 & 1 & -1 & 0 & 0 \\ 0 & 0 & -1 & 1 & 1 \end{bmatrix}_{2 \times 5}, \quad V_B = \begin{bmatrix} 0 \\ -12 \\ 0 \\ -24 \end{bmatrix}_{5 \times 1}$$

admittance

$$\text{Branch Voltage } V_B = \begin{bmatrix} 1/4 & 0 & 0 & 0 & 0 \\ 0 & 1/3 & 0 & 0 & 0 \\ 0 & 0 & 1/8 & 0 & 0 \\ 0 & 0 & 0 & 1/4 & 0 \\ 0 & 0 & 0 & 0 & 1/5 \end{bmatrix}$$

$$\text{Loop } [Y_L] = [Q_F] [Y_B] [Q_F]$$

Admittance

~~$$= \begin{bmatrix} -1 & 1 & -1 & 0 & 0 \\ 0 & 0 & -1 & 1 & 1 \end{bmatrix} \begin{bmatrix} 1/4 & 0 & 0 & 0 & 0 \\ 0 & 1/3 & 0 & 0 & 0 \\ 0 & 0 & 1/8 & 0 & 0 \\ 0 & 0 & 0 & 1/4 & 0 \\ 0 & 0 & 0 & 0 & 1/5 \end{bmatrix}$$~~

Rough -

$$1/4 = 4/10 = \frac{2}{5}$$

$$= \begin{bmatrix} -1 & 1 & -1 & 0 & 0 \\ 0 & 0 & -1 & 1 & 1 \end{bmatrix} \begin{bmatrix} -1 & 1 & -1 & 0 & 0 \\ 0 & 0 & -1 & 1 & 1 \end{bmatrix}$$

$$= \begin{bmatrix} 1+0 & 1+0 & 1+1 & 0 & 0 \\ 0 & 0 & 1+1 & 0+1 & 1 \end{bmatrix} = \begin{bmatrix} 1 & 1 & 2 & 0 & 0 \\ 0 & 0 & 2 & 1 & 1 \end{bmatrix}$$

$$\begin{bmatrix} 1 & 1 & 2 & 0 & 0 \\ 0 & 0 & 2 & 1 & 1 \end{bmatrix} \begin{bmatrix} 1/4 & 0 & 0 & 0 & 0 \\ 0 & 1/3 & 0 & 0 & 0 \\ 0 & 0 & 1/8 & 0 & 0 \\ 0 & 0 & 0 & 1/4 & 0 \\ 0 & 0 & 0 & 0 & 1/5 \end{bmatrix} = \begin{bmatrix} 1/4 & 1/3 & 1/4 & 0 & 0 \\ 0 & 0 & 1/4 & 1/4 & 1/5 \end{bmatrix}$$

$$= \begin{bmatrix} 0.708 & 0.125 \\ 0.125 & 0.575 \end{bmatrix} \quad (\text{Ans.})$$

Multiply
Loop -
Admittance

$$[Y_L] [V_L] = [Q_F] [V_B] [Y_B]$$

or

$$\times [V_{ba} \rightarrow V_{tb}]$$

Loop Admittance.

$$\begin{bmatrix} V_{ba} \\ V_{bb} \end{bmatrix} = \begin{bmatrix} 0.708 & 0.125 \\ 0.125 & 0.575 \end{bmatrix} \begin{bmatrix} -1 & 1 & 1 & 0 & 0 \\ 0 & 0 & -1 & 1 & 0 \end{bmatrix} = \begin{bmatrix} 0.708 \\ 0.575 \end{bmatrix}$$

$$= \begin{bmatrix} -4 \\ -6 \end{bmatrix} \Rightarrow \begin{bmatrix} V_{ba} \\ V_{bb} \end{bmatrix} = \begin{bmatrix} -3.96 \\ -9.57 \end{bmatrix}$$




$$\begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \\ V_5 \\ V_6 \end{bmatrix} = \begin{bmatrix} -1 & -1 & 0 & 0 \\ 0 & 0 & -1 & 1 \end{bmatrix} \begin{bmatrix} -3.96 \\ -9.57 \end{bmatrix} \rightarrow \begin{bmatrix} Z_{12} = Z_{21} \\ Z_{13} = Z_{31} \\ Z_{23} = Z_{32} \end{bmatrix}$$

Incase of (Independent Sources) :-

$$I_b = [Y_b] [V_b - V_s]$$

2.9.22
N

Network Theory Control Process.

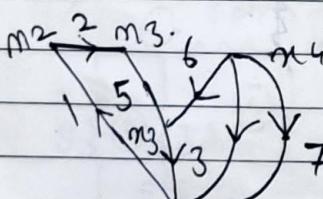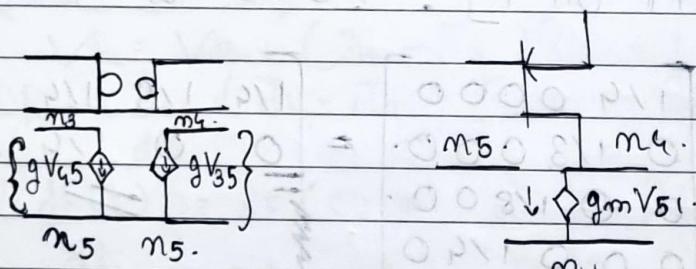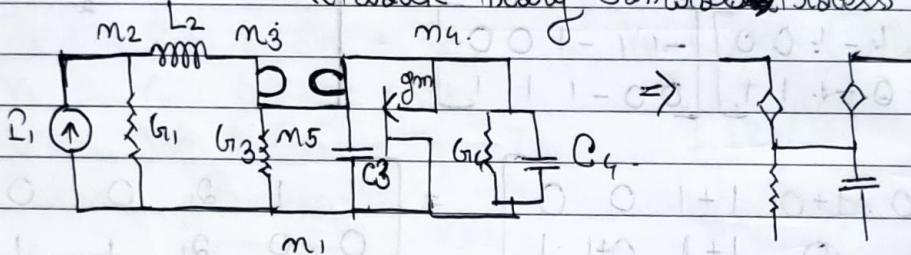

[A]



1	2	3	4	5	6	7
m ₂	-1	2	0	0	0	0
m ₃	0	-1	0	0	1	0
m ₄	0	0	0	1	0	1
m ₅	0	0	1	0	-1	-1
m ₆	1	0	-1	-1	0	0

$$Y_b = \begin{bmatrix} G_1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1/S_L & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & S_C & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & G_4 + S_C \end{bmatrix}$$

$$[Y_L] = [A][Y_b][A]$$

$$\bar{I}_S = \begin{bmatrix} \bar{I}_1 \\ 0 \\ 0 \end{bmatrix} \quad \begin{bmatrix} gV_{45} \\ -gV_{35} \\ 0 \end{bmatrix}$$
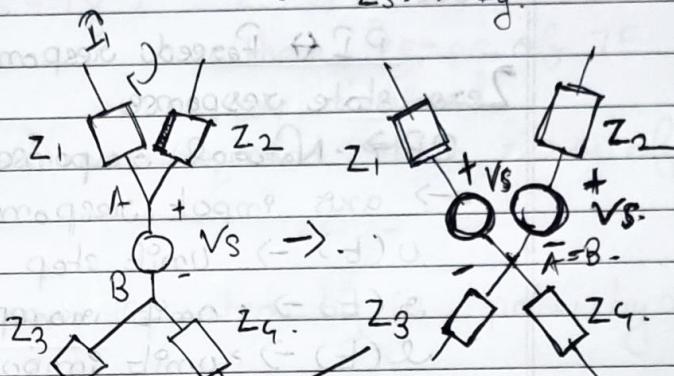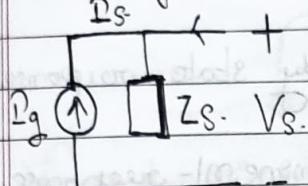
$$V_S = V_g + Z_S \bar{I}_S. \quad V_g = V_S - Z_S \bar{I}_S. \quad \bar{V}_S = \frac{V_g}{Z_S} + \bar{I}_S.$$



$$\rightarrow \bar{I}_1 Z_1 + V_2 Z_2 - Z_2 \bar{I}_1 = 0$$

$$V_2 Z_2 = Z_2 \bar{I}_1 - Z_1 \bar{I}_1 -$$


$$-V_5 + Z_1 \bar{I}_1 + V_2 Z_2 + Z_2 \bar{I}_1 + \bar{I}_3 = 0.$$



$$-V_2 Z_2 Z_3 + (\bar{I}_2 - \bar{I}_1) Z_4 - V_5 +$$

$$Z_2 (\bar{I}_2 - \bar{I}_1) = 0.$$

$$V_2 Z_2 Z_3 = (\bar{I}_2 - \bar{I}_3) Z_4 - V_5 + Z_2 (\bar{I}_2 - \bar{I}_1).$$
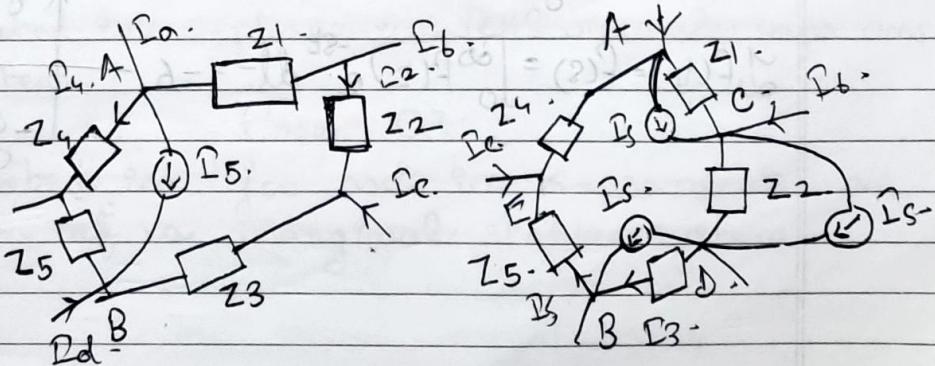
$$V_2 Z_2 = -(\bar{I}_1 Z_1 + \bar{I}_2 Z_2)$$



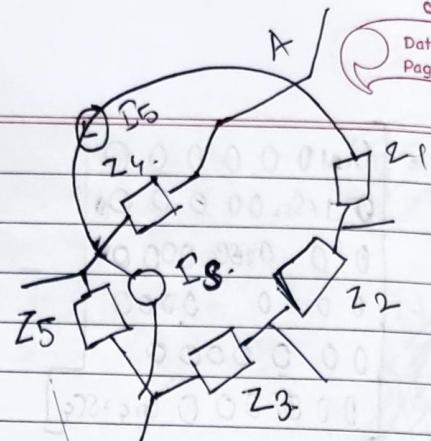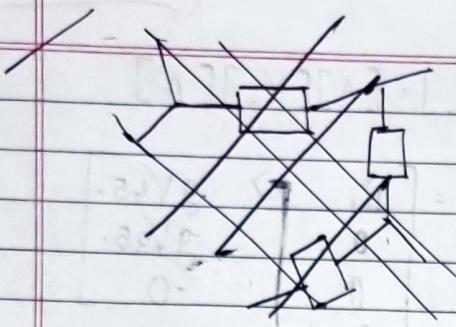

$$\frac{dY(t)}{dt} + aY(t) = n(t).$$

P I \leftrightarrow Forced response \leftrightarrow Steady state response
Zero state response

CF \Rightarrow Natural response \rightarrow permanent response \leftrightarrow
 \leftrightarrow unit input response.

$U(t)$ \rightarrow Unit step signal.

$r(t)$ \rightarrow Unit ramp signal

$\delta(t)$ \rightarrow Unit impulse signal

$\delta(t)$

$$s(t) = 1 \text{ at } t=0 \\ = 0 \text{ at } t \neq 0$$




$$0 \times \infty = 1 - \int_{-\infty}^{\infty} s(t) dt = 1$$

\hookrightarrow complex variable

Laplace Transformation : $(\mathcal{L}) f(t) = F(s)$

$$s = 6 \pm j\omega \rightarrow \text{and } s^{-1}$$
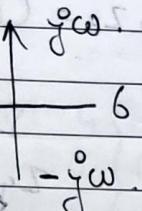
$$\mathcal{L} f(t) = F(s) = \int_0^{\infty} f(t) e^{-st} dt = -6$$



Representation of poles & zeros.

$$T(s) = \frac{(b_m s^m + b_{m-1} s^{m-1} + b_{m-2} s^{m-2} + \dots + b_0)}{(a_m s^m + a_{m-1} s^{m-1} + a_{m-2} s^{m-2} + \dots + a_0)}$$

(General exp for 7F ↑

Scaling Factor : $\sum_{i=1}^m (s - z_i)$ ← when numerator factors are equated to zero,
 $\sum_{j=1}^m (s - p_j)$ → then zeros of 7F are obtained.

When denominator factors are equated, then zeros of 7F are obtained.

In S-planes zeros are separated by 0, poles by ∞

Stability
= \oint

The location of s-planes decides an important role in controlling stability of system.

Case - 01



Poles located on S-plane in LHS give absolute stability of system.

Case - 02

Poles located on S-plane in RHS reveals an unstable system.

Case - 03

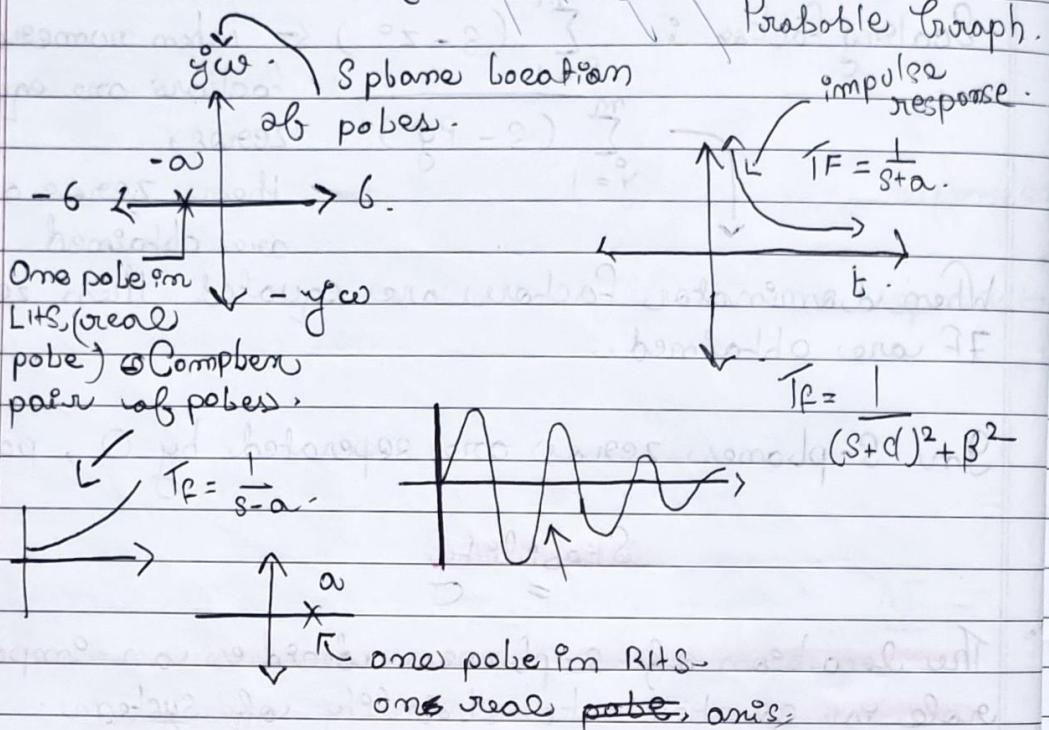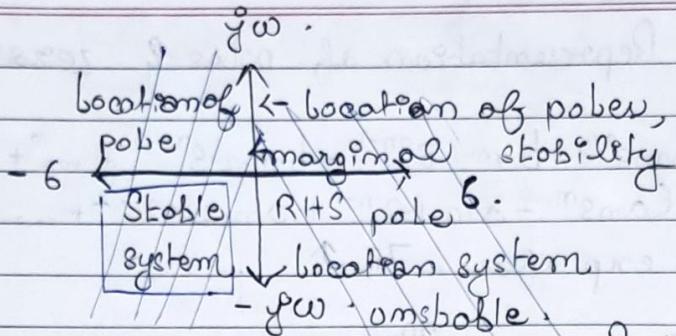Poles located on 'jω' axis in S-plane is an indication of a marginal stable system.



12.09.22

Two port - N/W


A pair of available terminals.
Devices.

One port n/w
(one pair of terminals)

Two port n/w
(two pairs of terminals)


Multiport n/w
(multiple pairs of terminals)

Ex : Fan, microwave, tube light etc. } Ex : Transistor, op-amp -

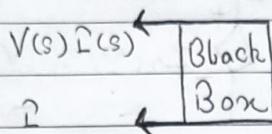Schematic Diagram.One portm/wRelationship between voltage & current (V_s & I_s)

$$Z(s) = V(s) / I(s) \leftarrow \text{point impedance}$$

$$Y(s) = I(s) / V(s) \leftarrow \text{point admittance}$$

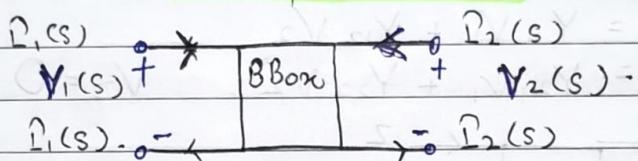Two port - m/w


There are 4 variables & the relationship between them is established by different equations also known as characteristic equations.

$$(V_1, V_2) = f(I_1, I_2) \leftarrow z\text{-parameters, open C/CL}$$

$$V_1 = Z_{11}I_1 + Z_{12}I_2 \quad \leftarrow \text{impedance}$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

Port 2 = 0 i.e. output port-2;

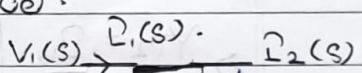

$$V_1 = Z_{11}I_1$$

$$\checkmark \quad \frac{V_1}{I_1} = Z_{11} \quad | \quad I_2 = 0 \quad | \quad Z_{11} \text{ & } Z_{22} \text{ are}$$

$$\checkmark \quad Z_{21} = \frac{V_2}{I_1} \quad | \quad I_2 = 0 \quad | \quad \text{Forward transfer impedance.}$$

$\nabla (Z_{21} \text{ & } Z_{12} \text{ are})$

$$\checkmark \quad \text{Port 1} = 0 \quad | \quad \text{i.e. open chl- port-1}$$


$$| \quad Z_{12} = V_1 / I_2 \quad | \quad I_1 = 0 \quad | \quad \text{Reverse Transfer}$$

$$| \quad Z_{22} = V_2 / I_2 \quad | \quad I_1 = 0 \quad | \quad \text{Impedance-}$$

$\hookrightarrow \text{O/P Impedance.}$

If the two port under consideration is reciprocal, then

$$Z_{12} = Z_{21}$$

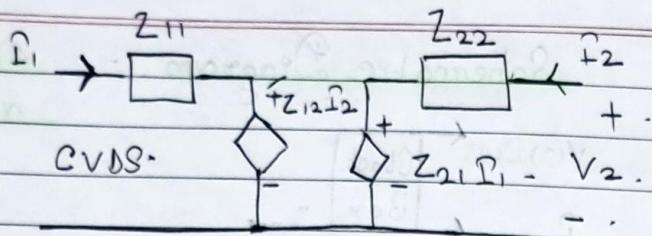

CVDS (This generates eq.)

(current-def. voltage source)

Y -parameter short-ckt admittance parameter
 $(\bar{I}_1, \bar{I}_2) = f(V_1, V_2)$

→ ↪ Taylor Series -

Itakios.

$$\bar{I}_1 = Y_{11}V_1 + Y_{12}V_2$$

$$\bar{I}_2 = Y_{21}V_1 + Y_{22}V_2 \quad | V_2 = 0$$


1		2
V ₁	$\boxed{\text{BBox}}$	I ₂
		$Y_2 = 0$
1		I ₂

$$Y_{21} = \bar{I}_2 / V_1 \quad | V_2 = 0$$

$$Y_{11} = \bar{I}_1 / V_1 \quad | V_2 = 0$$

Douvin point admittance factor.


$$Y_{12} = \frac{\bar{I}_1}{V_2} \quad | V_1 = 0$$

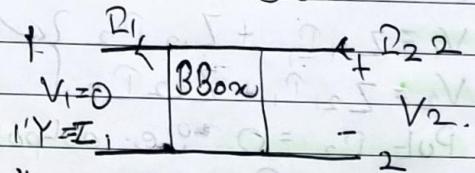

Reverse transfer admittance.

$$Y_{22} = \bar{I}_2 / V_2 \quad | V_1 = 0$$

O/P admittance

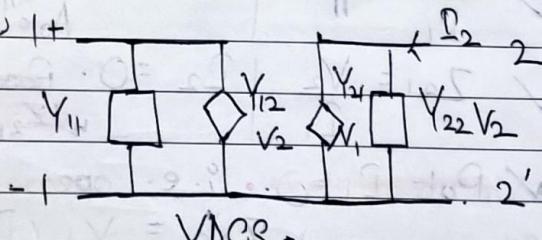


T-Parameters, ABCD Parameters, chain para.

Enclosure for overhead transmission

$$V_1 \bar{I}_1 = f(V_2, -\bar{I}_2)$$


$$V_1 = A V_2 + B(-\bar{I}_2) \quad \bar{I}_1 = C V_2 + D(-\bar{I}_2)$$

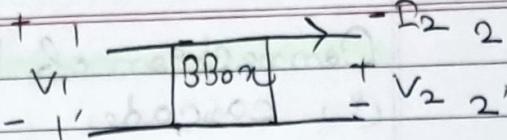$\frac{V_2}{V_{12}} = \frac{R_2}{R_1 + R_2}$, i.e. open
PoT $R_2 = 0$. cht port 2 -



$$A = V_1 / V_2 \mid -R_2 = 0$$

Reverse voltage gain.

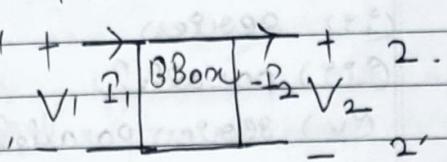

$$C = I_1 / V_2 \mid -R_2 = 0$$

Reverse transfer admittance (T) -

PoT $V_2 = 0$ i.e. cht port 2, 2' (short-cht)

$$\beta = V_1 / I_2 \mid V_2 = 0 \quad (\text{2nd Reverse trans. imp})$$

$D_R = I_1 / -R_2 \mid V_2 = 0$ Reverse current-gain


Hybrid / h-parameter.

Popularly used for small signal analysis of
transistors.

$$(V_1, I_2) = P(I_1, V_2). \quad V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

PoT $V_2 = 0$. i.e. short-cht port 2, 2'

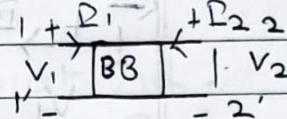

Driving point imp $\rightarrow h_{11} = V_1 / I_1 \mid V_2 = 0$.


current gain $\rightarrow h_{21} = I_2 / I_1 \mid V_2 = 0$.

PoT $I_1 = 0$ i.e. short-cht port 1, 1' $\rightarrow I_1 = 0 \quad I_2 = 0$



$$h_{12} = V_1 / V_2 \mid I_1 = 0 \quad \text{voltage gain}$$

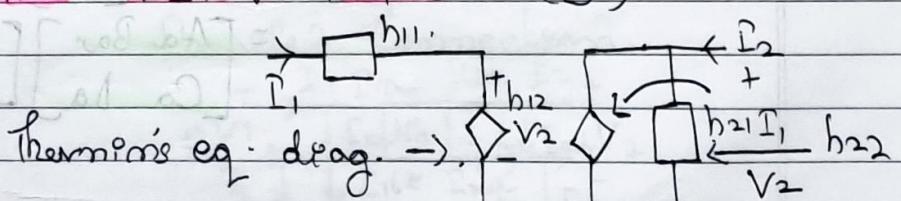O/P admittance $h_{22} = I_2 / V_2 \mid I_1 = 0 \quad (\text{IJ})$



Norton's
eq cht diagram.

Connection of two port n/w s.

(i) cascade connection


(ii) series

(iii) parallel

(iv) series parallel

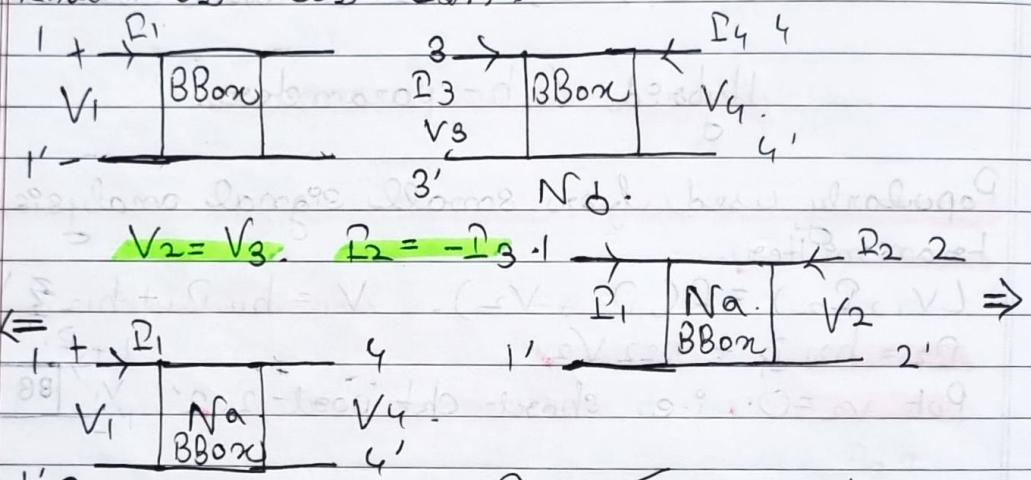(v) parallel series

Cascade connection: When output of one device becomes input of another device it is known as casc. conn.



Find T-parameter of N_a.

$$N_a = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix}$$

Find T-parameter of N_b.

$$N_b = \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix}$$

The overall T-parameter will be

$$[T] = [T_a][T_b]$$

$$= \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix}$$


15.9.22

CLASSMATE

Date _____

Page _____

Series Connection

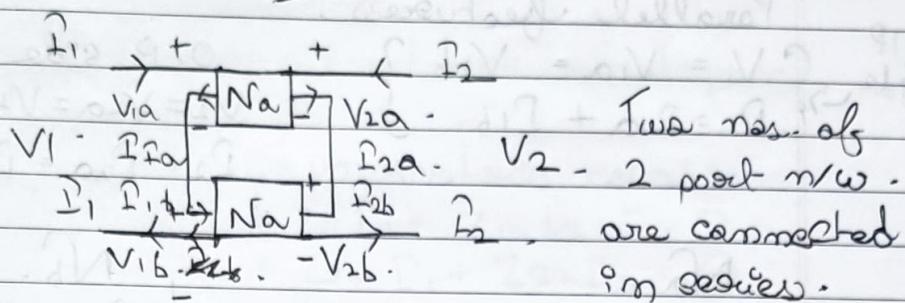

Write 2 parameters of each two port n/w.

Z-parameters n/w Na

$$V_{1a} = Z_{11a} I_{1a} + Z_{12a} I_{2a}$$

$$V_{2a} = Z_{21a} I_{1a} + Z_{22a} I_{2a}$$

Z-parameters for

n/w Nb

$$V_{1b} = Z_{11b} I_{1b} + Z_{12b} I_{2b}$$

$$V_{2b} = Z_{21b} I_{1b} + Z_{22b} I_{2b}$$

Using series prop.

$$I_1 = I_{1a} = I_{1b}$$

$$Z_{11} = Z_{11a} + Z_{11b}$$

$$I_2 = I_{2a} = I_{2b}$$

$$Z_{12} = Z_{12a} + Z_{12b}$$

$$V_1 = V_{1a} + V_{2a} \quad \textcircled{A}$$

$$Z_{21} = Z_{21a} + Z_{21b}$$


$$V_2 = V_{2a} + V_{2b} \quad \textcircled{B}$$

$$Z_{22} = Z_{22a} + Z_{22b}$$

* For series connections Z-parameters are used & the overall connection's Z-parameter will be of additive nature.

(910)

Parallel Connection

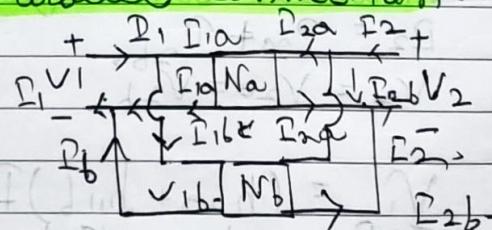

DIP
side

Parallel features.

$$\left. \begin{array}{l} V_1 = V_{1a} = V_{1b} \\ P_1 = P_{1a} + P_{1b} \end{array} \right\}$$

ORP side

$$V_2 = V_{2a} = V_{2b}$$

$$P_2 = P_{2a} = P_{2b}$$

Na.

$$P_{1a} = Y_{11a} V_{1a} + Y_{12a} V_{2a}$$

Nb.

$$P_{1b} = Y_{11b} V_{1b} + Y_{12b} V_{2b}$$

$$P_{2a} = Y_{21a} V_{1a} + Y_{22a} V_{2a}$$

$$P_{2b} = Y_{21b} V_{1b} + Y_{22b} V_{2b}$$

$$P_1 = P_{1a} + P_{1b}$$

$$P_1 = (Y_{11a} + Y_{11b}) V_1 + (Y_{12a} + Y_{12b}) V_2$$

$$P_2 = (Y_{21a} + Y_{21b}) V_1 + (Y_{22a} + Y_{22b}) V_2$$


$$Y_{11} = Y_{11a} + Y_{11b}$$

$$Y_{21} = Y_{21a} + Y_{21b}$$

$$Y_{12} = Y_{12a} + Y_{12b}$$

$$Y_{22} = Y_{22a} + Y_{22b}$$

Series Parallel Connection.

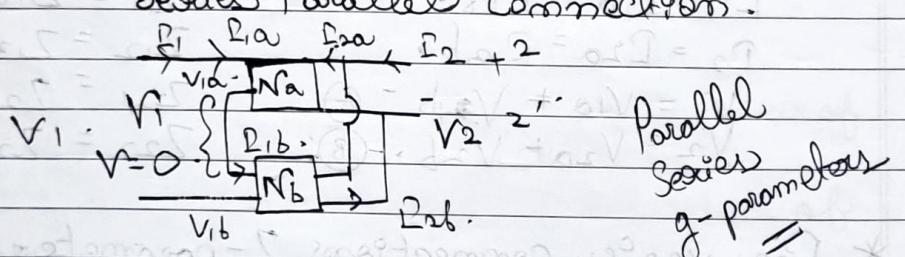

Series com-features (DIP)

$$P_1 = P_{1a} = P_{1b}$$

$$V_1 = V_{1a} + V_{1b}$$

Parallel com-features (ORP)

$$P_2 = P_{2a} + P_{2b}$$

$$V_2 = V_{2a} = V_{2b}$$

$$V_1 = (h_{11a} + h_{11b}) I_1 + (h_{12a} + h_{12b}) V_2$$

$$P_2 = (h_{21a} + h_{21b}) P_1 + (h_{22a} + h_{22b}) V_2$$

Inter-relationship between different parameters

Express z-parameters in terms of T-para.

Step 1 Write z-parametric equations

$$V_1 = Z_{11} I_1 + Z_{12} I_2 \quad \text{--- (1)}$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2 \quad \text{--- (2)}$$

Step 2 Write t-parametric equations-

$$V_1 = A V_2 + B (-I_2) \quad \text{--- (3)}$$

$$I_1 = C V_2 + D (-I_2) \quad \text{--- (4)}$$

Step 3 - Compare the variables in eq (1) & (3),
- Replace V_2 in (3) using (4)

Step 4 From eq. (4)

$$V_2 = (I_1 + D I_2) / C \quad \text{--- (5)}$$

Use V_2 from (5) in (3)

$$V_1 = A \left[\frac{I_1 + D I_2}{C} \right] + B (-I_2)$$

$$= \frac{A}{C} I_1 + \frac{AD}{C} I_2 + B (-I_2)$$

$$V_1 = \frac{A}{C} I_1 + \left(\frac{AD - BC}{C} \right) I_2 \quad \text{--- (6)}$$

Compare eq (1) & (6)

$$Z_{11} = A / C$$

$$Z_{12} = ((AD - BC) / C) // \checkmark$$

Step 5 Compare (2) & (5)

All variables in eq (5) are present in eq (2)

but these positions are different.

$$V_2 = \frac{P_1}{C} + \frac{D P_2}{C} - \textcircled{3} \textcircled{5}$$

Compare $\textcircled{2}$ & $\textcircled{5}$

$$Z_{21} = 1/C$$

$$Z_{22} = D/C$$

~~Re~~ Step ① Write h parameters

$$V_1 = h_{11} P_1 + h_{12} V_2 \quad \textcircled{1}$$

$$P_{21} = h_{21} P_1 + h_{22} V_2 \quad \textcircled{2}$$

~~Re~~ Step ② T-parameters

$$V_1 = A V_2 + B (-P_2) - \textcircled{3}$$

$$P_1 = C V_2 + D (-P_2) - \textcircled{4}$$

~~Re~~ Step ① $V_1 = Z_{11} P_1 + Z_{12} F_2 - \textcircled{1}$

$$V_2 = Z_{21} P_1 + Z_{22} P_2 - \textcircled{2}$$

~~Re~~ Step ② $P_1 = Y_{11} V_1 + Y_{12} V_2 - \textcircled{3}$

$$P_2 = Y_{21} V_1 + Y_{22} V_2 - \textcircled{4}$$

Reciprocity Conditions

~~Def~~ If 2 port networks are said to be reciprocal if the reciprocal of the ratio of two response by the excitation remains unchanged even if their positions are interchanged.

Parameters.

Reciprocity Condition

w

Z

$$Z_{12} = Z_{21}$$

Y

$$Y_{12} = Y_{21}$$

T

$$AD - BC = 1$$

h_1

$$h_{12} = -h_{21}$$


Substitution Theorem

↳ Non Linear & Time varying

It states that in particular edge / branch N/W are circuit can be replaced by in a suitable voltage source, current source combination of voltage source along with impedance provided that the voltage & current in other remain untouched.

Limitations :-

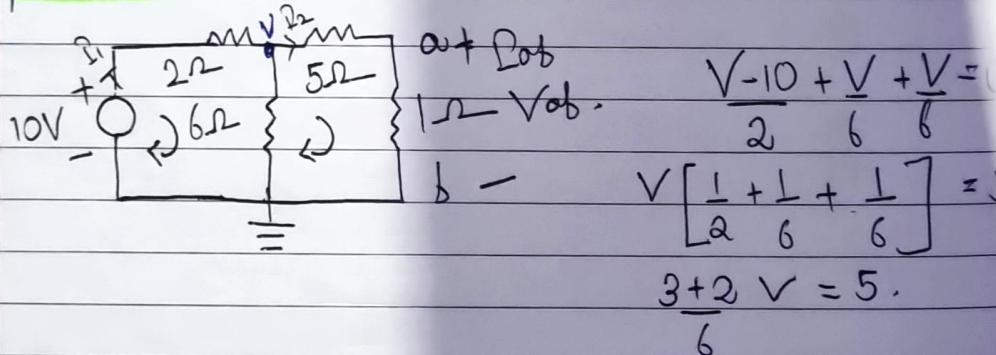- ① Not useful for circuit / N/W having components.
- ② The voltage & current of the branch to be placed must be known.



$$I_{ob} = V / 6 = 1 \text{ amp}$$

$$V_{ob} = I_{ob} \times 1 = 1 \text{ Volt}$$

Replace 1Ω resistance by 1 volt voltage source

$$\frac{V-10}{2} + \frac{V}{6} + \frac{V-1}{5} = 0$$

$$\frac{26V - 60}{30} = 0 \Rightarrow V = 6 \text{ Volt}$$

$$P_{ab} = (V - 1) / 5 = 6 - 1 / 5 = 1 \text{ Amp}$$

~~Using KVL~~ : $\frac{V-10}{2} + V + 1 = 0$

$$3V - 30 + V + 6 = 0$$

$$4V = 24 \Rightarrow V = 6 \text{ V}$$

Using KVL

$$-6 + 5 \times 1 + V_{ab} = 0$$

$$V_{ab} = 1 \text{ V}$$

$$V_{ab} = V + IR$$

$$1 = V + R$$


Space State Analysis.

System
matrix input
motion
matrix
input coupling
matrix

$$\text{Output } X = AX + BU \leftarrow \text{state eq}$$

$$\text{Output } Y = CX + DV \leftarrow \text{O/P eq}$$

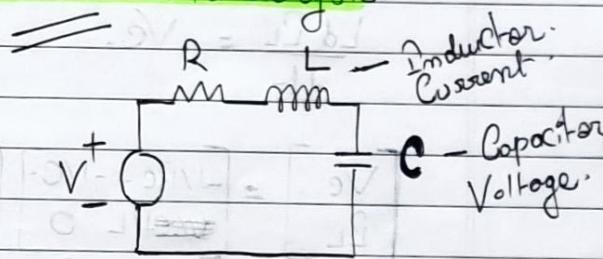Output
coupling
matrix
transmission
matrix.



$$CdV = L \frac{dI}{dt}$$

Using KVL

$$-V + R\frac{dI_L}{dt} + LdI_L + V_C = 0 \Rightarrow \frac{dV}{dt} = \frac{R}{L}I_L - \frac{V_C}{C}$$


$$\frac{dI_L}{dt} = \frac{V_C}{L} - \frac{V}{R}$$

$$L \frac{dI_L}{dt} = V - R\frac{dI_L}{dt} - V_C \Rightarrow -\frac{R}{L}\frac{dI_L}{dt} - \frac{V_C}{L} + \frac{V}{R} = 0 \quad (2)$$

State eq

$$\begin{bmatrix} V_C \\ I_L \end{bmatrix} = \begin{bmatrix} 0 & 1/C \\ -1/L & -R/L \end{bmatrix}_{2 \times 2} \begin{bmatrix} V_C \\ I_L \end{bmatrix} + \begin{bmatrix} 0 \\ 1/L \end{bmatrix}_{2 \times 1} \quad (3)$$

20. 9. 22

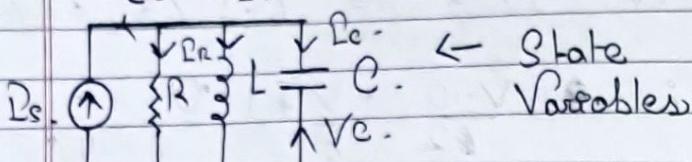 $V_C \cdot \Omega_L$ 

$\stackrel{I_L}{\text{Inductor current } I_L}$ State

$\stackrel{V_C}{\text{Capacitor voltage } V_C}$ State Variables

$$\Omega_R + \Omega_L + \Omega_C = \Omega_s.$$


$$\frac{V_C}{R} + \cancel{\frac{dI_L}{dt}} \Omega_L + C \frac{dV_C}{dt} = \Omega_s.$$

$$C \frac{dV_C}{dt} = \Omega_s - \Omega_L - \frac{V_C}{R} \Rightarrow \frac{dV_C}{dt} = \frac{\Omega_s}{C} - \frac{\Omega_L}{C} - \frac{V_C}{RC}.$$

$$x = Ax + Bu$$

$$\frac{dI_L}{dt} = V_C \quad \frac{dI_L}{dt} = \frac{V_C}{L} - \textcircled{2}$$
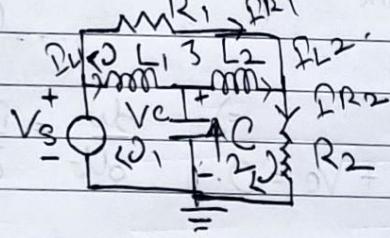
$$\begin{bmatrix} V_C \\ I_L \end{bmatrix} = \begin{bmatrix} -1/R & -1/C \\ 0 & 1/L \end{bmatrix} \begin{bmatrix} V_C \\ I_L \end{bmatrix} + \begin{bmatrix} -1/C & 0 \\ 0 & \Omega_s \end{bmatrix}$$



$$\text{KCL at } b: C \frac{dV_C}{dt} - \Omega_{L1} - \Omega_{L2} = 0$$

$$\frac{dV_C}{dt} = \Omega_{L1} - \Omega_{L2} \text{ } \textcircled{1}$$

Three state variables

Three state equations

$$L_1 \rightarrow \Omega_{L1} \rightarrow I_{L1} \quad \text{}$$

$$L_2 \rightarrow \Omega_{L2} \rightarrow I_{L2} \quad \text{}$$

$$C \rightarrow V_C \rightarrow V_C$$

$$\frac{dV_C}{dt} = \frac{\Omega_{L1}}{C} - \frac{\Omega_{L2}}{C} \text{ } \textcircled{1}$$

Applying KVL in loop ①

$$L_1 \frac{dI_{L_1}}{dt} + V_C - V_S = 0$$

$$\frac{dI_{L_1}}{dt} = \frac{V_S - V_C}{L_1} \approx ②$$

For KVL in Loop

$$R_1 I_{R_1} = L_2 \frac{dI_{L_2}}{dt} - L_1 \frac{dI_{L_1}}{dt} = 0$$

KVL in loop ②

$$-V_C + L_2 \frac{dI_{L_2}}{dt} + I_{R_2} R_2 = 0$$

$$\cancel{L_2} \frac{dI_{L_2}}{dt} = \text{unknown value}$$

$$I_{R_1} = [L_2 \frac{dI_{L_2}}{dt} + L_1 \frac{dI_{L_1}}{dt}] / R_1$$

$$L_2 \frac{dI_{L_2}}{dt} = L_1 \frac{dI_{L_1}}{dt} - R_1 I_{R_1}$$

$$③ \frac{dI_{L_2}}{dt} = L_1 \frac{dI_{L_1}}{dt} - R_1 \left[L_2 \frac{dI_{L_2}}{dt} + L_1 \frac{dI_{L_1}}{dt} \right]$$

Representation of state space equation

① Phase variable representation.

$$④ 7 \frac{d^3 Y}{dt^3} + 5 \frac{d^2 Y}{dt^2} + 2 \frac{dY}{dt} + 3Y = 6U$$

$$7\ddot{Y} + 5\dot{Y} + 2Y + 3Y = 6U$$

State variables are \Rightarrow

$$x_1, x_2, x_3 \text{ Let } Y = x_1, ① Y = x_3, ②$$

$$Y = x_2, ③ Y = \dot{x}_1$$

$$\text{Use eq } ② \Rightarrow x_1 = x_2 - A$$

Differentiate eq. ① \nearrow

Differentiate eq. ② -

$$\dot{Y} = \dot{x}_2$$

Use eq. ③ -

$$\dot{x}_2 = \dot{x}_3 -$$

Differentiate eq. ③ -

$$\dot{Y} = \dot{x}_3$$

$$7\dot{x}_3 + 5x_9 + 2x_2 + 3x_1 = 60.$$

$$\begin{aligned} x_3 &= (60 - 5x_9 - 2x_2 - 3x_1) / 7. \quad \textcircled{c} \\ &= \cancel{2}x - \cancel{5}x^2 - \cancel{2}x^2 - \cancel{3}x^1 \end{aligned}$$


$$\begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \\ \dot{x}_3 \end{bmatrix} = \begin{bmatrix} 0 & 1 & 0 \\ 0 & 0 & 1 \\ -3/7 & -2/7 & -5/7 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \\ x_3 \end{bmatrix} + \begin{bmatrix} 0 \\ 0 \\ 6 \\ 7 \end{bmatrix} u.$$

$$[Y] = [1 \ 0 \ 0] \begin{bmatrix} x_1 \\ x_2 \\ x_3 \end{bmatrix}$$

$$Y + 6Y + 7Y + 6Y + 5Y = 60.$$

$10 + 10 + 22$

Reciprocity condition for z-parameter

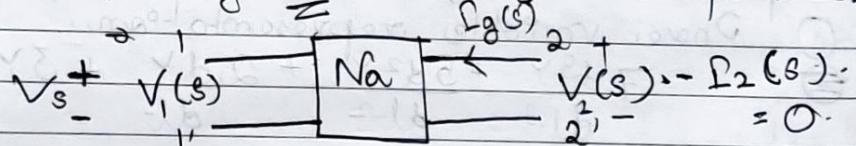

Condition ①

Apply α_s voltage source V_s at 1, 1' & short circuit the part 2, 2'.

Before making any changes at the terminals, z parametric eq. are:

$$V_1(s) = Z_{11} P_1(s) + Z_{12} P_2(s) \quad \text{--- (1)}$$

$$V_2(s) = Z_{21} P_1(s) + Z_{22} P_2(s) \quad \text{--- (2)}$$


Apply changes using com. ①.

From eq. ① & ②:

$$VS = Z_{11} P_1(s) + Z_{12} (-P_2(s)) \quad \text{--- (3)}$$

$$0 = Z_{21} P_1(s) + Z_{22} (-P_2(s)) \quad \text{--- (4)}$$
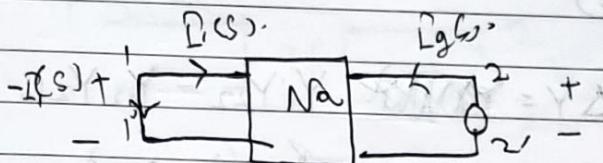
$$\frac{P_2(s)}{VS} = \frac{-Z_{21}}{Z_{11}Z_{22} - Z_{12}Z_{21}} \quad \text{--- (5)}$$



Apply a voltage source ~~at~~ VS at 2, 2' from the port 1, 1'.

Before making any changes at the terminals, 2 parametric eqn. are:

$$V_1(s) = Z_{11} P_1(s) + Z_{12} P_2(s) \quad \text{--- (1')}$$

$$V_2(s) = Z_{21} P_1(s) + Z_{22} P_2(s) \quad \text{--- (2')}$$

Applying changes using com. ②

$$0 = Z_{11} (-P_1(s)) + Z_{12} (P_2(s)) \quad \text{--- (6)}$$


$$VS = Z_{21} (-P_1(s)) + Z_{22} (P_2(s)) \quad \text{--- (7)}$$

$$\frac{P_2(s)}{VS} = \frac{-Z_{12}}{Z_{11}Z_{22} - Z_{12}Z_{21}}$$

For requirement of reciprocity from ⑤ & ⑧

$$Z_{12} = Z_{21}$$

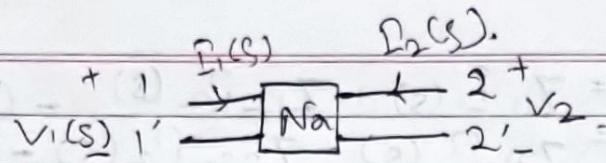This is applicable for all networks except ones having independent sources.



$$\underline{I}_1(s) = Y_{11}V_1(s) + Y_{12}V_2(s)$$

$$\underline{I}_2(s) = Y_{21}V_1(s) + Y_{22}V_2(s)$$

Apply current source $\underline{I}(s)$ at 1, 1' & open circuit the ports 2, 2'

$$\frac{V_2(s)}{I(s)} = \frac{\cancel{Y_{21}}V_1(s) - \cancel{Y_{22}}V_2(s)}{\cancel{Y_{11}} + \cancel{Y_{12}} - Y_{12}} = \frac{Y_{12}}{\Delta Y}$$

where $\Delta Y = \cancel{Y_{11}Y_{22}} - Y_{12}Y_{21}$

$$\frac{V_2(s)}{I(s)} = \frac{(Y_{11}s - Y_{12})}{(Y_{11}s + Y_{12})} = \frac{Y_{11}}{Y_{11} + Y_{12}}$$

Symmetry of two-port network

Definition: A two-port network is said to be symmetrical if parts can be interchanged without altering the port voltages & currents.


Currents parameters. Symmetry condition.

$$Z_{11} = Z_{22}$$

$$Y_{11} = Y_{22}$$

$$A = J$$

$$h_{11}h_{22} - h_{12}h_{21} = 1$$

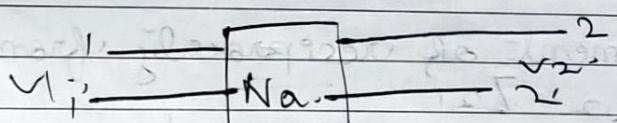

Z parameter -


$$V_1 = Z_{11} I_1 + Z_{12} I_2 \quad \text{--- (1)}$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2 \quad \text{--- (2)}$$

Apply a voltage source V_S at $1, 1'$ & open circuit the port $2, 2'$.

Then from eq (1) $V_S = Z_{11} I_1 \quad Z_{11} = V_S / I_1 \quad \text{--- (3)}$

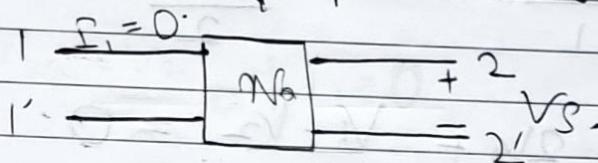Apply V_S at $2, 2'$ & open circuit at port $1, 1'$




from eq. (1)

$$V_2 = 0 + Z_{22} I_2$$

$$\frac{V_3}{I_2} = Z_{22}$$

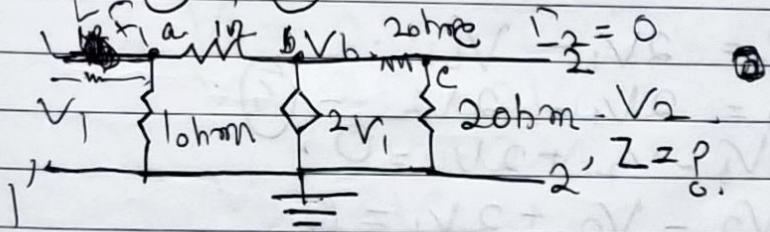In order for the Z-parameter to be symmetrical
from eq (2) & (3).



W

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

Put $I_2 = 0$ i.e. open circuit.

$$Z_{11} = \frac{V_1}{I_1} \quad | I_2 = 0$$

$$Z_{21} = \frac{V_2}{\frac{V_1}{2}} \quad I_{22} = 0.$$

✓ KCL at a -

$$I_1 = \frac{V_1}{1} + \frac{V_1 - V_a}{1}$$

$$I_1 = 2V_1 - V_a \quad \text{--- (1)} \quad \checkmark$$

w KCL at b -

$$\frac{V_b - V_1 + 2V_1 + V_b - V_2}{2} \quad \text{--- (2)} \quad V_a = V_2.$$

$$\frac{V_b - V_1 + 2V_1}{2} + \frac{V_b - V_2}{2} = 0.$$

$$2V_b - 2V_1 + 4V_1 + V_b - V_2 = 0$$

$$3V_b - V_2 = 0 \quad \text{--- (2)}$$

w KCL at C -

$$0 = \frac{V_a}{2} + V_2 - V_b. \quad \text{Also } V_a = V_1$$

$$0 = 2V_2 - V_b \quad \text{--- (3)}$$

$$\boxed{3V_b - 2V_2}$$

$$V_{12} = 2V_2$$

$$I_1 = 2V_1 - V_b.$$

$$I_1 = 2V_1 - 2V_2 \quad \text{--- (4)}$$

$$3V_b - V_2 + 2V_1 = 0,$$

$$6V_2 - V_2 + 2V_1 = 0$$

$$5V_2 + 2V_1 = 0.$$

$$V_2 = -\frac{2V_1}{5}$$

$$I_1 = 2V_1 - \frac{5}{2} \left(-\frac{2V_1}{5} \right)$$

$$\begin{aligned} & 2V + \frac{4V_1}{5} \\ & = \frac{14V_1}{5}. \end{aligned}$$

Put $\Omega_1 = 0$ & reopen circuit 1, 1'

$$Z_{12} = \frac{V_1}{\Omega_2} \quad | I_1 = 0$$

$$; V_h = V_1.$$

$$Z_{22} = \frac{V_2}{\Omega_2} \quad | I_1 = 0$$

$$\Omega_a = \frac{V_1}{1} = V_1 - ①$$

$$\Omega_b = V_1 + 2V_1$$

$$= 3V_1 - ②$$

$$\Omega_c = \frac{V_2}{2} - ③$$

$$\Omega_2 = \Omega_b + \Omega_c$$

$$\Omega_2 = 3V_1 + V_2/2 - ④$$

$$V_b = 2V_1.$$


$$V_2 = 2\Omega_b + 2V_1.$$

$$= 6V_1 + 2V_1$$

$$V_2 = 8V_1.$$

$$\Omega_2 = 3V_1 + \frac{8V_1}{5} = 3V_1 + 4V_1 = 7V_1$$

$$\Omega_2 = 7V_1.$$

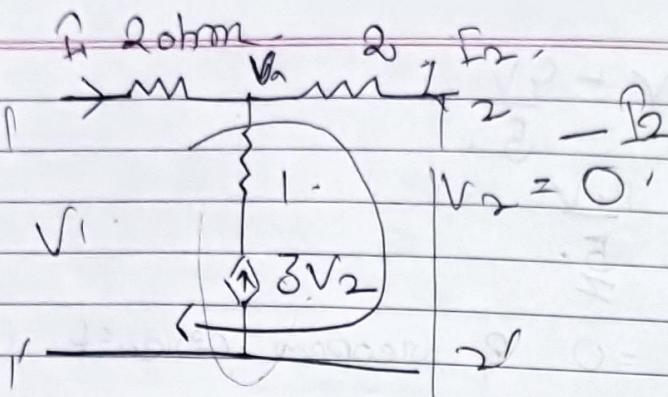

$$R_1 = Y_{11} V_1 + Y_{12} V_2$$

$$R_2 = Y_{21} V_1 + Y_{22} V_2$$

$$Y_{11} = \frac{I_1}{V_1} \quad | \quad V_2 = 0$$

$$Y_{21} = \frac{I_2}{V_1} \quad | \quad V_2 = 0$$

$$\frac{V_a - V_1}{2} - 3V_2 - 2I_2 = 0$$

~~$$V_a - V_1 - 6V_2 - 2I_2 = 0$$~~

~~$$V_a - 7V_1 - 2I_2 = 0 \quad \text{(2)}$$~~

KVL in outer loop:

$$V_1 = 2I_1 - 2I_2$$

$$V_1 = 2I_1 + V_a \quad \text{(3)}$$

$$7V_1 = V_a - 2I_2 \quad \text{(4)}$$

~~V_a~~ = Substituting value of (4) in eq(3)

~~$V_a - 2I_2 = 2I_1 - 2I_2$~~

$$V_a - 2I_2 = 7(2I_1 - 2I_2)$$


$$V_a - 2I_2 = 14I_1 - 14I_2$$

$$12I_2 = 14I_1 - V_a$$

$$I_2 = \frac{7I_1 - \frac{V_a}{12}}{6}$$

$$I_2 = -\frac{7I_1}{12} -$$

$$Y_{22} = R_2 / V_2 \quad | \quad V_1 = 0$$

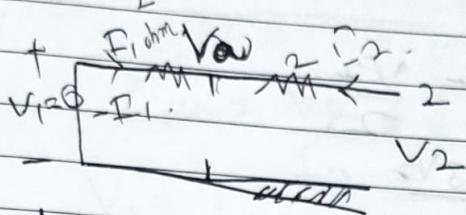

$$V_2 = 4R_2$$

$$\frac{F_2}{V_2} = 1 \text{ inho.} - \textcircled{2}$$

V2

$$+ \frac{\sum_1}{V_2} \text{ am } b \cdot \frac{F_2}{V_2} = 0$$

$$V_1 \quad \left\{ \begin{array}{l} 1 \\ 2 \end{array} \right\} + \left\{ \begin{array}{l} 2 \\ 3 \end{array} \right\} V_1 - \left\{ \begin{array}{l} 3 \\ 2 \end{array} \right\} V_2 = 0$$

~~000000~~

$$P_{oL} \quad R_2 = 0 \cdot V$$

$$Z_{11} = V_1 / R_{11}, \quad | \quad R_2 = 0$$

$$Z_{21} = V_2 / R_1, \quad | \quad R_2 = 0$$

KCL at node 'a'

$$F_1 = V_1 + V$$

$$2 \textcircled{1} = V_1 \quad 2 F_1 = V_1 - V_2$$

$$2 F_1 = \frac{V_1 - V_2}{2} - \textcircled{1}$$

KCL @ node b.

$$0 = \frac{V_2}{3} + \frac{V_2 + 2V_1 - V_1}{2} \quad \cancel{+} \quad \cancel{V_2 + 2V_1 - V_1}$$

$$2V_2 + 3V_2 + 6V_1 - 3V_1 = 0$$

$$5V_2 + 3V_1 = 0$$

$$3V_1 = -5V_2 / 3$$

$$F_1 = -\frac{8V_2}{6}$$

~~$$F_1 = -4V_2 / 3$$~~

$$\frac{V_2}{F_1} = \frac{3}{4} V$$

$$3V_1 = -5V_2$$

3.

$$\underline{\underline{I_1}} = \frac{-5V_2}{6} - \frac{V_2}{2}$$


$$= \frac{-5V_2 - 3V_2}{6}$$

6.

$$= \frac{-8V_2}{6} = \frac{-4V_2}{3}$$

$$\frac{V_2}{I_1} = -\frac{3}{4}$$

$$Z_{11} = V_1 / I_1$$

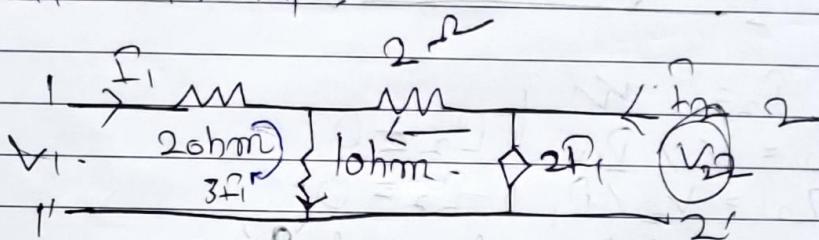

$$Z_{11} = V_1 / I_1 \quad | \quad R_2 = 0 \Omega$$

$$Z_{21} = V_2 / I_1 \quad | \quad R_2 = 0 \Omega$$

$$V_1 = 2R_1 + 3R_1 \times 1$$

$$= 5R_1 = 0$$


$$\frac{V_1}{R_1} = 5 \text{ ohm}$$

KVL in middle loop -

$$V_2 = 2 \times 2 \Omega + 3 \Omega \times 1$$

$$V_2 = (4 + 3) \Omega$$
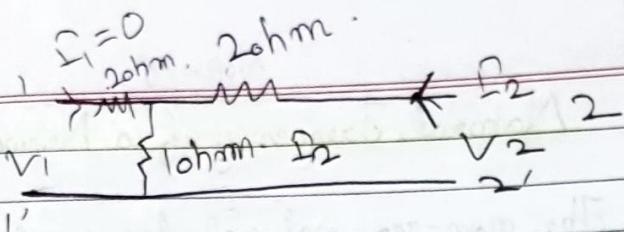
$$Z_{21} = \frac{V_2}{R_1} = 7 \text{ ohm}$$



$$Z_{22} = \frac{V_2}{I_2} = 30 \text{ ohm}$$

$$V_1 = I_2 \times R_1$$

$$Z_{12} = \frac{V_1}{I_2} = 10 \text{ ohm}$$

~~10~~

$$(89-2)(49-2)(19-2)18 \dots H = 500 \text{ L}$$

$$(62-2)(8-2)$$

$$1 = 4$$

$$2 \text{ GENE} \quad 0 \text{ GENE} \quad 0 \text{ GENE} \quad 0 \text{ GENE}$$

$$0 \text{ GENE} \quad 0 \text{ GENE} \quad 0 \text{ GENE} \quad 0 \text{ GENE}$$

$$0 \text{ GENE} \quad 0 \text{ GENE} \quad 0 \text{ GENE} \quad 0 \text{ GENE}$$

$$(89-2)(49-2)(19-2)18 \dots H = 500 \text{ L}$$

$$(89-2)(49-2)$$